



KIIT, Deemed to be University
School of Electronics Engineering
Digital System Design Laboratory [EC 29005]

EXPERIMENT - 7

Aim:

Design and simulation of a pseudo random sequence generator in Verilog.
Implementation of pseudo random sequence generator using shift register.

Component/Software Used:

Component/Software	Specification
ICs	7495,7486
Bread Board, Power supply, LEDs, Resistors, Switches, Connecting wires	As per requirement
Software(s) Used	Vivado 2016.1

Theory:

A register is a device capable of storing a number of bits. We know that a flip-flop has a memory element. Thus, flip-flop can be connected together to form a register. A register capable of shifting the binary information held in each cell to its neighboring cell, in a selected direction is called a shift register.

Shift registers are synchronous sequential circuits consists of a group of flip-flops connected so that each flip-flop transfers its bit of data to the next flip-flop of the register when a clock pulse arrives. Data may have to be shifted left or shifted right. We have shifted left and shifted right registers.

An n - bit register consists of a group of n flip-flops capable of storing n bits of binary information. In addition to the flip-flops, a register may have combinational gates that perform certain data-processing tasks. The flip-flops hold the binary information. and the gates determine how the information is transferred into the register.

Serial in - Serial out:

The data is loaded into and read from the shift register serially. Fig.7.1 shows the circuit of a 4-bit serial in-serial out (SISO) shifts right register using four D flip-flops. The Q outputs of one state (FF) are connected to the D input of the next state(FF). Thus, the inputs to second, third and fourth flip-flop are conditioned by their preceding flip-flops. The data in each flip-flop is shifted to the next flip-flop on the arrival of a positive edge of clock pulse. Since it is a 4 bit register, 4 clock pulses are required to shift the data through this register.

 


Figure 7.1: Logic diagram of 4 bit serial-in serial-out shift register

The data shifting in the 4-bit SISO is summarized below in the Table.7.1 with an example of 4 bit data "1110". Load the shift register with a 4-bit data ' $B_3B_2B_1B_0$ ' one by one serially. In the 1st clock pulse, B_0 is shifted to Q_1 (FF1). In the 2nd clock pulse, B_0 is shifted to Q_2 (FF2) and B_1 is shifted to Q_1 (FF1). In the 3rd clock pulse, B_0 is shifted to Q_3 (FF3), B_1 is shifted to Q_2 (FF2) and B_3 is shifted to Q_1 (FF1). At the end of 4th clock pulse, B_0 is shifted to Q_4 (FF4), B_1 is shifted to Q_3 (FF3), B_2 is shifted to Q_2 (FF2) and B_3 is shifted to Q_1 (FF1). In the next clock pulse, the second data ' B_1 ' will appear at Q_4 (FF4). In the next clock pulse, the third data ' B_3 ' will appear at Q_4 (FF4). Application of next clock pulse will enable the 4th data ' B_3 ' to appear at Q_4 (FF4). Thus the data applied serially at the input comes out serially at Q_4 (FF4).

Clock	Serial I/P	Q_1	Q_2	Q_3	Q_4
1	$B_0 = 0$	0	X	X	X
2	$B_1 = 1$	1	0	X	X
3	$B_2 = 1$	1	1	0	X
4	$B_3 = 1$	1	1	1	0
5	X	X	1	1	1
6	X	X	X	1	1
7	X	X	X	X	1

Table 7.1: Truth table of 4-bit SISO shift register

Parallel in-Parallel out:

The data is loaded in parallel and read from the register in parallel, i.e., all bits are loaded simultaneously and read simultaneously. Figure 7.2 shows the circuit of a 4-bit parallel in-parallel out (PIPO) shifts right register using four D flip-flops. The data in each flip-flop is shifted to the output the arrival of a positive edge of clock pulse. Output terminals and data are available at all of them together. The parallel data bits are $B_0B_1B_2B_3$ and $Q_1, Q_2, Q_3,$ and Q_4 are parallel data outputs. After one clock pulse, all the input data is available in the outputs.

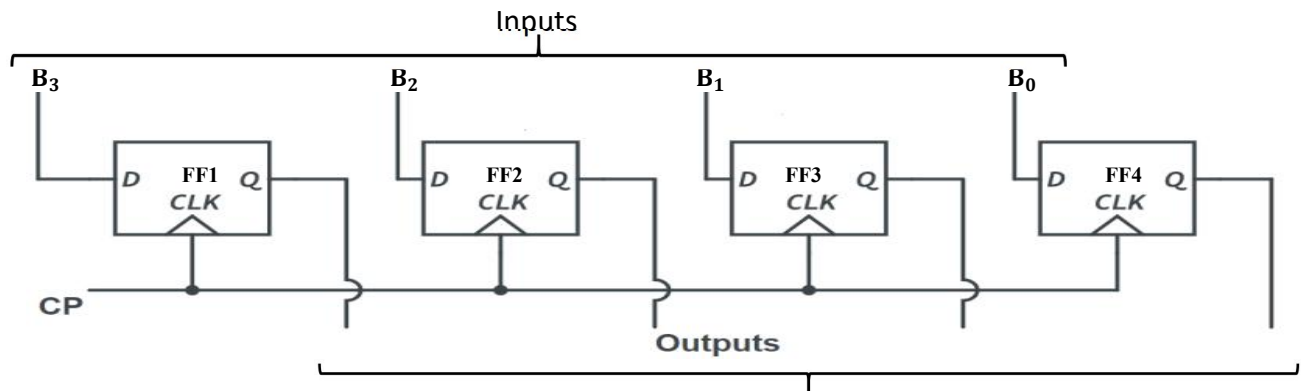


Figure 7.2: Logic diagram of PIPO shift register

Serial in-Parallel out: The data is loaded into the register serially but read in parallel mode, i.e., data is available from all flip-flops simultaneously. Figure 7.3 shows the circuit of a 4-bit serial in-parallel out (SIPO) shifts right register using four D flip-flops. The Q outputs of one state are connected to the D input of the next state. Thus, the inputs to second, to the third and fourth flip-flop are conditioned by their preceding flip-flops. The data in each flip-flop is shifted to the next flip-flop on the arrival of a positive edge of the clock pulse. Output terminals and data are available at all of them together. Since it is a 4 bit register, after 4 clock pulses we see all the data is available in the outputs of this register.

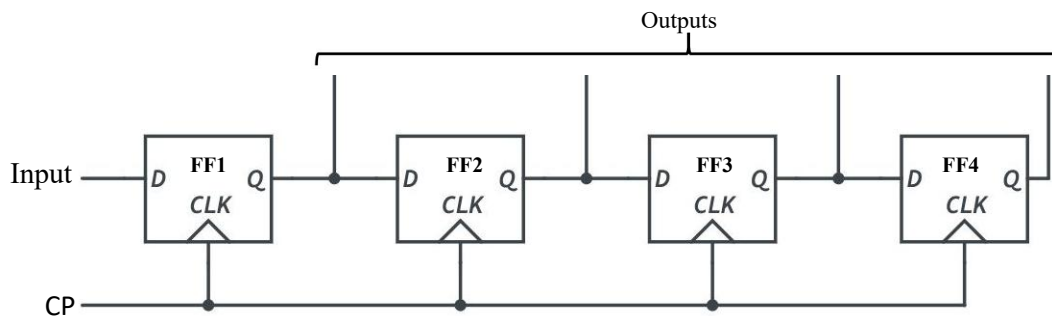


Figure 7.3: Logic diagram of SIPO shift register

The data shifting in the 4-bit SIPO is summarized below in the Table.7.2 with an example of 4 bit data "1110". Load the shift register with a 4-bit data 'B₃B₂B₁B₀' one by one serially. In the 1st clock pulse, B₀ is shifted to Q₁(FF1). In the 2nd clock pulse, B₀ is shifted to Q₂ (FF2) and B₁ is shifted to Q₁(FF1). In the 3rd clock pulse, B₀ is shifted to Q₃(FF3), B₁ is shifted to Q₂(FF2) and B₂ is shifted to Q₁(FF1). At the end of 4th clock pulse, B₀ is shifted to Q₄(FF4), B₁ is shifted to Q₃(FF3), B₂ is shifted to Q₂ (FF2) and B₃ is shifted to Q₁(FF1). Thus after 4th clock pulse all the outputs are available.

Clock	Serial I/P	Q ₁	Q ₂	Q ₃	Q ₄
1	B ₀ = 0	0	X	X	X
2	B ₁ = 1	1	0	X	X
3	B ₂ = 1	1	1	0	X
4	B ₃ = 1	1	1	1	0

Table 7.2: Truth table of 4-bit SIPO shift register

Parallel in-Serial out: The data is loaded in parallel form and read serially. Figure 7.4 shows the circuit of a 4-bit parallel in-serial out (PISO) shifts right with four bits. It uses D flip-flops and four data input lines: B₀ (LSB), B₁, B₂, and B₃ (MSB).

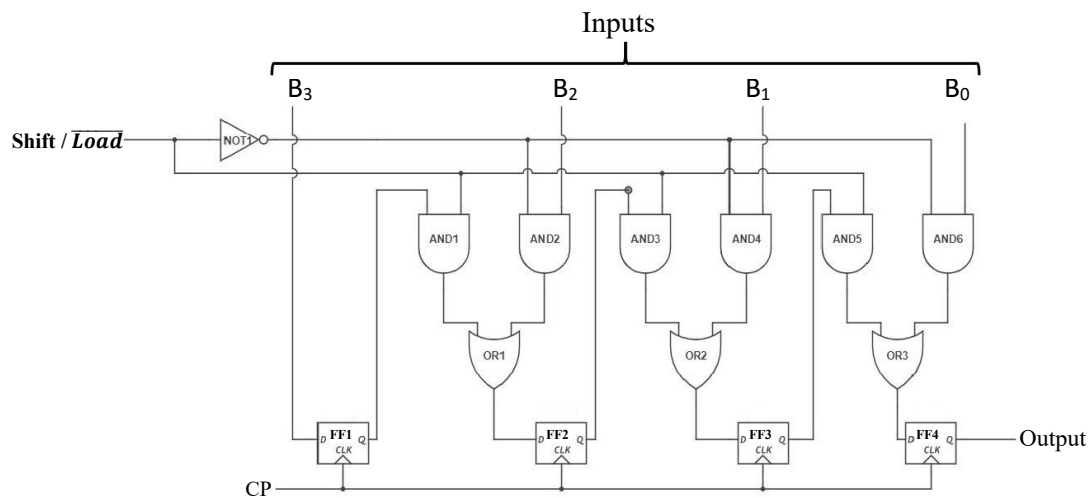


Figure 7.4: Logic diagram of PISO shift register

The data shifting in the 4-bit PISO is summarized below in the Table 7.3 with an example of 4 bit data "1110". Load the shift register with a 4-bit data 'B₃B₂B₁B₀' simultaneously in the 1st clock pulse. In the 2nd clock pulse, B₃ is shifted to Q₂ (FF2), B₂ is shifted to Q₃ (FF3) and B₁ is shifted to Q₄ (FF4). In the 3rd clock pulse, B₃ is shifted to Q₃ (FF3) and B₂ is shifted to Q₄ (FF4). At the end of 4th clock pulse B₃ is shifted to Q₄ (FF4).

Clock	Parallel I/P	Q ₁	Q ₂	Q ₃	Q ₄
1	B ₃ B ₂ B ₁ B ₀ = 1110	1	1	1	0
2		X	1	1	1
3		X	X	1	1
4		X	X	X	1

Table 7.3: Truth table of 4-bit PISO shift register

IC7495:

The IC-7495 is a 4-Bit Shift Register with serial and parallel synchronous operating modes. The serial shift right and parallel load are activated by separate clock inputs which are selected by a mode control input. The data is transferred from the serial or parallel D inputs to the Q outputs synchronous with the HIGH to LOW transition of the appropriate clock input. It has a Serial (D_S) and four Parallel (P₀ – P₃) Data inputs and four Parallel Data outputs (Q₀ – Q₃). The serial or parallel mode of operation is controlled by a Mode Control input (S) and two Clock Inputs (\overline{CP}_1) and (\overline{CP}_2). The serial (right-shift) or parallel data transfers occur synchronous with the HIGH to LOW transition of the selected clock input.

 


Figure 7.5: Pin diagram of IC 7495

Pin No	Pin Name	Pin Description
1	D _S	Serial Data Input
2 to 5	P ₀ to P ₃	Parallel Data Inputs 0 to 3
6	S	Mode Control Input
7	GND	Ground Pin
8	\overline{CP}_2	Negative edge Parallel Clock input
9	\overline{CP}_1	Negative edge Serial Clock input
10 to 13	Q ₃ to Q ₀	Parallel Outputs 3 to 0
14	Vcc	Supply Voltage

Table 7.4: Pin description of IC 7495

When the Mode Control input ($S = 1$) is HIGH, \overline{CP}_2 is enabled. A HIGH to LOW transition on enabled \overline{CP}_2 transfers parallel data from the P₀ – P₃ inputs to the Q₀ – Q₃ outputs.

When the Mode Control input ($S = 0$) is LOW, \overline{CP}_1 is enabled. A HIGH to LOW transition on enabled \overline{CP}_1 transfers the data from Serial input (D_S) to Q₀ and shifts the data in Q₀ to Q₁, Q₁ to Q₂, and Q₂ to Q₃ respectively (right-shift).

A left-shift is accomplished by externally connecting Q₃ to P₂, Q₂ to P₁ & Q₁ to P₀ and operating the IC7495 in the parallel mode ($S = 1$) HIGH.

For normal operation, S should only change states when both Clock inputs are LOW. However, changing S from LOW to HIGH while \overline{CP}_2 is HIGH, or changing S from HIGH to LOW while \overline{CP}_1 is HIGH and CP₂ is LOW will not cause any changes on the register outputs.

Implementation of various shift registers using IC 7495 has been show below.

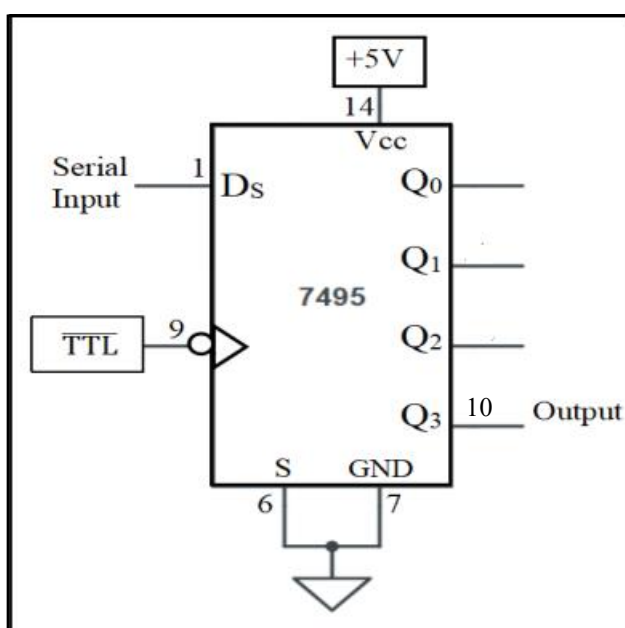


Figure 7.6: Logic diagram of 4 bit SISO shift register using IC 7495

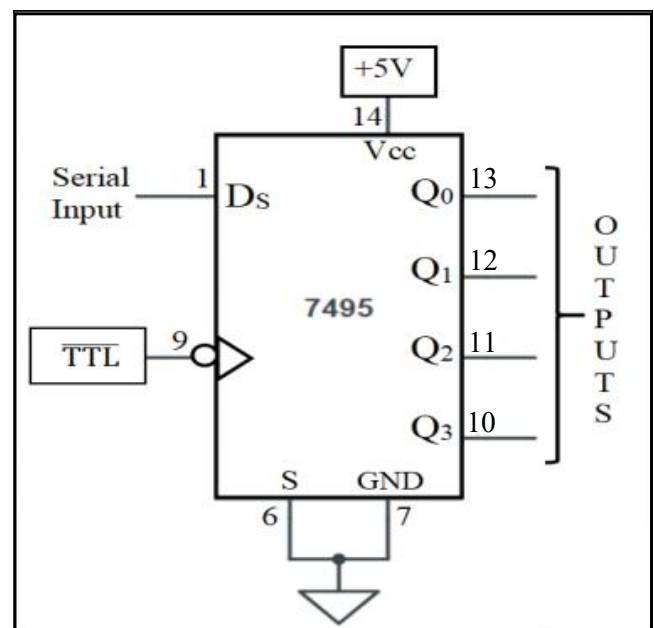


Figure 7.7: Logic diagram of 4 bit SIPO shift register using IC 7495

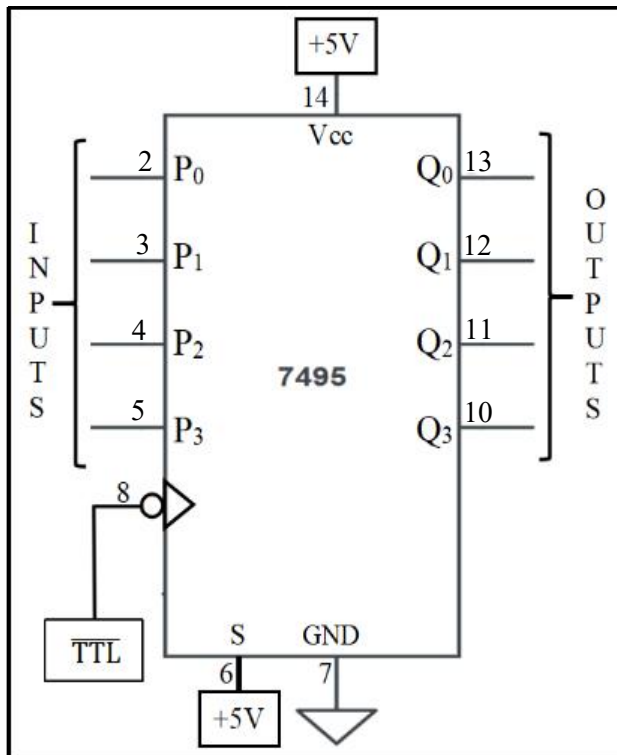


Figure 7.8: Logic diagram of 4 bit PIPO shift register using IC 7495

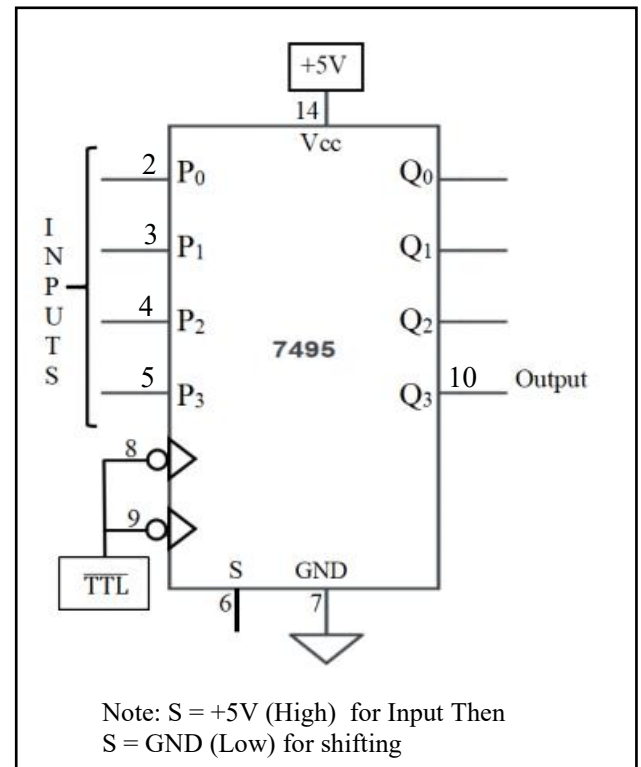


Figure 7.9: Logic diagram of 4 bit PISO shift register using IC 7495

Pseudo Random Sequence generator:

The sequence generator digital circuit which generates a set of outputs. This is a shift register where the input is a combinational logic function of the outputs of the flip-flops of the shift register. The sequence generator generates a sequence of binary bits. Thus, the length of the sequence is related to the number of flip-flops that are required to design a sequence generator. These generators are utilized in a wide variety of applications like coding and control. The length of the sequence is related to the number of flip-flops that are required to produce a sequence generator.

$$L \leq 2^n - 1$$

where **L** is the length of the sequence and **n** is the minimum number of flip-flops required.

Designing of a sequence generator is shown using IC7495 for the sequence “1101001”.

Q ₀	Q ₁	Q ₂	Q ₃	D _s
1	1	0	0	1
1	1	1	0	0
0	1	1	1	1
1	0	1	1	0
0	1	0	1	0
0	0	1	0	1
1	0	0	1	1

Q ₂ Q ₃					
Q ₀ Q ₁		00	01	11	10
		00	01	11	10
00		X	X	X	1
01		X		1	X
11		1	X	X	
10		X	1	X	X

Table 7.5: Truth Table of the Sequence Generator

K-Map for the Input(D_s) of the shift register

$$D_s(Q_0, Q_1, Q_2, Q_3) = \sum (2,7,9,12) + d(0,1,3,4,6,8,10,13,15) = Q_2 \oplus Q_0$$

Boolean expression for the input D_s

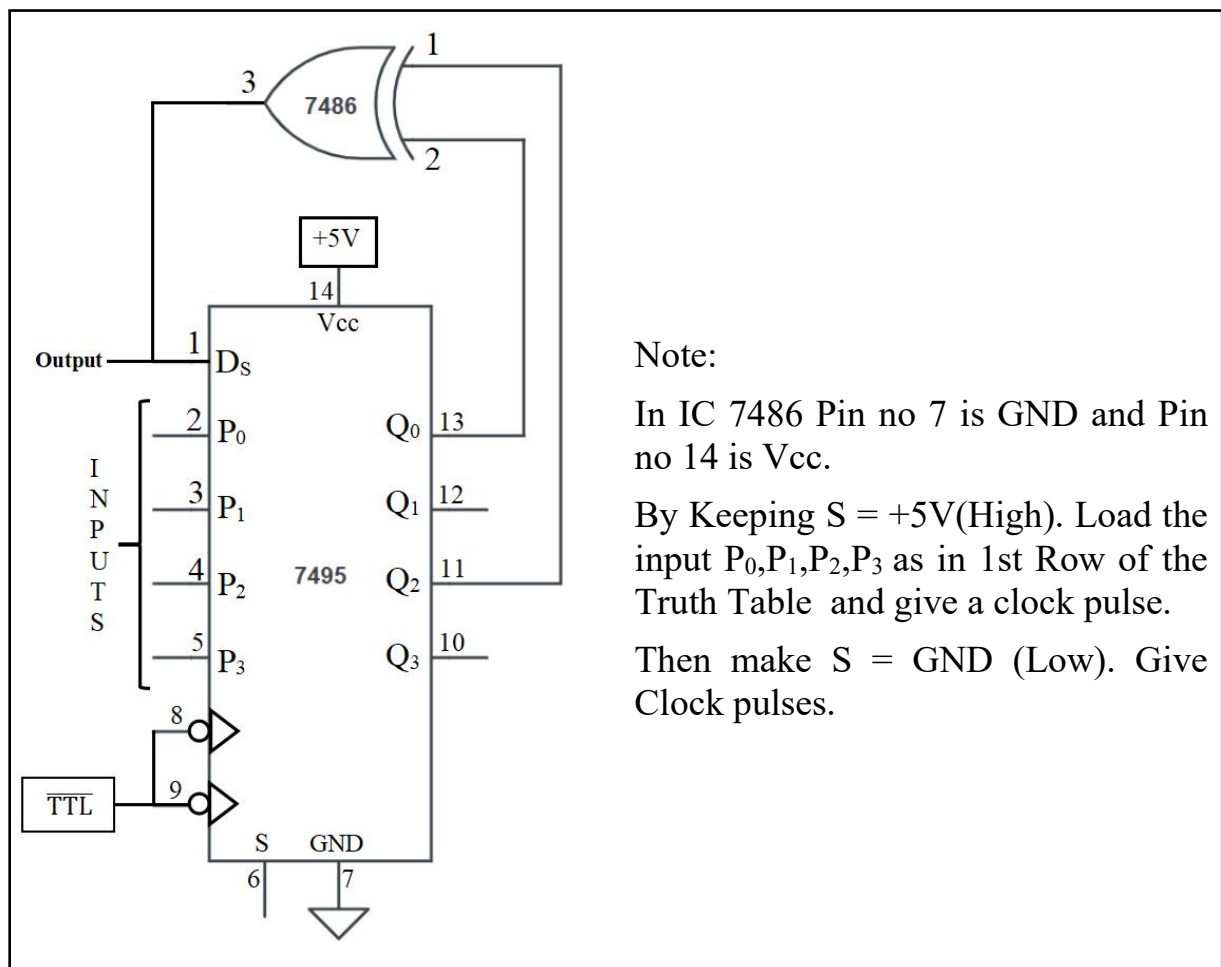


Figure 7.10: Logic diagram of “1101001” sequence generator using IC 7495

Procedure

For Software Simulation:

- a) Create a module with required number of variables and mention it's input / output.
- b) Write the description of given Boolean function using operators or by using the built in primitive gates.
- c) Synthesize to create RTL Schematic.
- d) Create another module referred as test bench to verify the functionality and to obtain the waveform of input and output.
- e) Follow the steps required to simulate the design and compare the obtained output with the corresponding truth table.
- f) Take the screenshots of the RTL schematic and simulated waveforms.

Note: Students need to write the Verilog HDL code by their own for which they can refer Appendix - A if required.

For Hardware implementation:

- a) Turn off the power of the Trainer Kit before constructing any circuit.
- b) Connect **power supply (+ 5 V DC)** pin and **ground** pin to the respective pins of the trainer kit.
- c) Place the ICs properly on the bread board in the Trainer Kit.
- d) Connect VCC and GND pins of each chip to the power supply and ground bus strips on the bread board.
- e) Connect the input and output pins of chips to the input switches and output LEDs respectively in the Trainer Kit.
- f) Check the connections before you turn on the power.
- g) Apply various combinations of inputs according to truth tables and observe outputs of LEDs.

Observation:

To be written by students

Design Problem

Design and Simulation of 4 bit Ring counter and 4 bit Johnson counter using Verilog HDL.

Hardware implementation of 4 bit Ring counter and 4 bit Johnson counter.

Solution:

Ring Counter:

Ring counter is a sequential logic circuit that is constructed using shift register. Same data recirculates in the counter depending on the clock pulse. It consists of a group of flip-flops connected in a circular chain or "ring" formation, where the output of one flip-flop is connected to the input of the next, and the last flip-flop is connected back to the first.

When a clock pulse is applied to the ring counter, the data is shifted from one flip-flop to the next, with each flip-flop in the ring taking turns being in the "high" or "low" state. The output of each flip-flop represents a different bit of the counter's binary value, with the least significant bit (LSB) being the first flip-flop in the ring, and the most significant bit (MSB) being the last flip-flop.

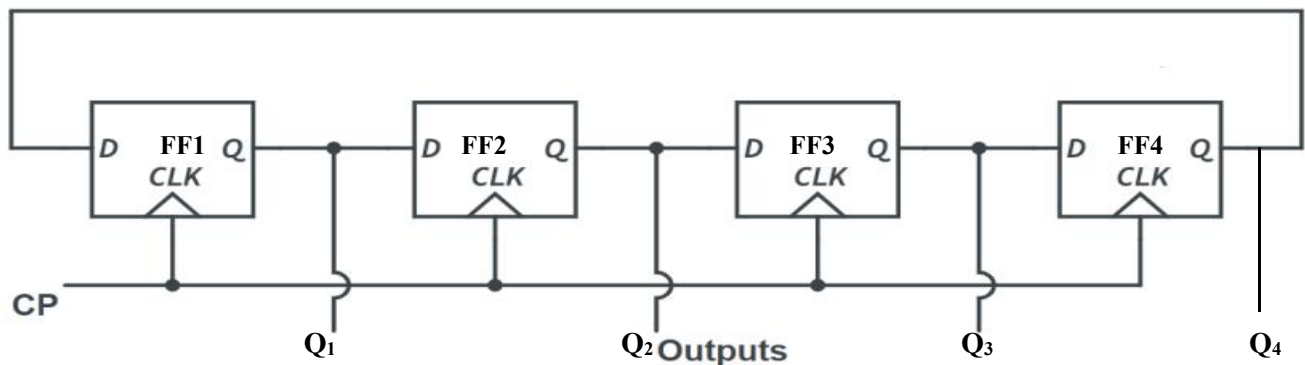


Figure 7.11: Logic diagram of 4 bit Ring Counter

Assume, initial status of the D flip-flops from leftmost to rightmost is $Q_1 Q_2 Q_3 Q_4 = "1000"$. This status repeats for every four(4) clock pulse. which is shown in below Table 7.6. A "mod-n" ring counter will require "n" number of flip-flops connected together to circulate a single data bit providing "n" different output states. Each state repeats after every "n" clock pulse.

Clock Pulse	Q_1	Q_2	Q_3	Q_4
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	0	0	0	1
4	1	0	0	0

Table 7.6: Truth table of 4-bit Ring Counter

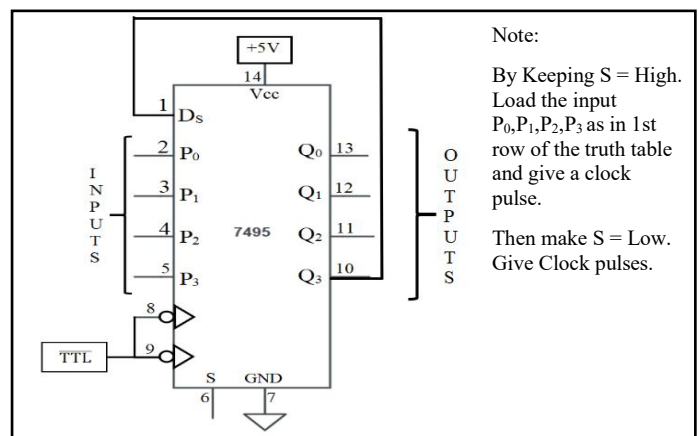


Figure 7.12: Logic diagram of Ring Counter using IC 7495

Johnson Counter:

A Johnson counter is a type of shift register that is similar to a ring counter, but with an additional invert stage. It is sometimes also called a "twisted ring counter" counter". The operation of a Johnson counter is similar to that of a ring counter, with each flip-flop output changing state on each clock pulse. However, in a Johnson counter, the output of the last flip-flop is inverted and fed back into the first flip-flop. This causes the counter to cycle through a sequence of states that includes both ascending and descending binary values.

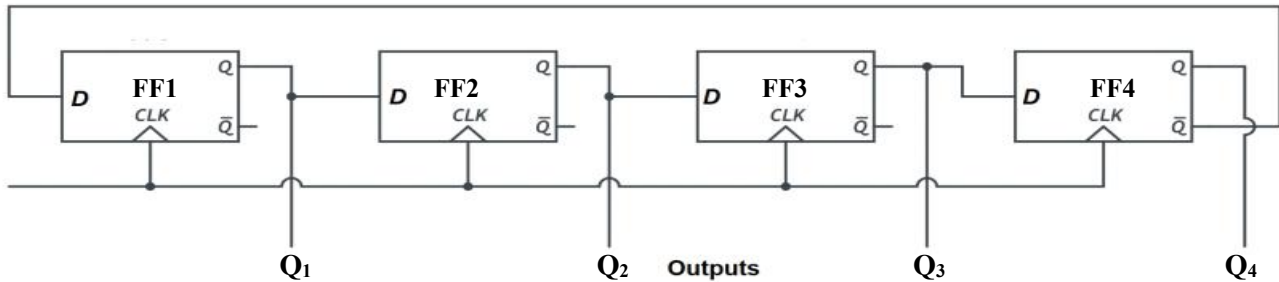


Figure 7.13: Logic diagram of Johnson Counter

Assume, initial status of the D flip-flops from leftmost to rightmost is $Q_1 Q_2 Q_3 Q_4 = "0000"$. This status repeats for every Eight (8) clock pulse which is shown in below Table 7.7.

A "mod- $2n$ " ring counter will require " n " number of flip-flops connected together to circulate a single data bit providing " $2n$ " different output states. Each state repeats after every " $2n$ " clock pulse.

Clock Pulse	Q_1	Q_2	Q_3	Q_4
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1

Table 7.7: Truth table of 4-bit Johnson Counter

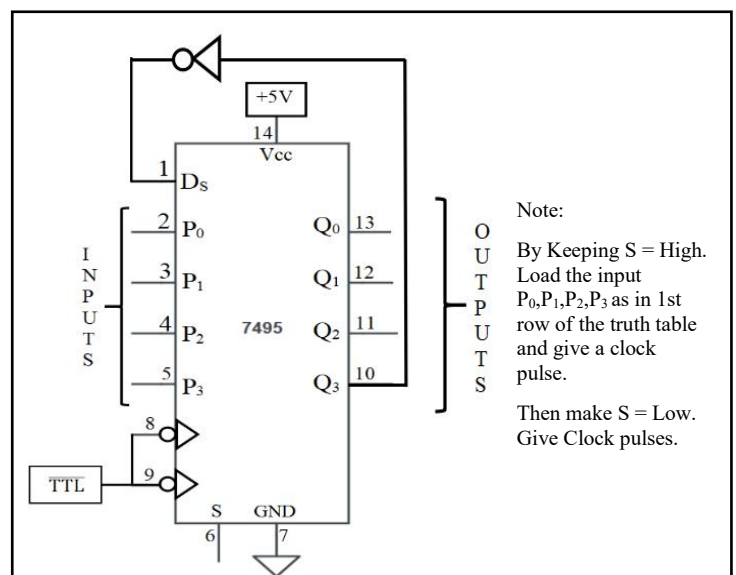


Figure 7.14: Logic diagram of 4-bit Johnson Counter using IC 7495

Conclusion:

To be written by students.

Sample viva-voice questions

1. What do you mean by serial and parallel data?
2. What is a register?
3. What are the types of loading the registers?
4. What is the basic difference between a shift register and a counter?
5. What are the applications of shift registers?
6. How will you use a shift register to multiply or divide a binary number by 2?
7. What are the basic types of shift registers?
8. What is a bi-directional shift register?
9. What is a universal shift register?
10. What is the advantage and disadvantage of ring counter?

