

EXPERIMENT - 1

- **AIM** Design and Simulation of boolean functions using Verilog HDL. Hardware implementation of a Boolean function in sum of products and product of sums expressions using Universal gates

■ **COMPONENT / SOFTWARE USED**

- ① ICs - 7400, 7402
- ② Breadboard, power supply, LED's, Resistors, Switches, Connecting wires
- ③ Software(s) used - Vivado 2016.1

■ **THEORY**

A binary variable may appear either in its normal form (A) or in its complement form (\bar{A}). Binary variables combined with an AND operations is called minterms or standard product. Similarly binary variables forming an OR terms called maxterms, or standard sums. For " n " variables with each variable being primed or unprimed, provide " 2^n " possible minterms or maxterms.

The eight (2^3) different minterms and maxterms are shown in the table for three (3) variables.

A boolean function can be expressed algebraically from the given truth table by forming a minterm for each combination of the variables that produces a "1" in the boolean function can alternatively be written algebraically by constructing a maxterm for each combination of variables that yields a "0" in

Teacher's Signature : _____

			Minterms		Maxterms	
A	B	C	Term	Designation	Term	Designation
0	0	0	$\bar{A}\bar{B}\bar{C}$	m_0	$A+B+C$	M_0
0	0	1	$\bar{A}\bar{B}C$	m_1	$A+B+\bar{C}$	M_1
0	1	0	$\bar{A}B\bar{C}$	m_2	$A+\bar{B}+C$	M_2
0	1	1	$\bar{A}BC$	m_3	$A+\bar{B}+\bar{C}$	M_3
1	0	0	$A\bar{B}\bar{C}$	m_4	$\bar{A}+B+C$	M_4
1	0	1	$A\bar{B}C$	m_5	$\bar{A}+B+\bar{C}$	M_5
1	1	0	$AB\bar{C}$	m_6	$\bar{A}+\bar{B}+C$	M_6
1	1	1	ABC	m_7	$\bar{A}+\bar{B}+\bar{C}$	M_7

Minterms and Maxterms for 3 binary variables

Input			Output
A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Truth table of the boolean function
 $F(A,B,C) = A\bar{B}\bar{C} + A\bar{B}C + BC$

the function and then taking the AND of all these terms. Boolean functions expressed as sum of minterms or product of maxterms are said to be in canonical form. The two canonical forms are basic forms of expressing Boolean function which is obtained from reading a given function from the truth table.

Another way to express Boolean functions is in standard form. In digital logic, the "sum of products" (SOP) and "product of sums" (POS) are two distinct standard forms to describe a Boolean expression. These representations are used to simplify and analyze logic circuits.

Sum of Products (SOP): SOP is a Boolean expression containing AND terms, called product terms, with one or more literals each. The sum denotes the ORing of these terms.

Product of sums (POS): POS is a Boolean expression containing OR terms, called sum terms, with each term having any number of literals. The product denotes the ANDing of these terms.

Consider a Boolean function $F(A, B, C) = ABC + A\bar{B}C + BC$ for which the minterms and maxterms can be derived from the truth table shown. The function can be implemented with NAND gates as shown as well as NOR gates by considering POS expression.

NAND or NOR gates are called Universal gates. Digital circuits are frequently constructed with NAND or NOR gates rather than with AND and OR gates.

Teacher's Signature : _____

 


Fig: SOP Implementation of Boolean function using NAND gate

 


Fig: POS Implementation of Boolean function using NOR gate

$$\begin{aligned}
 \text{SOP: } F(A, B, C) &= m_1 + m_3 + m_6 + m_7 \\
 &= \sum (1, 3, 6, 7) = AB + \bar{A}C \\
 &= ((\bar{A}B)(\bar{A}C))
 \end{aligned}$$

$$\begin{aligned}
 \text{POS: } F(A, B, C) &= M_0 M_2 M_4 M_5 \\
 &= \prod (0, 2, 4, 5) = (A+C)(\bar{A}+B) \\
 &= ((\bar{A}+C) + (\bar{A}+B))
 \end{aligned}$$

PROCEDURE

For software simulation

- Create a module with required number of variables and mention its input/output.
- Write the description of given Boolean function using operators or by using the built in primitive gates
- Synthesize to create RTL schematic
- Create another module referred as test bench to verify the functionality and to obtain the waveform of input and output.
- Follow the steps required to stimulate the design and compare the obtained output with corresponding truth table.
- Take the screenshots of the RTL schematic and

For hardware simulation

- Turn off the power of the trainer kit before constructing any circuit.

Teacher's Signature : _____

File Edit Flow Tools Reports Window Layout View Help Quick Access

Implementation Complete ✓
Default Layout

ELABORATED DESIGN - sr7a5chrg736-1

Sources Netlist

R: SOP

Netlist

Leaf Cells

Properties

Select an object to see properties

Project Summary Schematic

5 Cells 4 I/O Ports 8 Ports

Tcl Console Messages Log Reports Design Runs

Name	Constraints	Status	WNS	TNS	WHS	THS	WBSS	TPWS	Total Power	Failed Routes	Methodology	RQA Score	QoR Suggestions	LUT	FF	BRAM	URAM	DSP
✓ synth_1	constr_1	synth_design Complete!												1	0	0	0	0
✓ Impl_1	constr_1	route_design Complete!	NA	NA	NA	NA		NA	0.021	0				1	0	0	0	0

5V & GND pin and ground kit.
the bread board
of each chip to
the bread board.
put pins of chips
respectively in the
you turn on the
of inputs according
to the truth table.

an function using

F, input A, input

);


B);

sl, c);

w3);

NAND gate and waveform

Teacher's Signature

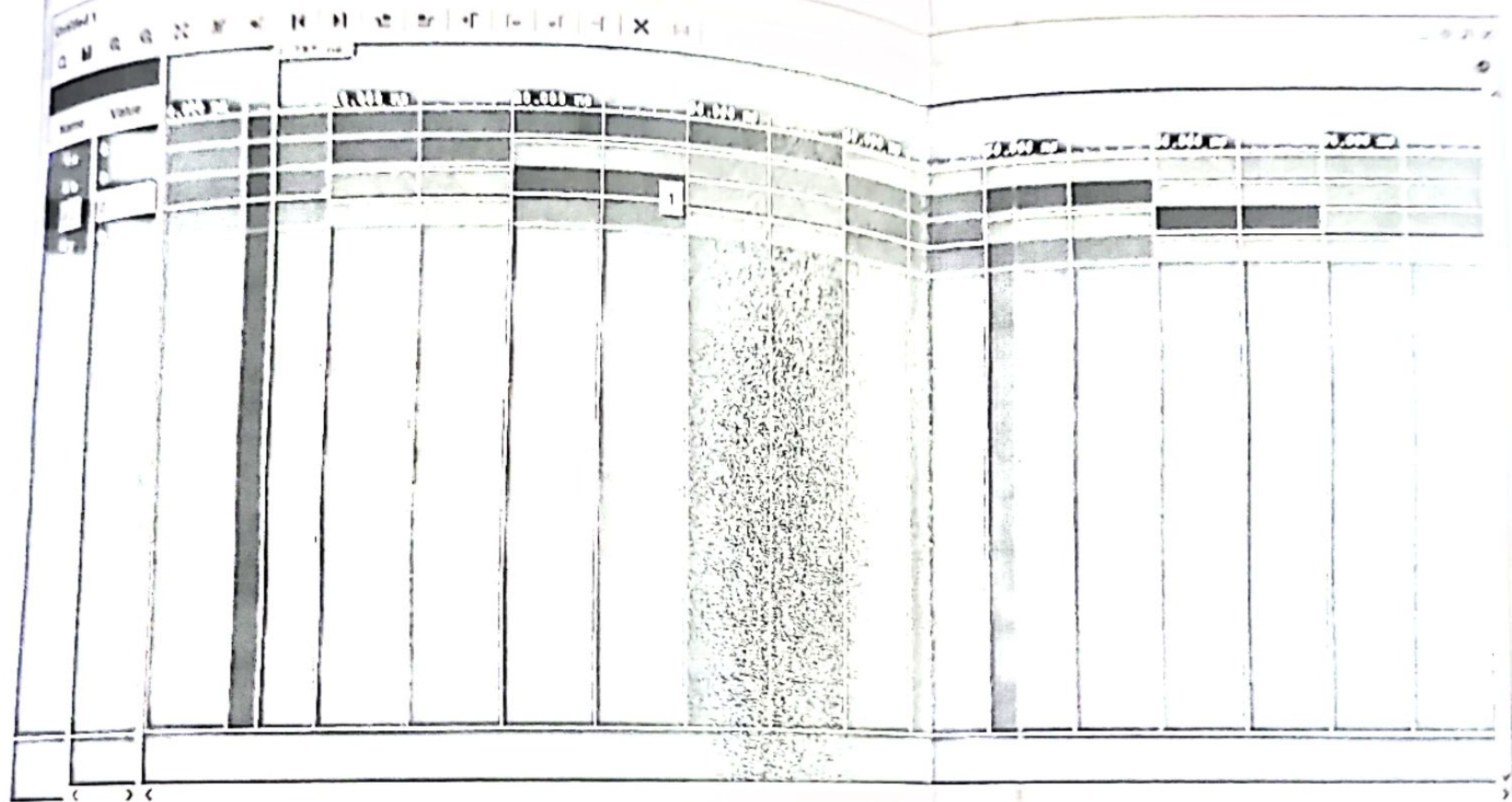

NAND gate and waveform

x) pin and
not kit.

a bread boar
of each chip
bread boar

pins of ch
spectively i
you turn on
inputs ac

a function

input A, i

;

);

, c);

3);

- (b) Connect power supply (+5V DC) pin and ground pin to the respective pins of the trainer kit.
- (c) Place the ICs properly on the bread board in the trainer kit.
- (d) Connect VCC and GND pins of each chip to the power supply and ground bus strips on the bread board.
- (e) Connect the input and output pins of chips to the input switches and output LEDs respectively in the trainer kit.
- (f) Check the connections before you turn on the power.
- (g) Apply various combinations of inputs according to truth tables and observe outputs of LEDs.

■ HDL Code

- SOP implementation of boolean function using $F(A,B,C) = \sum(1,3,6,7)$ using NAND gates

```

module SOP (output F, input A, input B, input C);
  wire w1, w2, w3;
  nand NAND1(w1, A, A);
  nand NAND2(w2, A, B);
  nand NAND3(w3, w1, C);
  nand NAND4(F, w2, w3);
endmodule

```


ELABORATED DESIGN - w7a50cpg235-1

Project Manager

- Settings
- Add Sources
- Language Templates
- IP Catalog

IP INTEGRATOR

- Create Block Design
- Open Block Design
- Generate Block Design

SIMULATION

- Run Simulation

RTL ANALYSIS

- Run Linter
- Open Elaborated Design
- Report Methodology
- Report DRC
- Report Noise
- Schematic
- Open Dataflow Design

SYNTHESIS

- Run Synthesis
- Open Synthesized Design
- Constraints Wizard

Sources Netlist

- NOR1
- NOR2
- NOR3
- NOR4
- Local Cells (7)
 - NOR1_J (RTL_OR)
 - NOR2_J (RTL_OR)
 - NOR3_J (RTL_OR)
 - NOR4_J (RTL_OR)

Net Properties

Name: F

Type: SIGNAL

Cell pin count: 1

General Properties Connectivity Aliases Cell Pins

Tcl Console Messages Log Reports Design Runs

Name Constraints Status

Name	Constraints	Status	WNS	TNS	WHS	THS	WDS	TPWS	Total Power	Failed Routes	Methodology	EQA Score	QoR Suggestions	LUT	FF	BRAM	URAM	DSP
✓ synth_1	constraints_1	synth_design Completed												1	0	0	0	0
▷ Impl_1	constraints_1	Not started																

Project Summary Schematic

5 Cells 4 I/O Ports 8 Nets

```


graph LR
    A --> NOR1_J[NOR1_J]
    C --> NOR1_J
    A --> NOR2_J[NOR2_J]
    C --> NOR2_J
    B --> NOR3_J[NOR3_J]
    NOR1_J --> NOR4_J[NOR4_J]
    NOR2_J --> NOR4_J
    NOR4_J --> NOR5_J[NOR5_J]
    NOR5_J --> F
  
```

an function using F

des. A, input B, input C);

olean functions usi
and hardware impl
products and pro
has been done suc

NOR gate and waveform

 

function using
input B, input C

can functions
and hardware
products and
at been done

NOR gate and Waveform

- POS implementation of boolean function using $F(A,B,C)$
 $= \prod(0,2,4,5)$ using NOR gates.

```
module POS (output F, input A, input B, input C);  
    wire w1, w2, w3;  
    nor NOR1 (w1, A, A);  
    nor NOR2 (w2, A, C);  
    nor NOR3 (w3, w1, B);  
    nor NOR4 (F, w2, w3);  
endmodule
```

■ CONCLUSION

Design and simulation of boolean functions using verilog HDL has been done successfully and hardware implementation of boolean functions in sum of products and product of sums using NAND and NOR gates has been done successfully.