

KIIT Deemed to be University
SPRING 2ND MID-SEMESTER EXAMINATION – 2017
DIGITAL ELECTRONICS (EC-2011)

Full Marks: 25

Duration: 1 hrs 30mins

- Answer any 5 Questions and Q1 is compulsory.
- The figures in the margin indicate full marks.
- Candidates are required to give their answers in their own words as far as practicable and all parts of a question should be answered at one place only.

- 1) a What are the drawbacks of 4-bit binary parallel adder circuit? [1X5]
- b Define 'error detecting codes' and 'error correcting codes'.
- c Implement OR gate in a 2X1 MUX.
- d Draw a buffer gate using XNOR gate.
- e Draw a D-Flip-Flop using JK- Flip-Flop

- 2) Implement the following function using 8X1 MUX [5]


$$F = \bar{A}B + \bar{C}D + \bar{A}C$$

- 3) Obtain the minimized expression using K-map for the function [5]

$f = \sum m(0,1,2,3,8,9,10,11,14,15) + \sum d(6,7)$ and implement the minimized expression using NAND gates only

 - 4) a Draw the logic diagram of full subtractor using minimum number of NAND gates. [3]

- b Identify the Boolean function **F(A,B)** implemented with MUX [2]



- 5) a Draw a 4-bit PISO Shift Register using D- Flip-Flop [3]

- b What is Demultiplexer? How does it differ from a Decoder circuit [2]

- 6) a Implement a Full-Adder in an active low decoder and using 2-input gates only. [3]

- b What is BCD-SSD decoder? Also draw its truth table. [2]

