

ETC



2009 Adm. Batch Onwards  
IV-B-Tech(Regular& Back)  
DEC EC-402  
[ E&EE, E&TC, E&I, EE, IT, CSE ]

**FOURTH SEMESTER EXAMINATION-2012**  
**DIGITAL ELECTRONICS CIRCUITS**  
**EC-402**

**Full Marks: 60**

**Time: 3 Hours**

*Answer any six questions including question No.1 which is compulsory.*


*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable and  
All parts of a question should be answered at one place only.*


- Q1. a) What is *don't care term* and how can such term arise in practice? [1x10]  
b) Differentiate synchronous and asynchronous input terminals of FFs, explain with the help of J-K FF.  
c) 'XOR and XNOR gates can be used as a buffer as well as an inverter', Justify.  
d) What is the difference between active LOW and active HIGH terminals?  
e) Define (i)Self-complementing code,(ii)Sequential codes. Give examples of both.  
f) Define Noise Margin and Fan-out?  
g) Perform following arithmetic : (i) BCD addition (749+858),  
(ii) (-14) - (-6) using 2's complement method.  
h) Calculate the modulus of the counter which counts in **prime numbers** (2, 3, 5...N, 2, 3....) where N < 50.  
i) What is the difference between SRAM and DRAM?  
j) An 8-bit successive approximation type ADC has a resolution of 15mV.What will its digital output be for an analog input of 2.65V?
- Q2. a) Design a synchronous sequential circuit which produces an output Z=1, whenever the following input sequence '10110' occurs. (Assume overlapping is allowed and use Mealy Model) [6]  
b) Draw the logic diagram of a 4-bit Bi-directional shift register and explain in brief. [4]
- Q3. a) Design a synchronous counter that goes through states 0,2,3,5,6,7,0,2,3..... using J-K FFs. [4]  
b) Using 2-4 decoders (having enable input) design **3-8 decoder with enable input** so that the new 3-8 decoder can be used for further expansion. [4]  
c) Draw the circuit for 2-input NOR gate using CMOS logic. [2]
- Q4. a) Implement 3-bit combined even and odd parity generator using a multiplexer having two select lines and XOR gate. (Hint: Use XOR gate as a buffer and as an inverter) [4]  
b) With the help of a neat diagram explain the working of a two-input totem-pole TTL NAND gate and also mention some advantages of this configuration. [4]  
c) What is the difference between PLA & PAL explain with suitable examples? [2]
- Q5. a) With the help of a neat diagram explain the working of Counter type A/D converter circuit and also discuss the drawbacks of this converter in brief. [4]  
b) Obtain the minimized expression for the following 4-variable Boolean expression using K-map method and implement the minimized expression using NAND gates only. [4]

$$F(P,Q,R,S) = \Pi M (0,1,4,7,10,11,13,14).d(2,7,8,13)$$

 
- c) Find out the resulting output  $Q(t)$  of the FF for next 6 clock pulses assuming initial condition ( $Q=0$  and  $\bar{Q}=1$ ) for the following circuit. [2]



 - Q6. a) Design a 4:2 priority encoder such that input having least decimal subscript should have highest priority (**Order of priority:  $D_0 > D_1 > D_2 > D_3$ , where all  $D_i$ 's are inputs to the encoder**) [4]  
 b) Encode 4-bit data word '1000' into a 7-bit even-parity Hamming code. If we transmitted a 7-bit even parity Hamming code through a noisy channel and at the receiver we obtained '1110110'. Decode the correct 4-bit data word. (Assume that at most a single bit error may occur in the code word during transmission) [4]  
 c) Identify the Boolean function  $F(A,B)$  implemented with MUX, [2]



 - Q7. a) Draw the circuit diagram of (i) MOD-6 Johnson counter (ii) MOD-4 Ring counter and compare N-bit Ring & Johnson counter from modulus and decoding circuit point of view. [4]  
 b) Simplify the given logic circuit and implement the simplified circuit using only NOR gates. [4]



- c) 'A decoder circuit having **enable input line** can be used as a demultiplexer circuit', Justify this statement with proper circuit diagram. [2]

- Q8. a) What is the difference between Astable multivibrator and Monostable multivibrator? Design an Astable Multivibrator using 555 timer to generate a square wave of 2KHz frequency with 60% duty cycle. [4]  
 b) Design J-K Flip-Flop using 2:1 MUX and a T Flip-Flop. [4]  
 c) A certain memory has a capacity of 16K x 32. [2]  
 (i) How many data I/P and O/P lines does it have?  
 (ii) How many address lines does it have?