



## AUTUMN END SEMESTER EXAMINATION-2015

1<sup>st</sup> Semester B.Tech & B.Tech Dual Degree

### BASIC ELECTRICAL ENGINEERING (EE-1003)

(Regular-2015 Admitted Batch)

Full Marks: 60

Time: 3 Hours

*Answer any SIX questions including Question No.1 which is compulsory.*


*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable and all parts of a question should be answered at one place only.*

1. a) Draw the sketch of a single phase autotransformer. [2 × 10]
- b) A current of  $40 \cos(314t - \pi/8)$  A is drawn from a supply voltage of  $500 \cos(314t + \pi/8)$  V. Calculate the power supplied from the source.
- c) In a series RC circuit, the voltage across the capacitor and resistor as obtained by a moving iron type AC voltmeter are 60 V and 80 V respectively. How much will the voltmeter read when it is connected across the combination?
- d) A 250 kVA, 11000 V/400 V, 50 Hz single phase transformer has 80 turns on the low voltage side. Calculate the number of turns of the high voltage side.
- e) State and explain Faraday's law of electromagnetic induction.
- f) Current in a circuit with impedance Z ohm is 18 A and leads the voltage across it by  $36^\circ$ . The voltage being 20 V. Draw the waveforms for the voltage and current in one plot and corresponding phasors in another plot.
- g) What is hysteresis loss and mention how it can be reduced for a transformer?

(1)

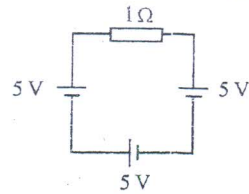- h) How much current will flow through the  $1\ \Omega$  resistor in the circuit?



- i) Draw a sketch of dynamometer type wattmeter and label different components.
- j) Define luminous flux and luminous intensity and mention their units.

2. a) using Thevenin equivalent approach obtain the voltage across the  $10\ \Omega$  resistor. [5]


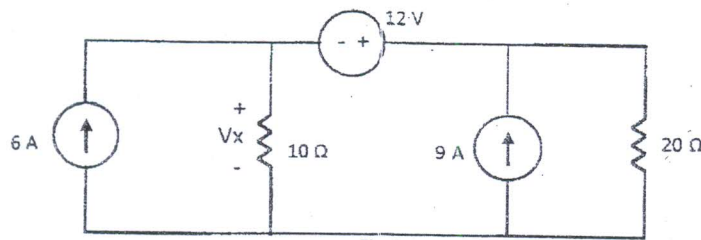


Fig.1

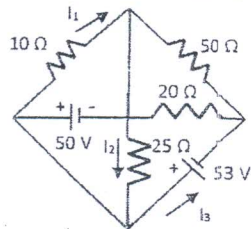- b) For the circuit shown find  $I_1$ ,  $I_2$  and  $I_3$ . [3]



3. a) Find the current phasor through  $10\ \Omega$  resistor. [4]

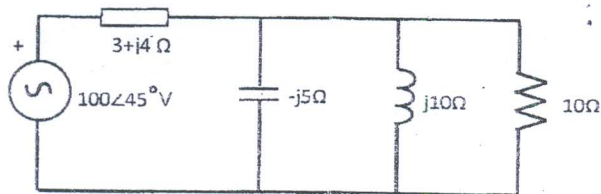



Fig.3

(2)


- b) The voltage drops across two components when connected in series across an AC supply are: [4]

$v_1 = 180\sin 314t$  and  $v_2 = 120\sin(314t + \pi/3)$  volts and the current through the combination is  $i = 10\sin 314t$  amperes. Calculate the RMS value of the supply voltage and the power consumed by the combination.

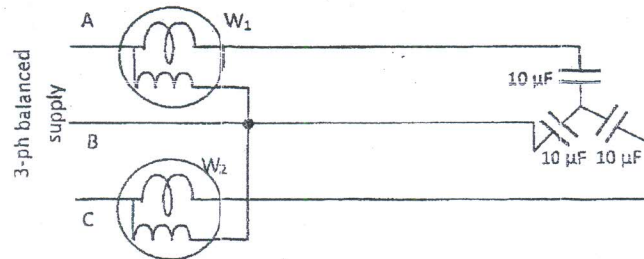4. a) Find the watt meter readings  $W_1$  and  $W_2$  for the circuit shown. Considering phase A voltage as reference and the sequence is A-B-C. Line to line voltage is 400 V and supply frequency is 50 Hz. [5]



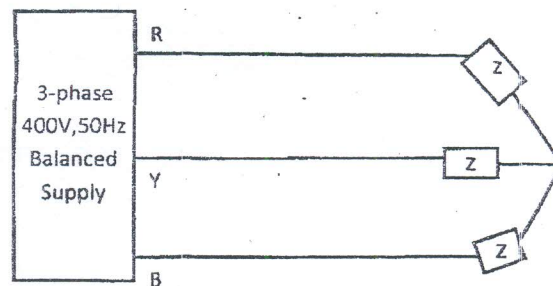- b) For the 3-phase balanced system calculate the power consumed in each impedance ( $Z$ ) and power supplied by the source. Each  $Z = 10\angle 30^\circ \Omega$ . [3]



5. a) A single phase transformer has 400 primary and 1000 secondary turns. The next cross sectional area of the core is  $60 \text{ cm}^2$ . If the primary is connected to 500 V, 50 Hz source, calculate the peak value of flux density in the core. [4]

(3)

b) Write how a rotating field is created in a three phase induction motor. [4]

6. a) An iron ring of mean circumference of 140 cm and cross section  $12 \text{ cm}^2$  is wound with 500 turns of wire. With the exciting current of 2A, the flux is found to be 1.2 mWb. [4]