

NETWORK THEOREMS

4

OBJECTIVES

After completing this Chapter, you will be able to:

- State and apply 'superposition theorem' to solve a circuit containing more than one source.
- State and apply 'Thevenin's theorem' to solve a circuit.
- State the benefits of 'Thevenin's theorem'.
- State and apply 'Norton's theorem' to solve a circuit.
- State, prove and apply 'maximum power transfer theorem'.
- Find a single equivalent voltage source for a number of voltage sources connected in parallel using 'Millman's theorem'.
- State and prove 'reciprocity theorem'.
- State and prove 'Tellegen's theorem'.
- State the importance of 'Tellegen's theorem'.

4.1 INTRODUCTION

Simple circuits can be solved by using Ohm's law, Kirchhoff's laws, voltage divider, current divider, series and parallel combination of sources and resistors, etc. Special techniques, known as *network theorems* and *network reduction methods*, have been developed which drastically reduce the labour of solving a more complicated network. The network theorems provide simple conclusions and good insight into the problems. Some of these have universal applications, whereas some are limited to the networks containing linear* elements only.

4.2 SUPERPOSITION THEOREM

This theorem states that *the response in a linear circuit at any point due to multiple sources can be calculated by summing the effects of each source considered separately, all other sources being made inoperative (or turned OFF)*. The theorem is applicable only to a linear network (containing independent and/or dependent sources).

How to Make a Source Inoperative

When a *voltage source* is made inoperative or turned OFF, no voltage drop exists across its terminals but *a current can still* flow through it. Hence, it acts like a *short-circuit* (Fig. 4.1a).

* A linear element obeys Ohm's law, e.g., resistance, inductance, etc. Semiconductor diodes and transistors are not linear elements.

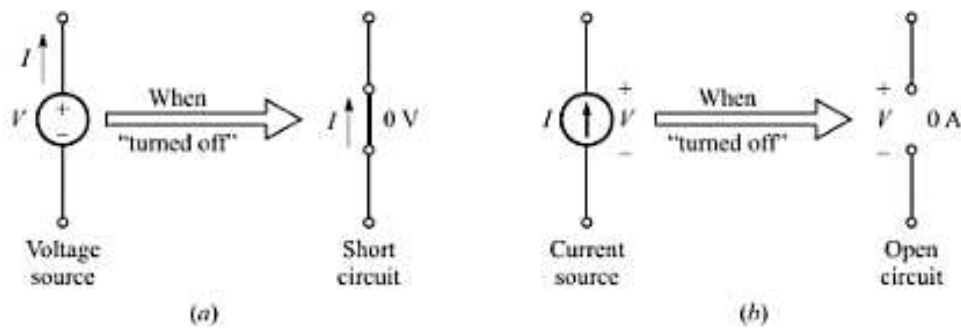


Fig. 4.1 "Turning off" the sources.

Similarly, when a *current source* is made inoperative or turned off, no current flows through it but a voltage can appear across its terminals. Hence, it acts like an *open-circuit* (Fig. 4.1b).

By making a source *inoperative* or turned OFF means that the voltage source is replaced by a short-circuit and the current source is replaced by an open-circuit.

EXAMPLE 4.1

Using superposition theorem, find the current I in the circuit shown in Fig. 4.2a.

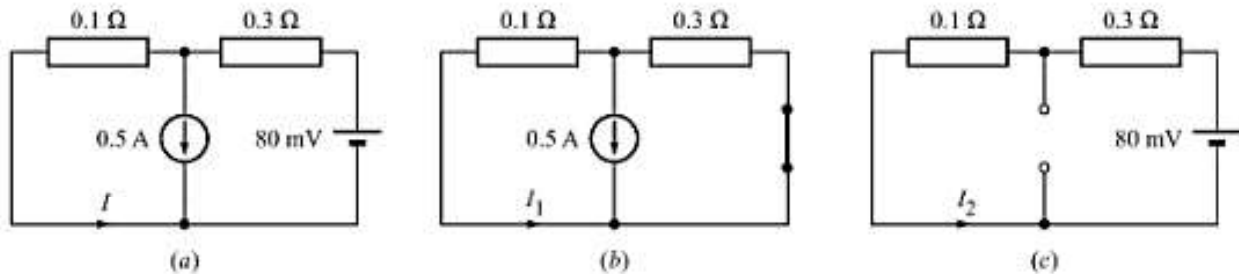


Fig. 4.2 Principle of superposition illustrated.

Solution Let us first consider the response I_1 due to the 0.5-A current source, and turn OFF the 80-mV voltage source by shorting it (Fig.4.2b). Applying current divider, we get

$$I_1 = -0.5 \times \frac{0.3}{0.1 + 0.3} = -0.375\text{ A}$$

Next, consider the voltage source, and turn OFF the current source by opening it (Fig.4.2c). Ohm's law gives

$$I_2 = \frac{80 \times 10^{-3}}{0.1 + 0.3} = 0.2\text{ A}$$


By the principle of superposition, the total current is given as

$$I = I_1 + I_2 = -0.375 + 0.2 = -0.175\text{ A}$$

Note that in redrawing the circuit for each source, we are always careful to mark the response current in the original direction and also assign a suitable subscript to indicate that we are not working with the original variables. This prevents the possibility of committing errors when we add the individual currents.


EXAMPLE 4.2

Use superposition theorem to find current I_x in the network given in Fig. 4.3.

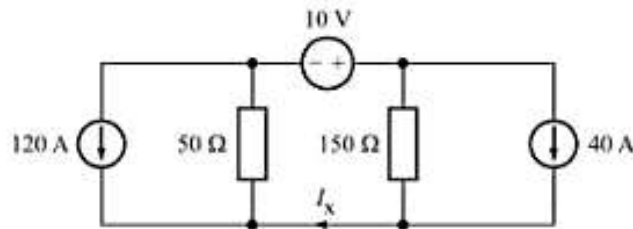**Fig. 4.3**

Solution Consider first the voltage source alone. Both current sources are made inoperative by open-circuiting them (Fig. 4.4a). Current I_1 is

$$I_1 = \frac{10}{50 + 150} = 0.05 \text{ A}$$

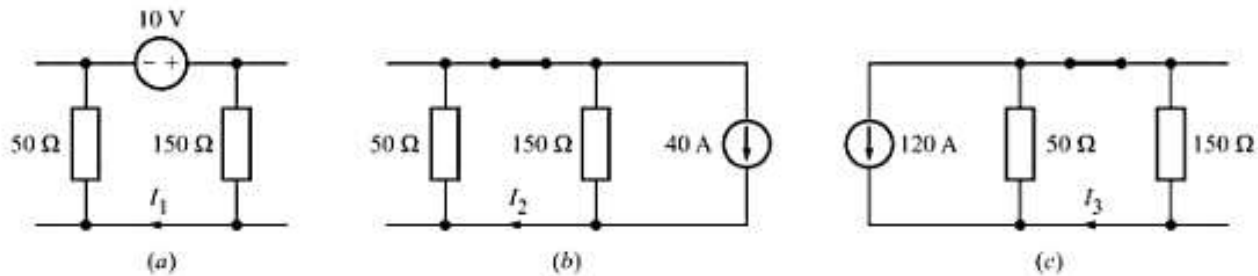**Fig. 4.4**

Next consider the 40-A current source alone (Fig. 4.4b). Applying current divider, the current I_2 is given as

$$I_2 = 40 \times \frac{150}{50 + 150} = 30 \text{ A}$$

Lastly consider the 120-A current source alone (Fig. 4.4c). The current I_3 is

$$I_3 = -120 \times \frac{50}{50 + 150} = -30 \text{ A}$$

Applying the principle of superposition, we get

$$I_x = I_1 + I_2 + I_3 = 0.05 + 30 - 30 = 0.05 \text{ A}$$

EXAMPLE 4.3

Consider our benchmark example (Fig. 3.24a) discussed in Example 3.11, wherein we had calculated the voltage across 3-Ω resistor as 2.5 V, by using source transformation. The same circuit is shown in Fig. 4.5a. We again find voltage v across 3-Ω resistor by applying the principle of superposition.

Solution Consider first the 4-A current source, while turning OFF the remaining two sources. The turned-OFF 5-A current source is replaced by an open-circuit and the turned-OFF 6-V voltage source is replaced by a short-circuit, as shown in Fig. 4.5b. We find that the current of 4 A divides into two parallel paths. Therefore, using current divider, we get

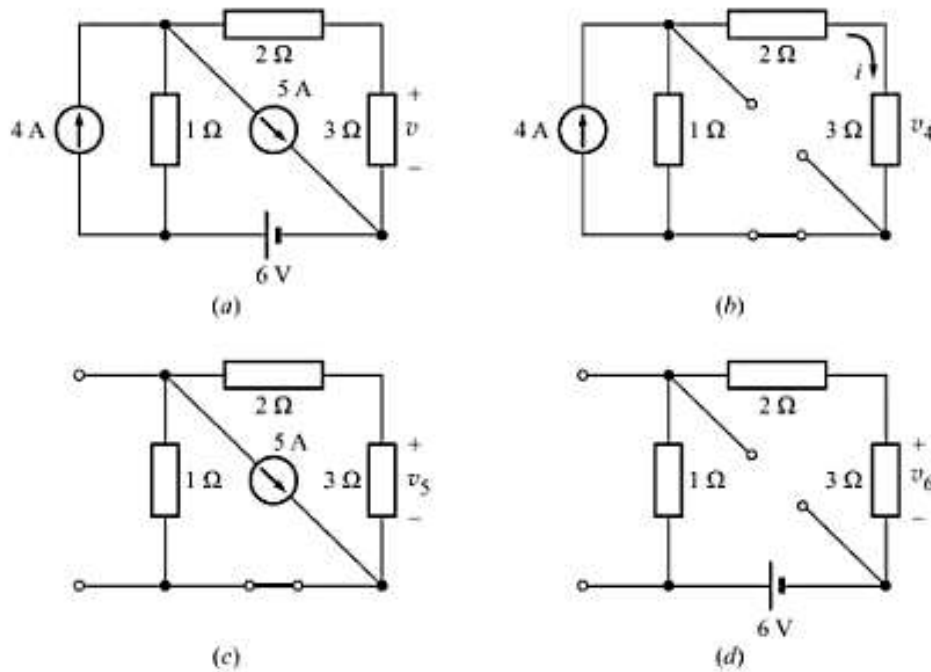


Fig. 4.5

$$i = 4 \times \frac{1}{1 + (2 + 3)} = \frac{2}{3} \text{ A}$$

Thus, voltage v_4 across 3- Ω resistor due to 4-A current source is

$$V_4 = i \times R = (2/3 \text{ A}) \times (3\Omega) = 2.0\text{V}$$

The polarity of this voltage is the same as the original polarity markings for v . Hence, this contribution to the final summation will appear with a + sign.

Next consider **5-A current source**, with 4-A and 6-V sources turned OFF (Fig. 4.5c). From the perspective of the 5-A source, the 2- Ω and 3- Ω resistances are in series and together in parallel with the 1- Ω resistor. Using current-divider, the voltage v_5 across 3- Ω resistor due to 5-A current source is given as

$$v_5 = \left[-5 \times \frac{1}{1 + (2 + 3)} \text{ A} \right] \times (3\Omega) = -2.5 \text{ V}$$

Note that the actual polarity of this voltage v_5 is opposite to the polarity marked on v . Hence, the minus sign.

We now consider **6-V voltage source**, with 4-A and 5-A sources turned OFF (Fig. 4.5d). The three resistances are connected in series. The resulting voltage v_6 is calculated by voltage divider, as

$$v_6 = 6 \times \frac{3}{1 + 2 + 3} = 3.0 \text{ V}$$

The polarity of this voltage is same as that of the original voltage v . Hence, the sign of v_6 will be positive in the final summation.

Using principle of superposition, we now obtain the total voltage v across 3- Ω resistor, as

$$v = +v_4 + v_5 + v_6 = +2.0 - 2.5 + 3.0 = +2.5 \text{ V}$$

EXAMPLE 4.4

For the circuit shown in Fig. 4.6a, find the value of I_s to reduce the voltage across 4- Ω resistor to zero.

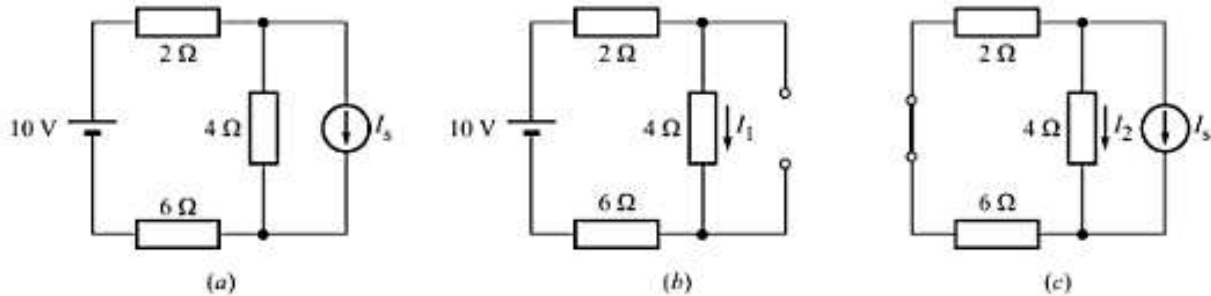


Fig. 4.6

Solution To solve this problem, we apply the principle of superposition. The current I_1 (from top to bottom) in 4- Ω resistor due to 10-V source in Fig. 4.6b is

$$I_1 = \frac{10}{2 + 4 + 6} = \frac{5}{6} \text{ A}$$

The current I_2 (from top to bottom) in 4- Ω resistor due to current source I_s in Fig. 4.6c is

$$I_2 = -I_s \times \frac{2 + 6}{2 + 6 + 4} = -\frac{2}{3} I_s$$

The voltage across 4- Ω resistor can be zero, only if the current through this resistor is zero. That is,

$$I_1 + I_2 = 0 \quad \text{or} \quad \frac{5}{6} + \left(-\frac{2}{3} I_s\right) = 0 \Rightarrow I_s = \frac{5 \times 3}{6 \times 2} = 1.25 \text{ A}$$

4.3 THEVENIN'S THEOREM

This theorem was first proposed by a French telegraph engineer M.L. Thevenin in 1883. Often, we need to find the response (*current, voltage or power*) in a single load resistance in a network. Thevenin's theorem enables us to do this without solving the entire network. It is specially very helpful and time-saving when we wish to find the response for different values of the load resistance.

Thevenin's Theorem states that *it is possible to simplify any linear circuit containing independent and dependent voltage and current sources, no matter how complex, to an equivalent circuit with just a single voltage source and a series resistance, between any two points of the circuit.*

Procedure

The procedure to apply Thevenin's theorem to a network will be explained in steps, by taking an example. Consider the circuit shown in Fig. 4.7a. Suppose that we are interested to find the current in resistor R_2 . We proceed as follows.

1. Designate the resistor R_2 as "load" (Fig. 4.7b).
2. Pull out the load resistor and enclose the remaining network within a dotted box (Fig. 4.7c).
3. Temporarily remove the load resistor R_2 , leaving the terminals A and B open (Fig. 4.7d).