

# Multiplexer

Lecture by  
Ganaraj P S


School of Electronics Engineering

# Outline


- $2 \times 1$  Multiplexer
- $4 \times 1$  Multiplexer
- $8 \times 1$  Multiplexer
- Higher-order Multiplexer design
- Boolean function realization using Multiplexers

# What is a Multiplexer?



General diagram

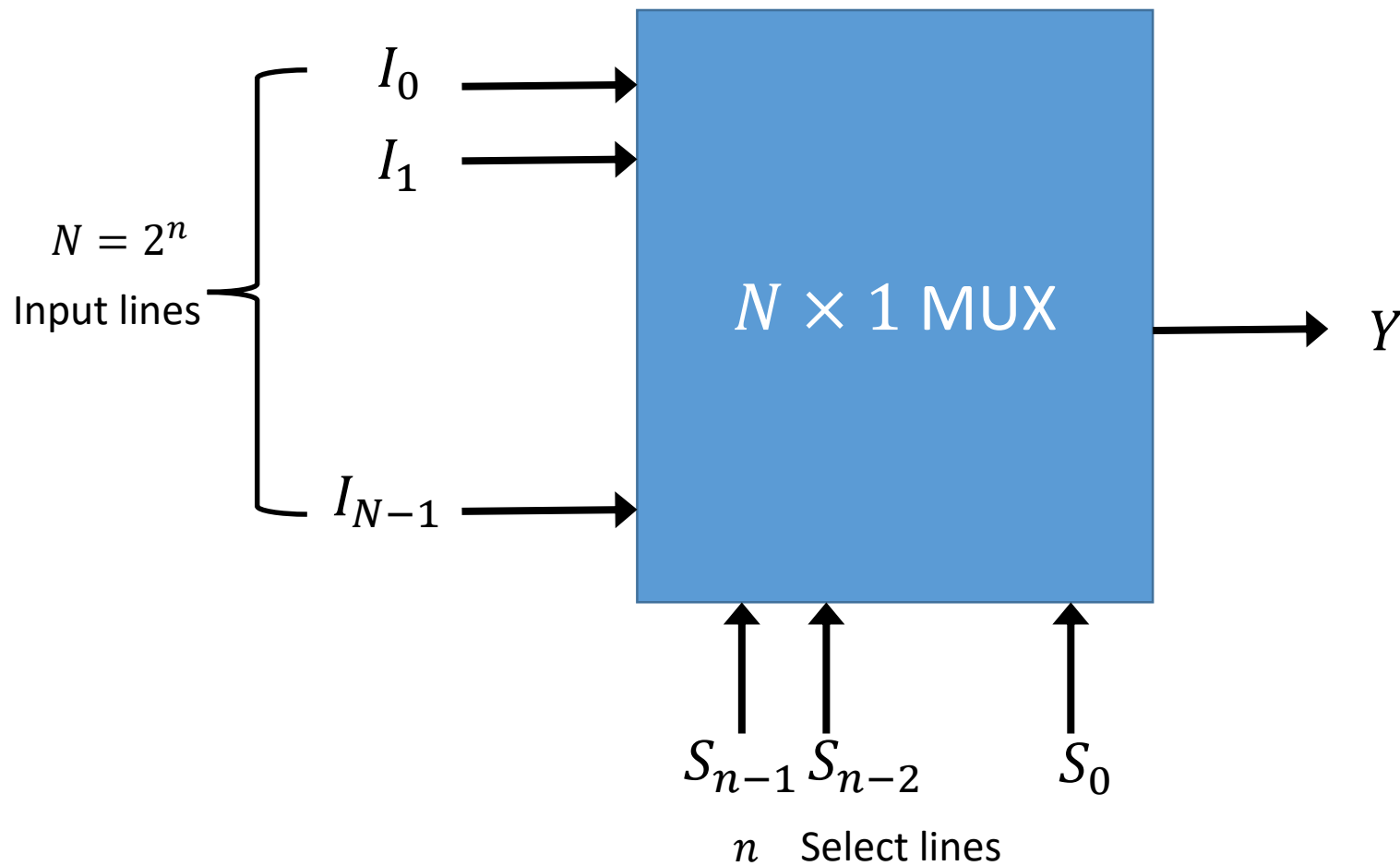

# $2 \times 1$ MUX

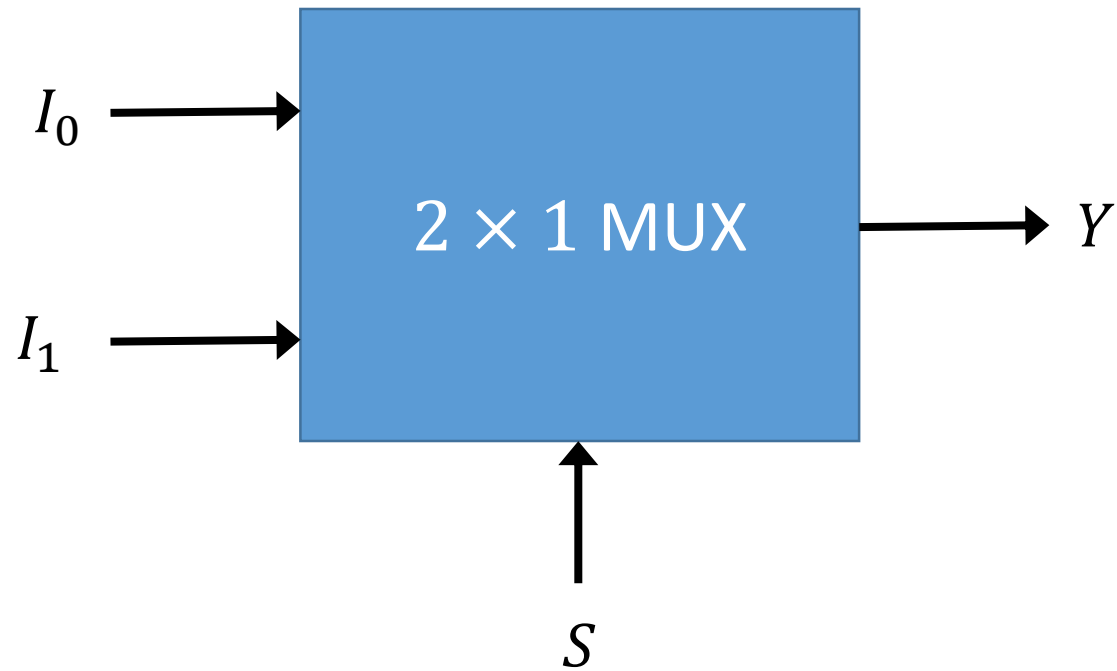

# Working of $2 \times 1$ MUX

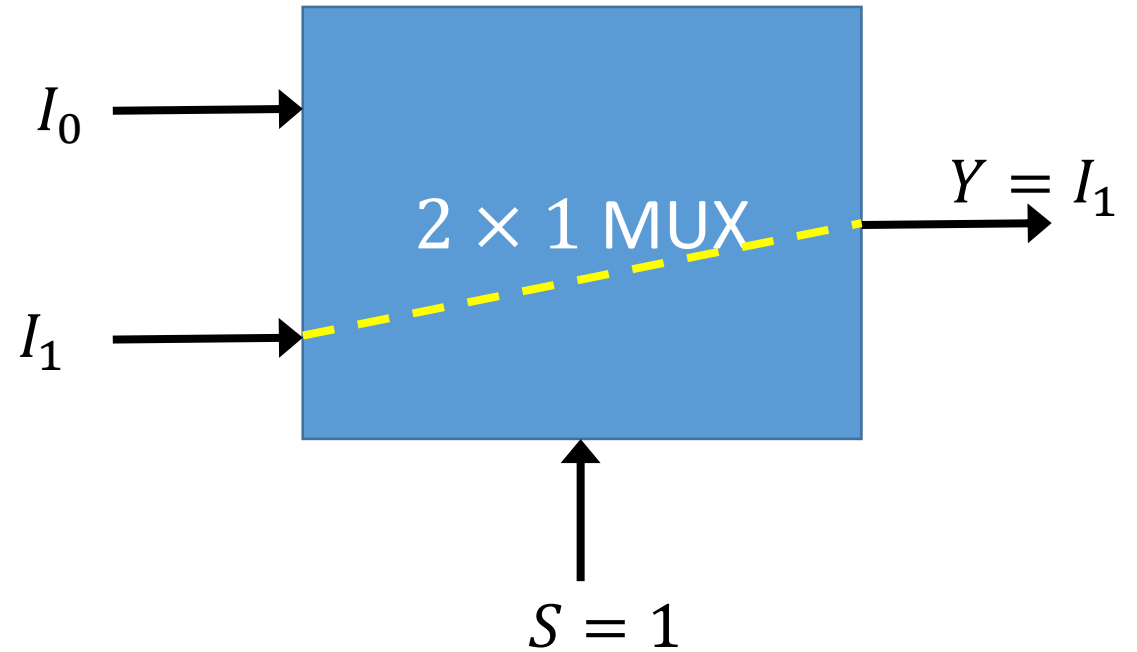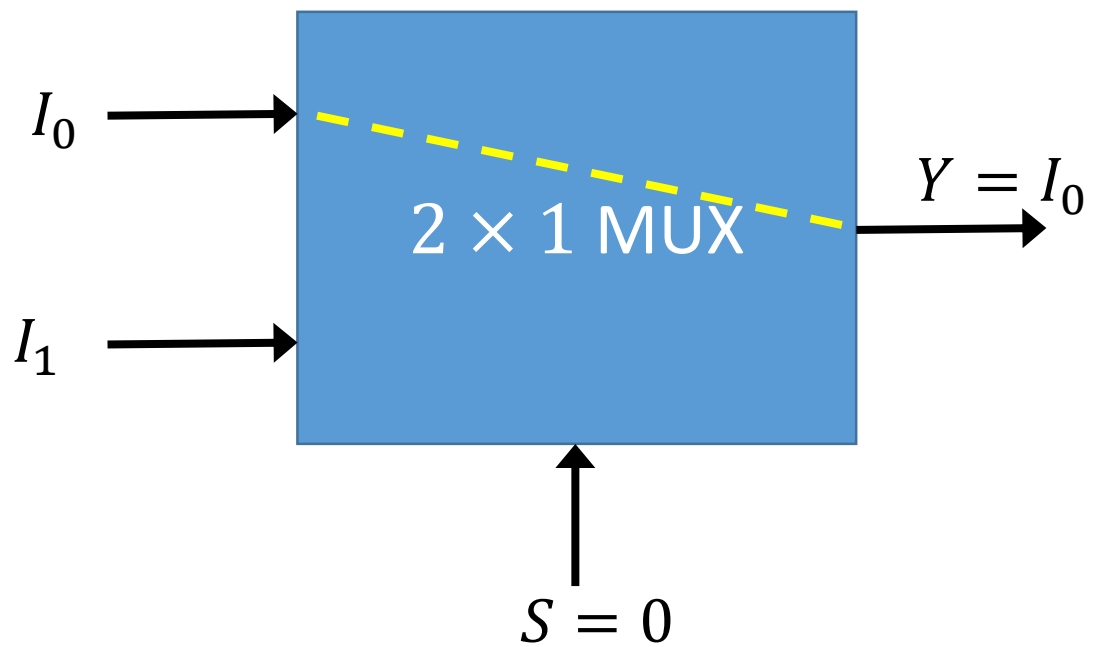

# Logic Circuit of $2 \times 1$ MUX


Truth table

Select line, $S$	Output, $Y$
0	$I_0$
1	$I_1$



Logic expression

$$Y = I_0\bar{S} + I_1S$$

Circuit based on AND-OR-Inverter logic

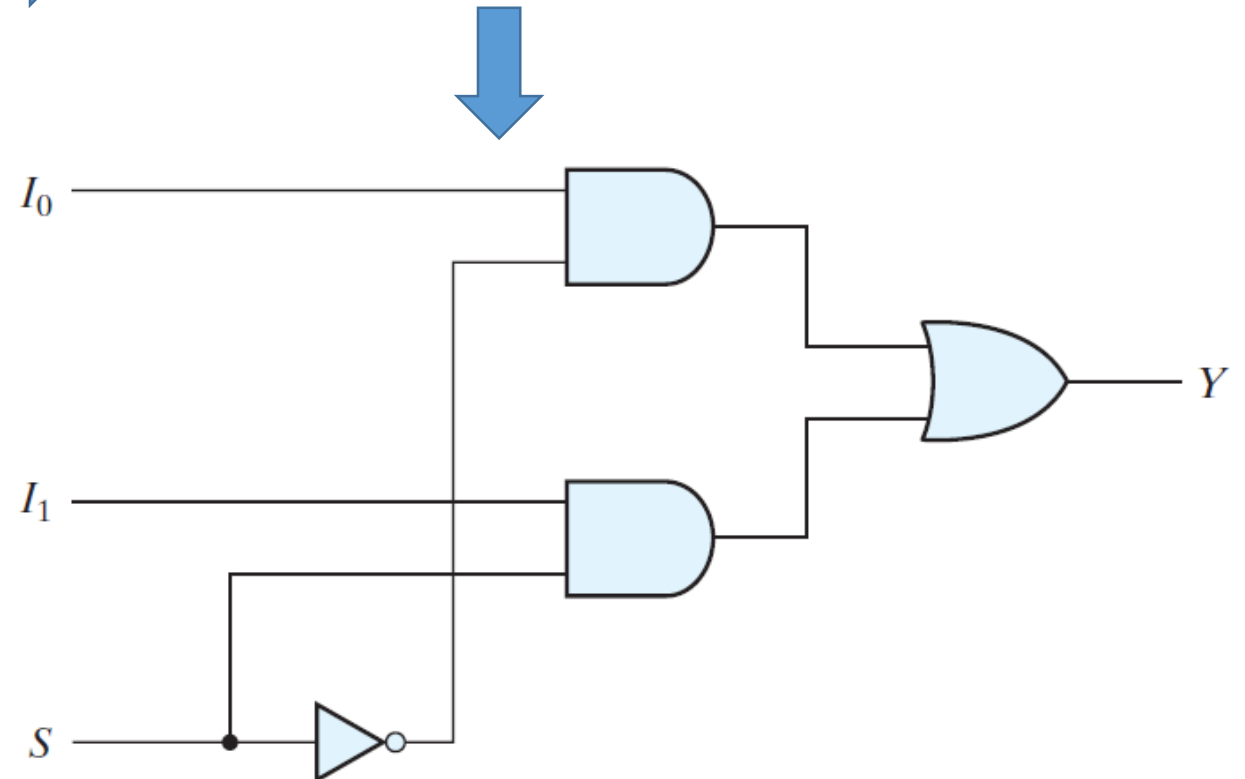


# Analyzing Circuit Operation

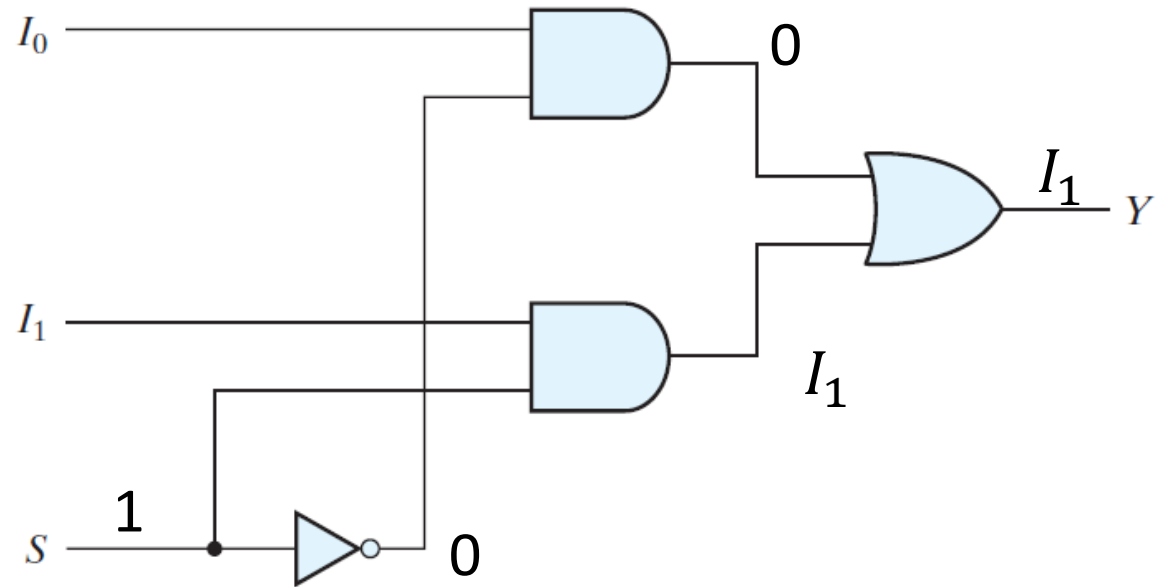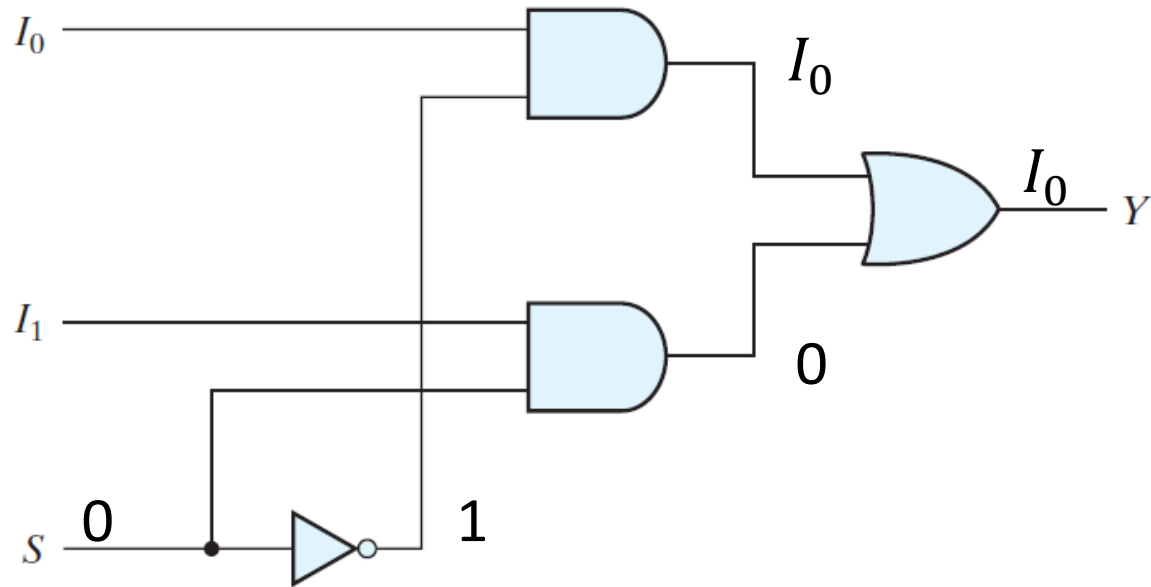
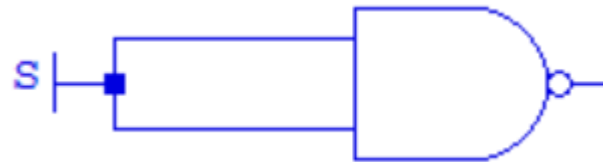
# Logic Circuit of $2 \times 1$ MUX

- NAND based circuit
- $Y = I_0 \bar{S} + I_1 S$
- $\bar{Y} = \overline{I_0 \bar{S} + I_1 S}$
- $\bar{Y} = \overline{I_0 \bar{S}} \overline{I_1 S}$
- $\bar{\bar{Y}} = Y = \overline{\overline{I_0 \bar{S}} \overline{I_1 S}}$





# Logic Circuit of $2 \times 1$ MUX


- NAND based circuit

- $Y = I_0 \bar{S} + I_1 S$

- $\bar{Y} = \overline{I_0 \bar{S} + I_1 S}$


- $\bar{Y} = \overline{I_0 \bar{S}} \overline{I_1 S}$

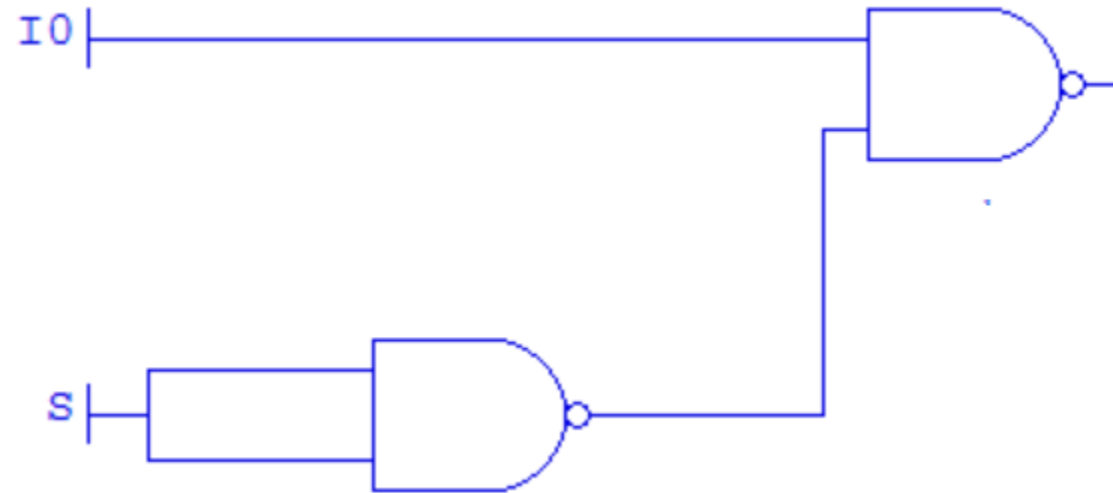- $\bar{\bar{Y}} = Y = \overline{\overline{I_0 \bar{S}} \overline{I_1 S}}$


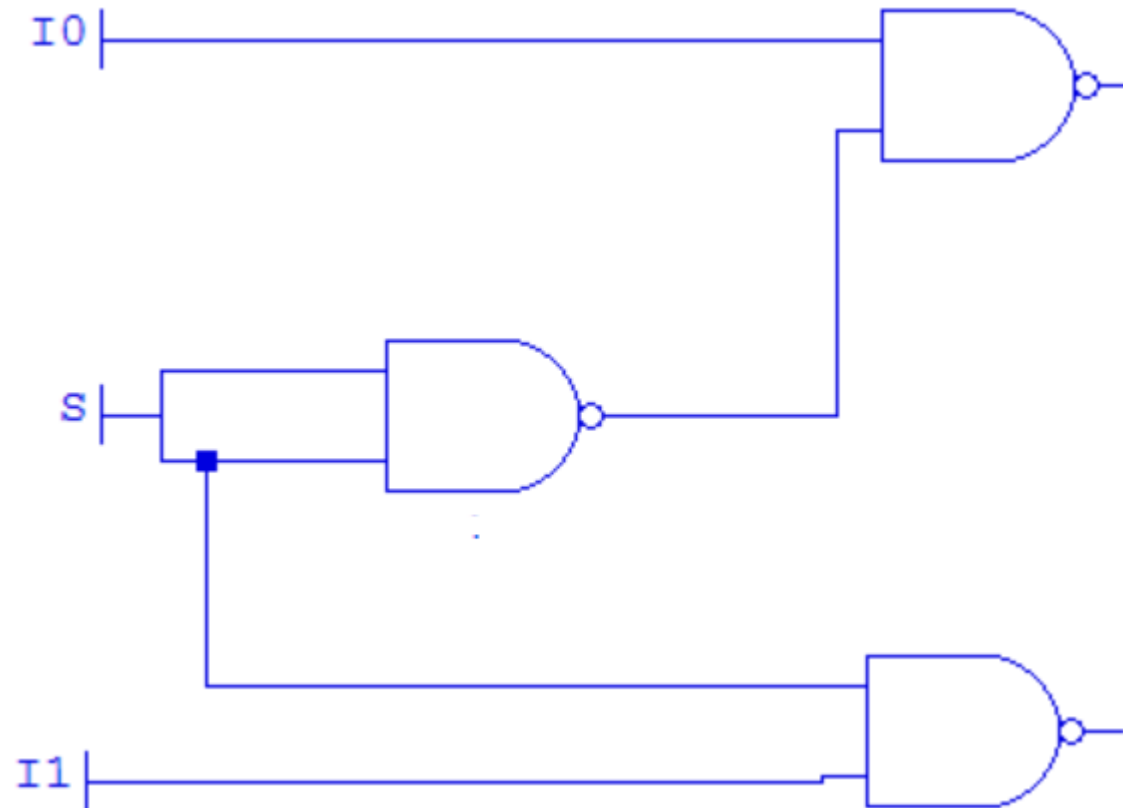
# Logic Circuit of $2 \times 1$ MUX

- NAND based circuit
- $Y = I_0 \bar{S} + I_1 S$
- $\bar{Y} = \overline{I_0 \bar{S} + I_1 S}$
- $\bar{Y} = \overline{I_0 \bar{S}} \overline{I_1 S}$
- $\bar{\bar{Y}} = Y = \overline{\overline{I_0 \bar{S}} \overline{I_1 S}}$



# Logic Circuit of $2 \times 1$ MUX


- NAND based circuit

- $Y = I_0 \bar{S} + I_1 S$


- $\bar{Y} = \overline{I_0 \bar{S} + I_1 S}$

- $\bar{Y} = \overline{I_0 \bar{S}} \overline{I_1 S}$

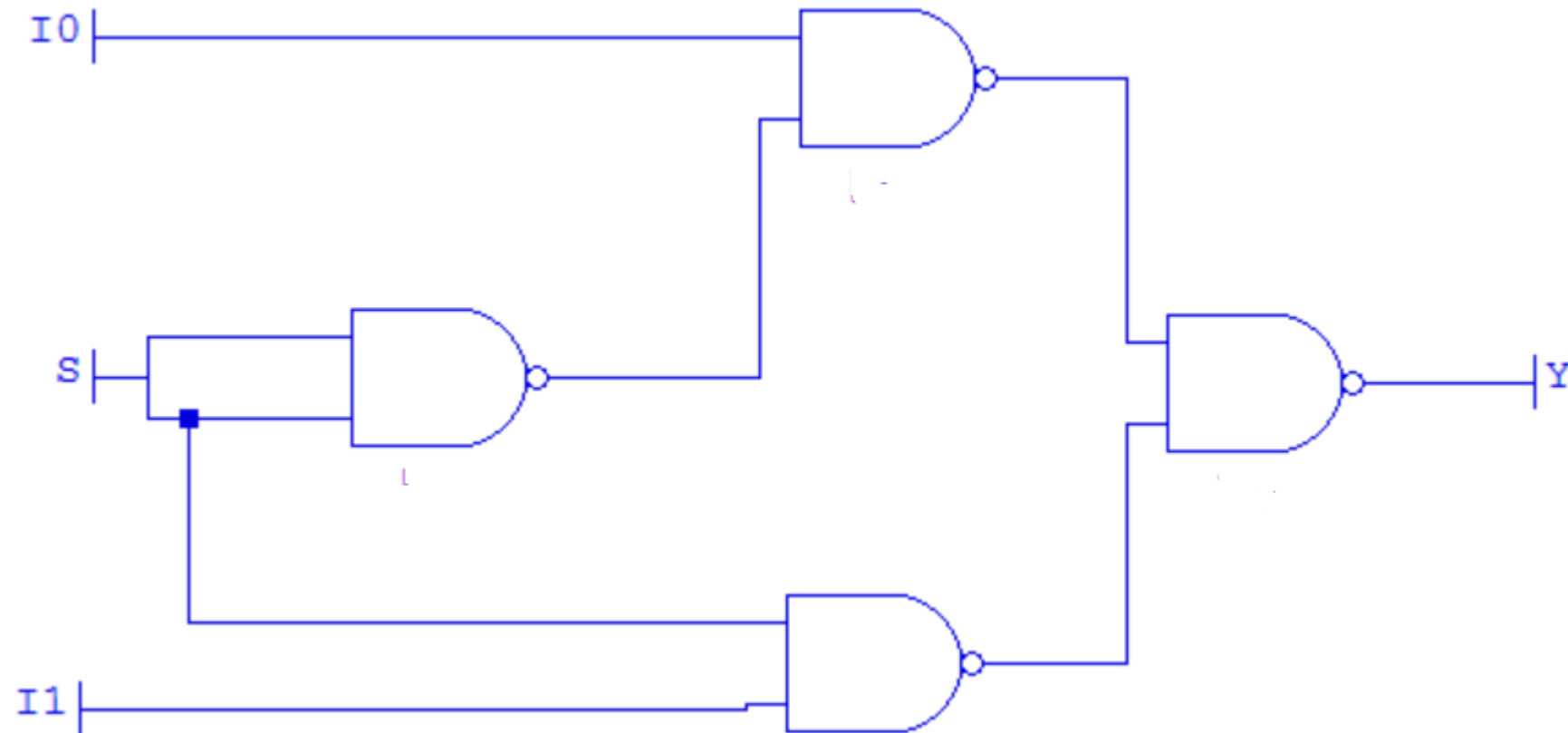- $\bar{\bar{Y}} = Y = \overline{\overline{I_0 \bar{S}} \overline{I_1 S}}$



# 4 × 1 MUX

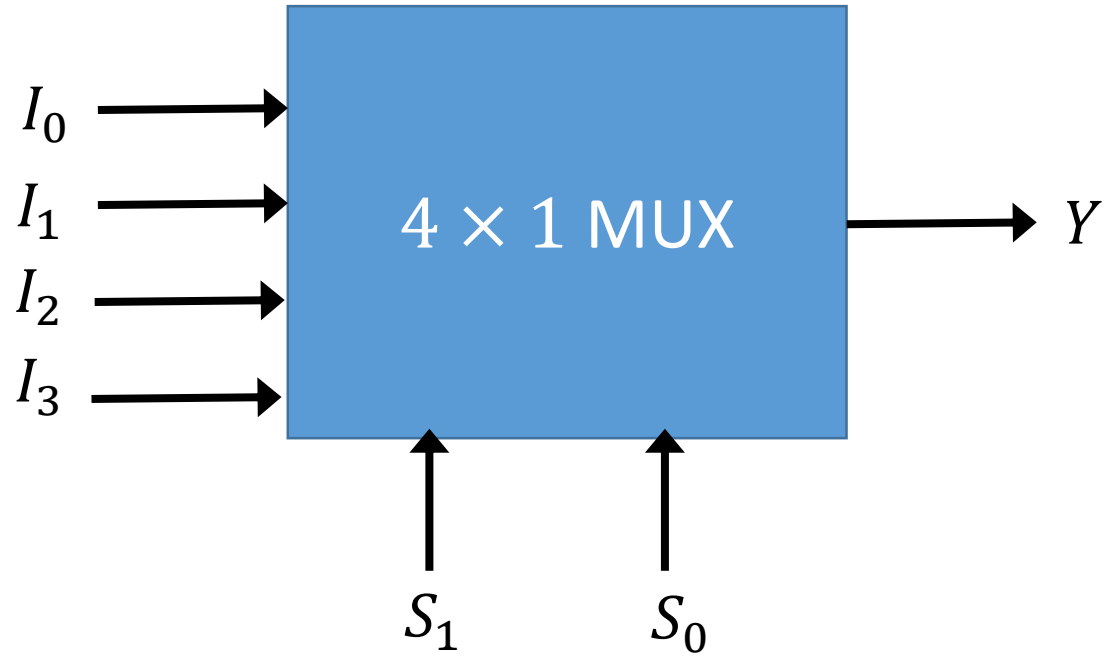


$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$



$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$

# 8 × 1 MUX

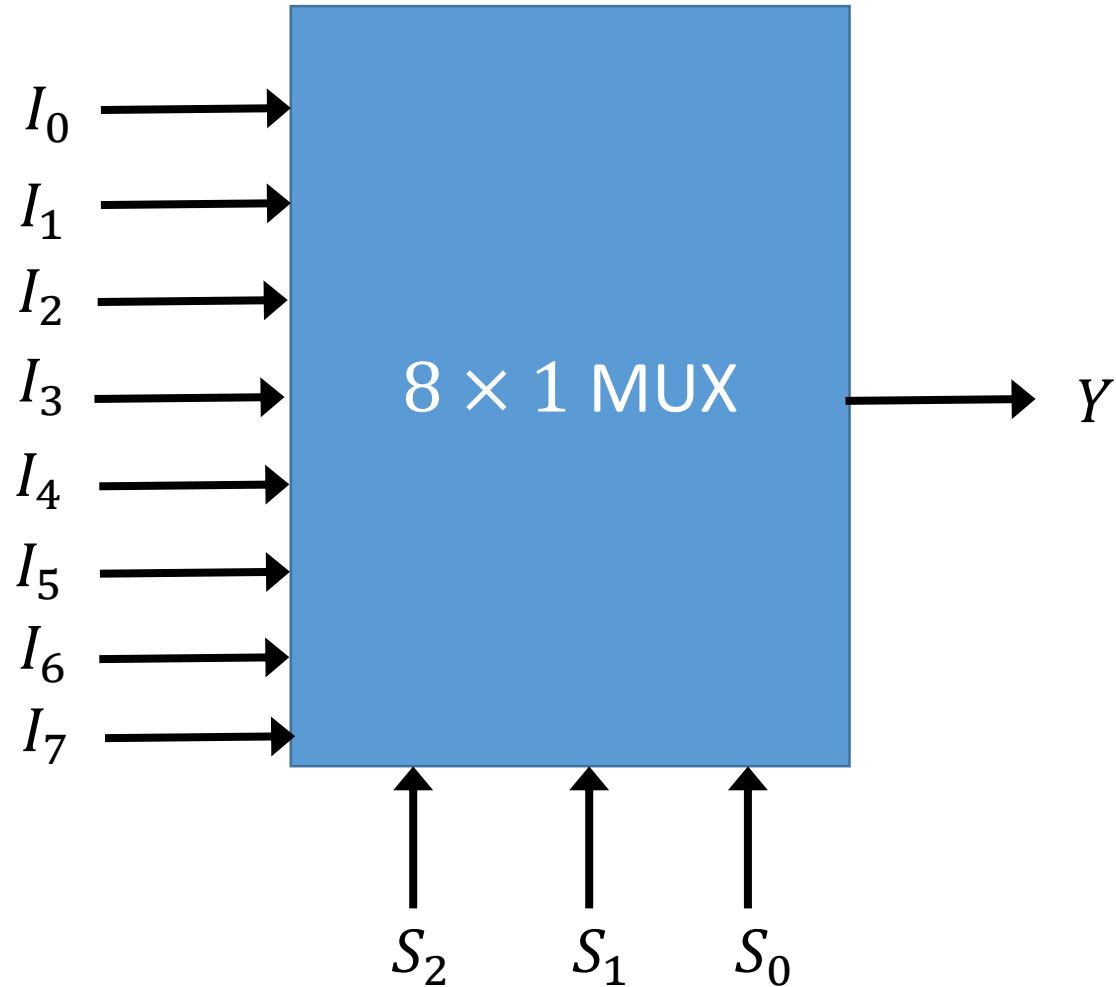



$S_2$	$S_1$	$S_0$	$Y$
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_2$
0	1	1	$I_3$
1	0	0	$I_4$
1	0	1	$I_5$
1	1	0	$I_6$
1	1	1	$I_7$

# 4 × 1 MUX using 2 × 1 MUX

$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$
$$= (\bar{S}_0 I_0 + S_0 I_1) \bar{S}_1 + (\bar{S}_0 I_2 + S_0 I_3) S_1 = Y_1 \bar{S}_1 + Y_2 S_1$$


↓  
 $Y_1$

↓  
 $Y_2$

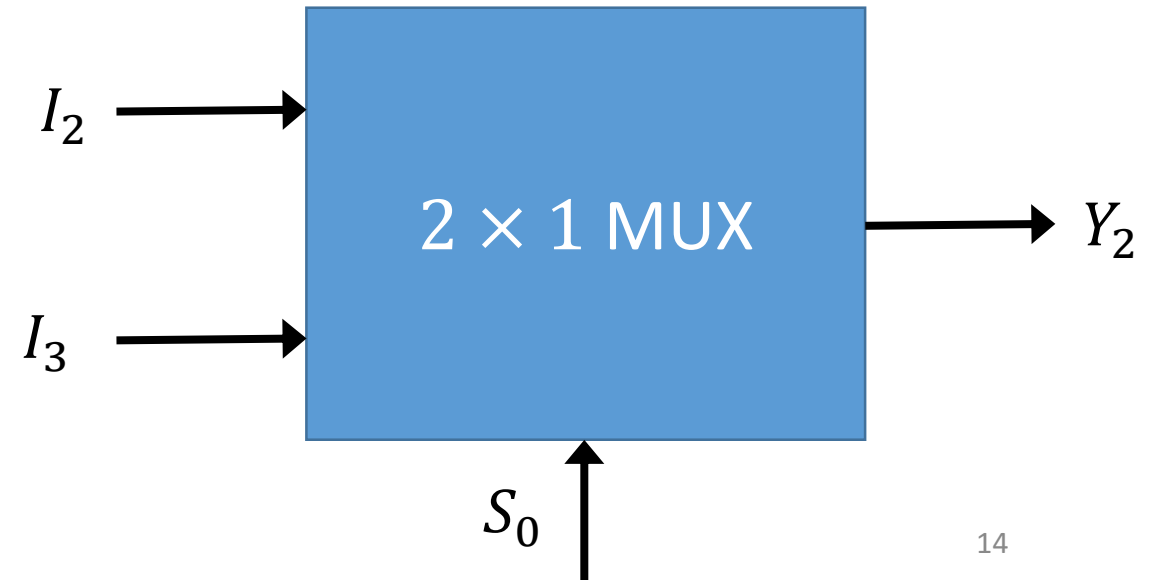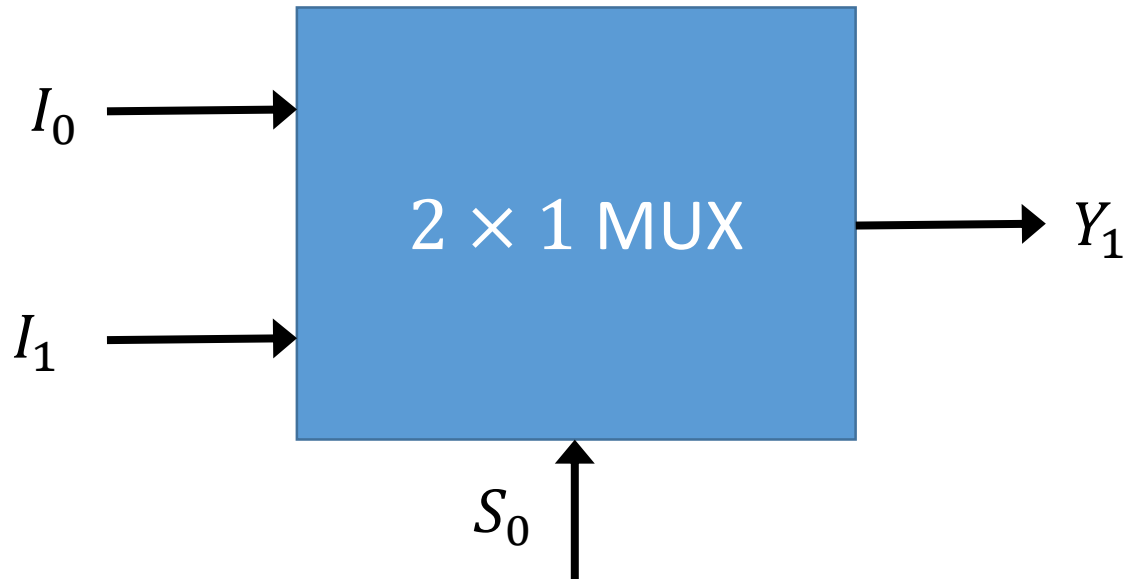


# 4 × 1 MUX using 2 × 1 MUX

$$Y = Y_1 \overline{S_1} + Y_2 S_1$$

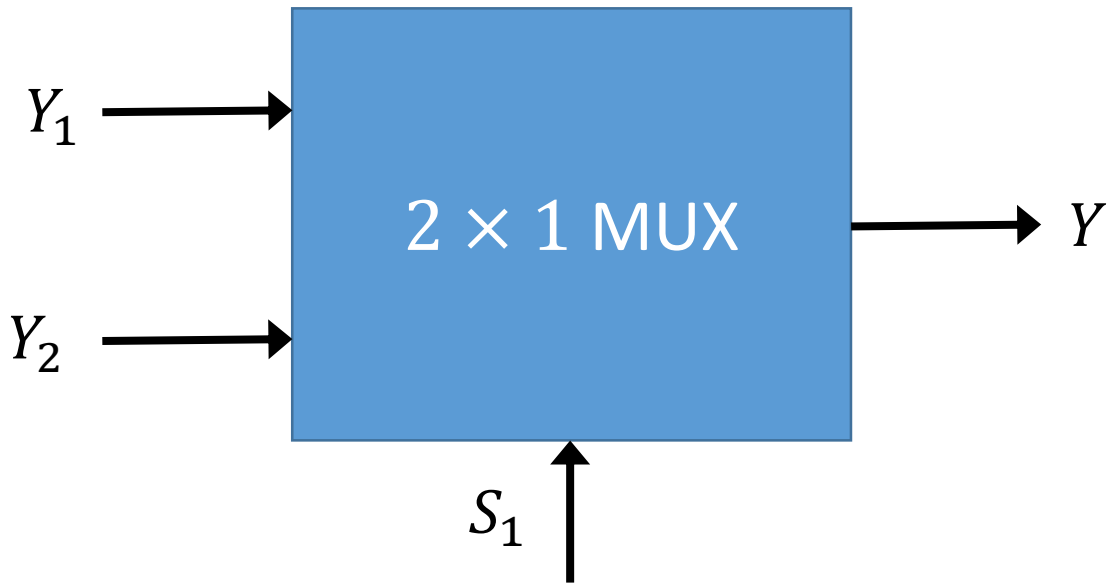

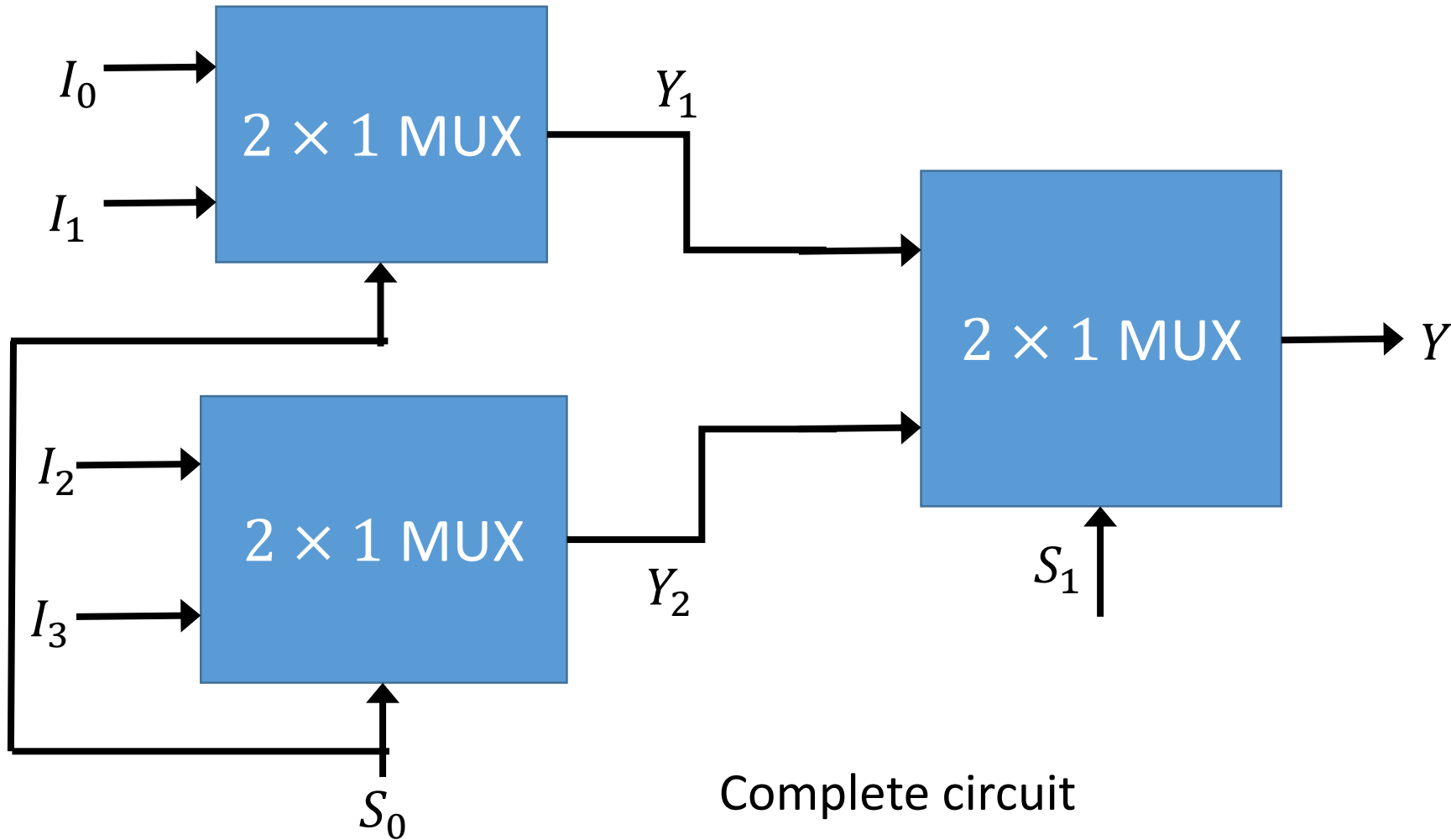
# $4 \times 1$ MUX using $2 \times 1$ MUX




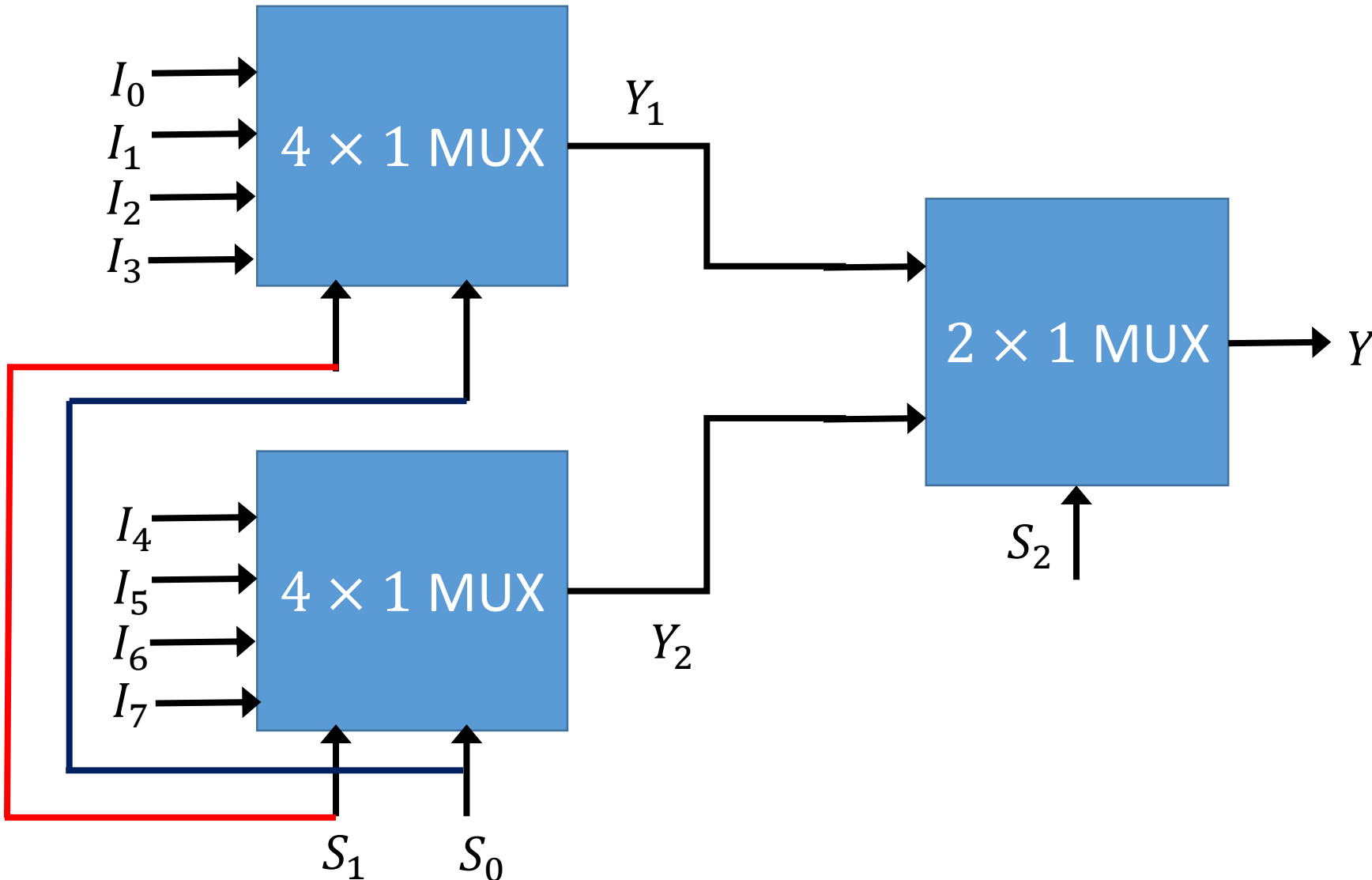
# $8 \times 1$ MUX using $4 \times 1$ and $2 \times 1$ MUX



# Implementation of Boolean Functions Using MUX

# Design Problem 1

- Implement the following function with a  $4 \times 1$  MUX:

$$F(a, b, c) = \sum m(1, 3, 5, 6)$$

- Solution: Step 1- Construct a truth table



Inputs			Output	
a	b	c	$F(a, b, c)$	
0	0	0	0	$F = c$
0	0	1	1	
0	1	0	0	$F = c$
0	1	1	1	
1	0	0	0	$F = c$
1	0	1	1	
1	1	0	1	$F = \bar{c}$
1	1	1	0	

# Design Problem 1

- Implement the following function with a  $4 \times 1$  MUX:

$$F(a, b, c) = \sum m(1, 3, 5, 6)$$

Inputs			Output
a	b	c	$F(a, b, c)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

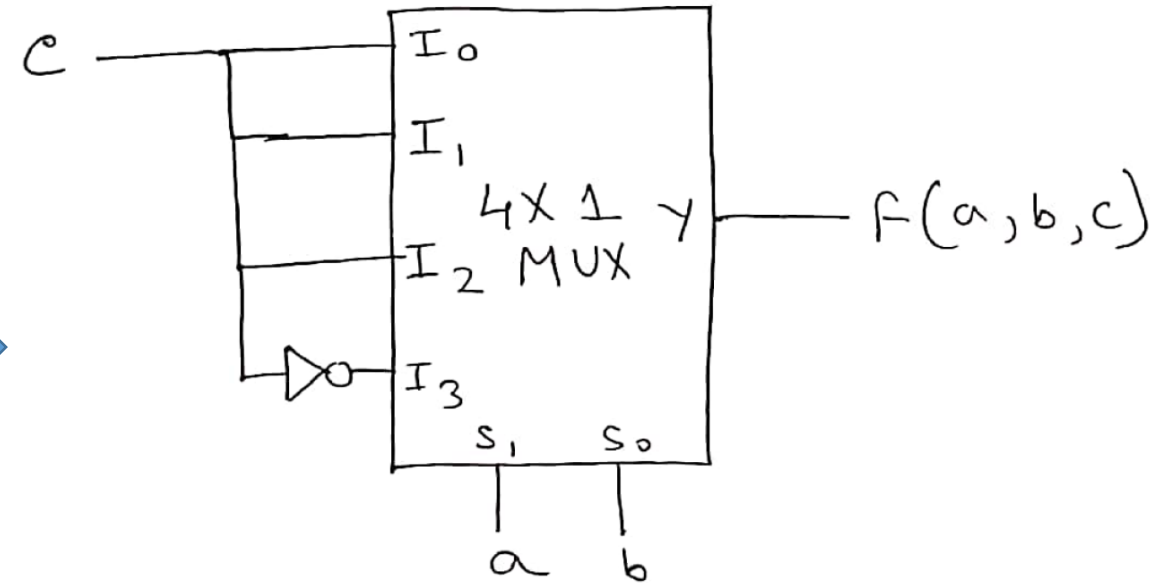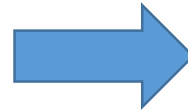

# Design Problem 2

- Implement the function  $F(a, b, c) = ab + \bar{b}c$  using a  $4 \times 1$  MUX.
- Solution:
- Express in terms of minterms
- $F(a, b, c) = ab + \bar{b}c = 11X + X01 = 110 + 111 + 001 + 101$
- $F(a, b, c) = \sum m(1, 5, 6, 7)$

# Design Problem 2

- Implement the function  $F(a, b, c) = ab + \bar{b}c$  using a  $4 \times 1$  MUX.

Solution:


- $F(a, b, c) = \sum m(1, 5, 6, 7)$

<u>Inputs</u>			<u>Output</u>	
<u>a</u>	<u>b</u>	<u>c</u>	<u><math>F(a, b, c)</math></u>	
0	0	0	0	$F = c$
0	0	1	1	
0	1	0	0	$F = 0$
0	1	1	0	
1	0	0	0	$F = c$
1	0	1	1	
1	1	0	1	$F = 1$
1	1	1	1	

# Design Problem 2

- Implement the function  $F(a, b, c) = ab + \bar{b}c$  using a  $4 \times 1$  MUX.

<u>Inputs</u>			<u>Output</u>	
<u>a</u>	<u>b</u>	<u>c</u>	<u><math>F(a, b, c)</math></u>	
0	0	0	0	$F = c$
0	0	1	1	
0	1	0	0	$F = 0$
0	1	1	0	
1	0	0	0	$F = c$
1	0	1	1	
1	1	0	1	$F = 1$
1	1	1	1	

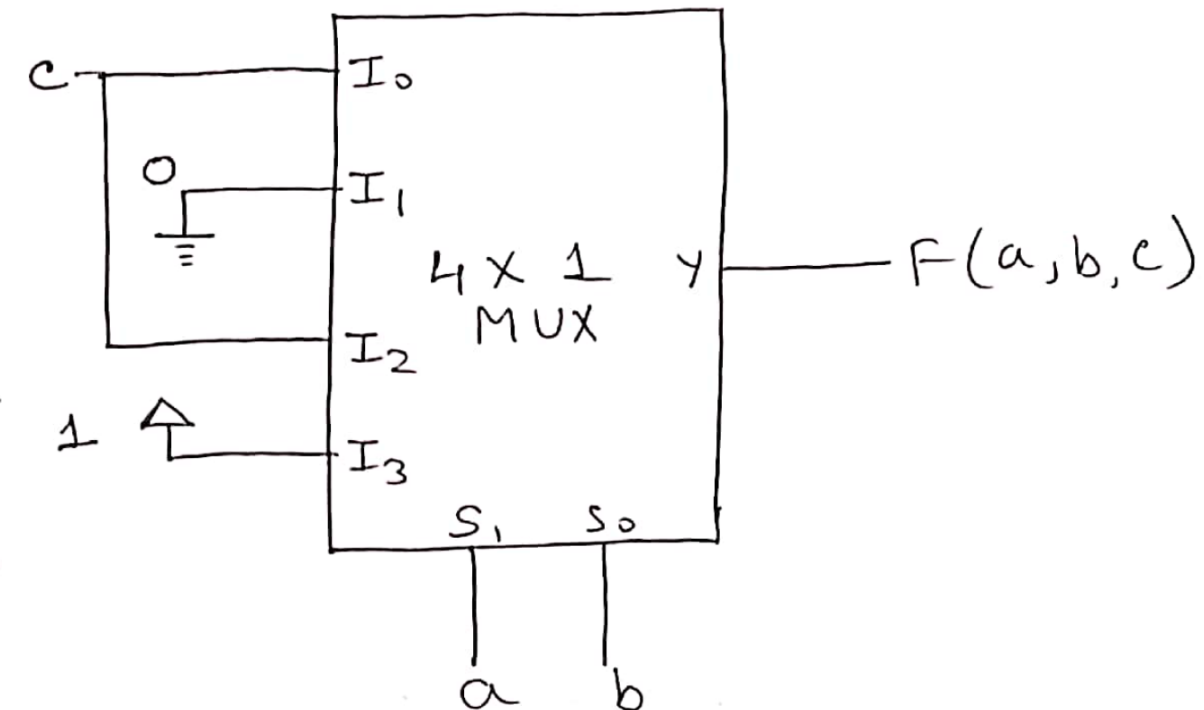

# Design Problem 3


- Implement the following logic function using an  $8 \times 1$  MUX:

$$F(A, B, C, D) = \prod M(0, 2, 5, 6, 7, 8, 9, 10)$$

Solution is shown in the next slide



<u>Inputs</u>				<u>Output</u>	
A	B	C	D	<u><math>F(A, B, C, D)</math></u>	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = \overline{D}$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

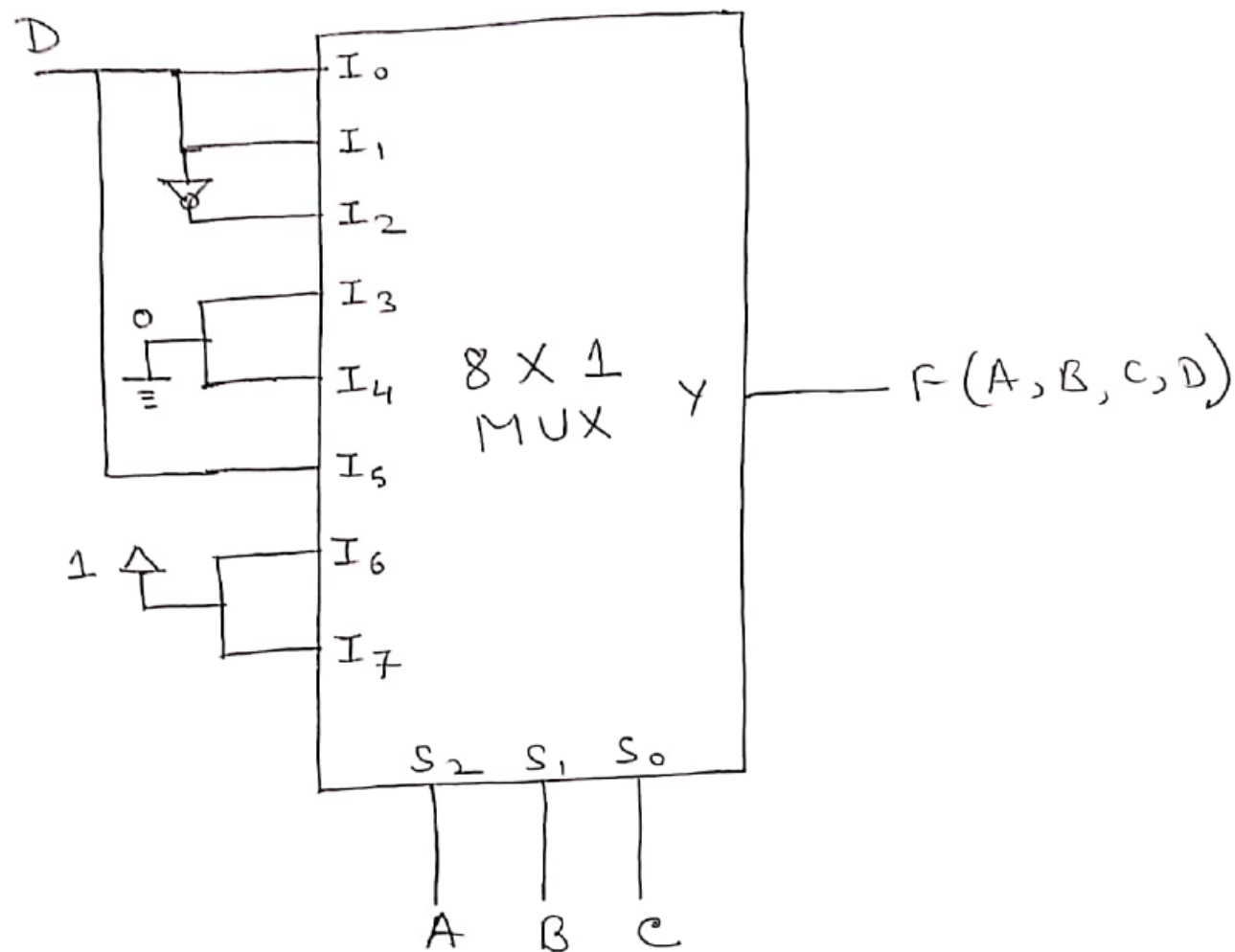

END