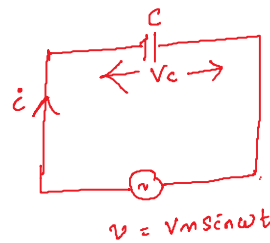


Behaviour of AC in Purely Capacitive Circuit



$$v = V_m \sin \omega t \quad \text{--- (1)}$$

$$i = C \frac{dv}{dt} = C \frac{dv_c}{dt}$$

$$= C \frac{d}{dt} (V_m \sin \omega t)$$

$$= C V_m \times \omega \cos \omega t \quad \text{--- (2)}$$


$$= C V_m \omega \cos \left(\frac{\pi}{2} + \omega t \right)$$

$$= \underbrace{\omega C V_m}_{I_m} \sin \left(\omega t + \frac{\pi}{2} \right) \quad \text{--- (3)}$$

$$\cos \omega t = \sin \left(\frac{\pi}{2} + \omega t \right) \quad \checkmark$$

$$= \sin \left(\frac{\pi}{2} - \omega t \right) \quad \times$$
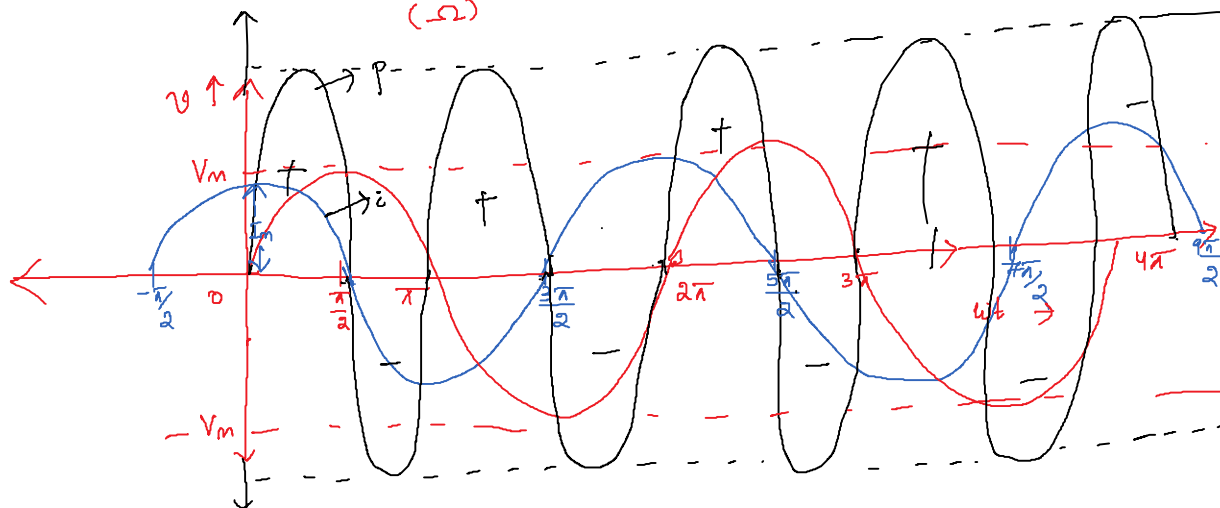
$$I_m = \frac{V_m}{X_c} = \frac{V_m}{\left(\frac{1}{\omega C} \right)}$$



$$\begin{aligned} \text{(1)} \quad P_{\text{instantaneous}} &= v i = V_m \sin \omega t \cdot I_m \sin \left(\omega t + \frac{\pi}{2} \right) \\ &= \frac{2 \cdot V_m \sin \omega t \cdot I_m \cos \omega t}{2} \\ &= V_m I_m / 2 \sin 2 \omega t \end{aligned}$$

$$\text{(2)} \quad P_{\text{avg}} = 0$$

$$\text{(3)} \quad P_{\text{active}} = V_{\text{rms}} I_{\text{rms}} \cos \frac{\pi}{2} = 0$$

$$\begin{aligned} \text{(4)} \quad P_{\text{reactive}} &= V_{\text{rms}} I_{\text{rms}} \sin \frac{\pi}{2} = V_{\text{rms}} I_{\text{rms}} \\ &= \text{Apparent} \end{aligned}$$

③

$Pf = \cos \frac{\pi}{2} = 0$ (leading) power

$Pf = 0$ leading
 $= 0$ lagging
 $= \Delta$ ($\phi = 0$)

Comparison of R, L, C

$i = I_m \sin(\omega t + \frac{\pi}{2})$

	<u>R</u>	<u>L</u>	<u>C</u>
Current	$I = \frac{V}{R}$	$I = \frac{V}{X_L}$ $I \propto \frac{1}{f}$	$I = \frac{V}{X_C}$ $I \propto f$
Frequency dependent	independent	$X_L \propto f$	$X_C \propto \frac{1}{f}$
Avg power	$I_{rms}^2 R / \frac{V_{rms}^2}{R}$	0	0
Phase diff	0°	90° lagging	90° leading

Q.1. A pure Capacitor of $318 \mu F$ is connected to a $230V, 50Hz$ supply. Calculate
 (i) X_C (ii) I_{rms} (iii) eqn for v, i

(i) $X_C = \frac{1}{\omega C} = \frac{1}{2\pi \times 50 \times 318 \times 10^{-6}} = 10 \Omega$

(ii) $I_{rms} = \frac{V_{rms}}{X_C} = \frac{230}{10} = 23 A$

(iii) $v = V_m \sin \omega t = V_{rms} \sqrt{2} \sin 314 \cdot 2t$
 $= \frac{23 \times \sqrt{2} \sin 314 \cdot 2t}{325 \cdot 27}$

(iv) $i = I_m \sin(\omega t + \frac{\pi}{2})$

$$(iv) \quad i = I_m \sin \left(\omega t + \frac{\pi}{4} \right) \quad \text{as } \omega =$$

$$= \frac{25\sqrt{2}}{32.5} \sin \left(314.2t + \frac{\pi}{4} \right)$$

$$\frac{180^\circ}{1^\circ} \rightarrow \frac{\pi}{180} \text{ rad.}$$

$$34^\circ \rightarrow \frac{34 \times \pi}{180} \text{ rad}$$

$$\pi \text{ rad} \rightarrow 180^\circ$$

$$1 \text{ rad} \rightarrow \frac{180}{\pi}^\circ$$

$$5 \text{ rad} \rightarrow \frac{5 \times 180}{\pi} \text{ degree}$$