

KIIT UNIVERSITY, BHUBANESWAR
AUTUMN MID-SEMESTER EXAMINATION – 2017
DIGITAL ELECTRONIC (EC-2011)

Full Marks: 25


Duration: 1hour 30 mins

- Answer any FIVE questions including question No.1 which is compulsory.
- The figures in the margin indicate full marks.
- Candidates are required to give their answers in their own words as far as practicable and all parts of a question should be answered at one place only.

- 1) A. The two numbers represented in signed 2's complement form are $P=11101101$ & $Q=11100110$. If Q is subtracted from P, then obtain the value in *signed 2's compliment* form. [1X5]

B. Represent 29_{10} in Hexadecimal & BCD.

 C. Simplify and minimize the output(f) of the logic circuit given below:



D. Design a **XNOR** gate using **NAND logic**.

E. Why the rows and columns of K-map are ordered in Gray code rather than binary numerical order. Explain in brief.

- 2) Obtain the minimized expression for the following 4-variable Boolean expression using K-map method. Implement the minimized expression using *minimum numbers of NAND gates only*. [5]

$$F = \pi M(4, 5, 8, 9, 12, 13). d(1, 6, 11)$$

- 3) A. 'XOR and XNOR gates can be used as a buffer as well as an inverter'. Justify [1]

B. Design a 4-bit **Full adder/subtractor** circuit using **XNOR** gates only. [2]

C. Implement 1-bit magnitude comparator using **2:4 active HIGH output decoder** and basic gates. [2]

- 4) A. Design a Combinational circuit **using 2-input basic gates only** which has three inputs A, B & C and three outputs X, Y & Z. When the decimal equivalent of the binary input is 0, 1, 3 or 5, the decimal equivalent of the binary output is one greater than the input and when decimal equivalent of the binary input is 2, 4, 6 or 7, the decimal equivalent of the binary output is one less than the input. [3]

B. (i) Simplify Boolean Expression $AB + AC + A\bar{C} + A\bar{B} + BC$ [2]

(ii) Perform BCD addition ($397+158$) [2]

- 5) What is Decoder? Implement a Full-Subtractor circuit using 3-8 decoder having active-Low output lines and **2-input AND gates**. [5]

- 6) A. Define '**positive logic system**' and '**negative logic system**'. [2]

B. Perform **BCD Subtraction** : ($206.7-147.8$) [2]

C. What is the **disadvantage** of binary parallel adder circuit? [1]

- 7) A. Draw a **Full Subtractor** using two **Half Subtractor** Circuits. [2]

B. State and Prove **Consensus Theorem**. [2]

C. **Minterms** and **Maxterms** are complement of each other. Justify [1]