




**KIIT UNIVERSITY, BHUBANESWAR**  
**AUTUMN MID-SEMESTER EXAMINATION – 2016**  
**DIGITAL ELECTRONICS (EC-2009), BRANCH: CSE & IT**

**Full Marks: 25**

**Duration: 2 hours**

- Answer any **FIVE** questions including question No.1 which is compulsory.
- The figures in the margin indicate full marks.
- Candidates are required to give their answers in their own words as far as practicable and all parts of a question should be answered at one place only.

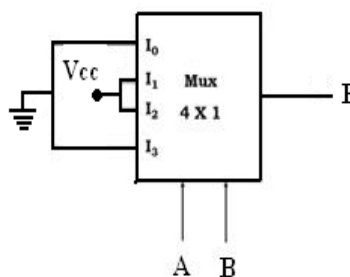1. a) Perform following arithmetic: (i) **BCD Subtraction** (858-749) [1x5]  
(ii) **(-13) - (-6)** using **2's complement** method  
b) Why the row and column values of the **K-Map** are ordered in **Gray code** rather than binary numerical order, explain in brief.  
c) With the help of a **4X1 MUX**, implement a **NOT** gate.  
d) If we transmitted a 7-bit **even parity hamming code** through a noisy channel and at the receiver we obtained '1110110'. Decode the correct 4-bit data word.  
e) Implement a **1 Bit Magnitude Comparator** in a **decoder** circuit.
2. Obtain a minimized expression for the following Boolean function using **K-map** and implement the minimized expression using minimum number of **NAND gates** only. [5]  
$$F(A,B,C,D) = \sum m(2,3,7,8,10,13) + d(9,11,15)$$
3. a) Implement a **Full-Subtractor** in a **Low Enable Decoder Circuit**. [3]  
b) Identify the Boolean function **F(A,B)** implemented with MUX [2]



4. a) Design a **2-bit Priority Encoder** where the input priorities are defined as **D<sub>1</sub> > D<sub>3</sub> > D<sub>0</sub> > D<sub>2</sub>** ; [4]  
where all **D<sub>i</sub>**'s are inputs to the priority encoder.  
b) Verify the following functions are **commutative but not associative**: [1]  
i) NOR ii) NAND

5. a) In a room, there are **3 electric lamps**. For sufficient light intensity, **at least two lamps** must be **turned on at the same time**. Design a circuit using **3x8 Decoder (Active High)** and basic gates, which enables an alarm when light intensity in the room is **not sufficient**. [3]
- b) Show that  $(X + Y' + XY)(X + Y')(X'Y) = 0$  [2]
6. a) Draw and explain a combined **4-bit adder/subtractor** block using full adders and **XNOR** gates only. [3]
- b) Define **minterms and maxterms**. Prove that minterms and maxterms are complement of each other [2]