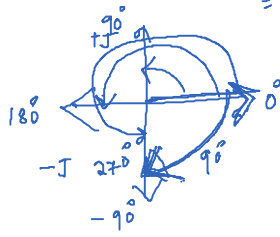



Monday, January 3, 2022 12:55 PM

$$0 + j = \tan^{-1}\left(\frac{j}{0}\right) = -90^\circ$$

$$0 - j = \tan^{-1}\left(\frac{-j}{0}\right) = +90^\circ$$



Series R-L Circuit

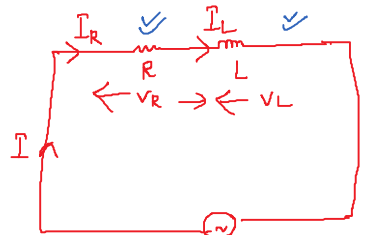

$$v = v_m \sin \omega t$$

$$= |V| \angle 0^\circ$$

polar form.

R



L



R-L


$$V = \vec{V}_R + \vec{V}_L$$

Phasor diagram

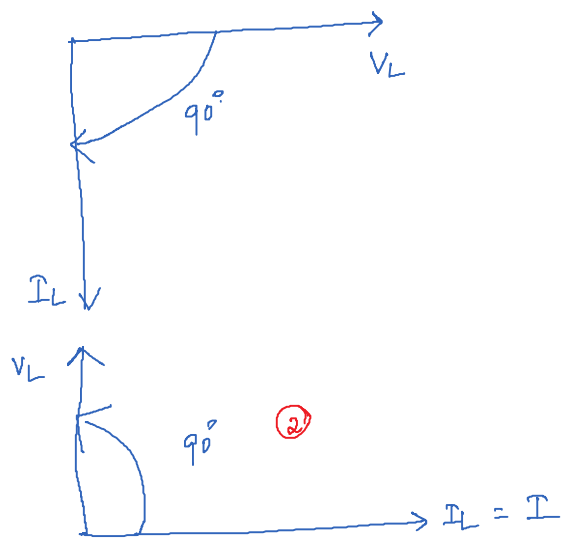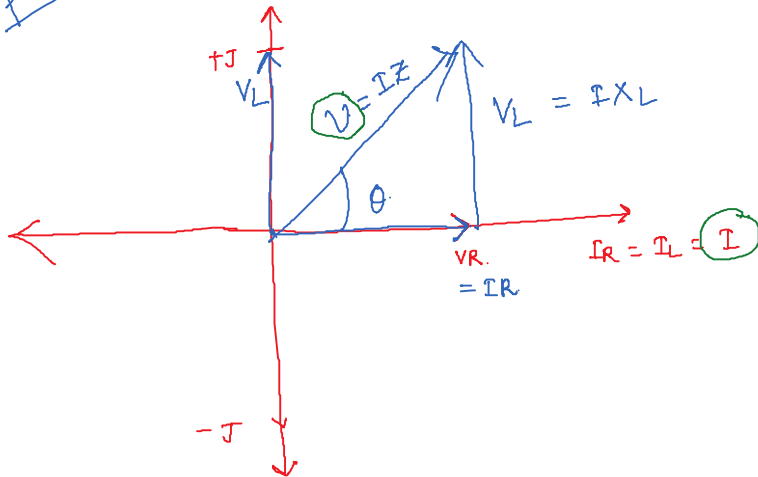

Impedance Triangle

Method 1

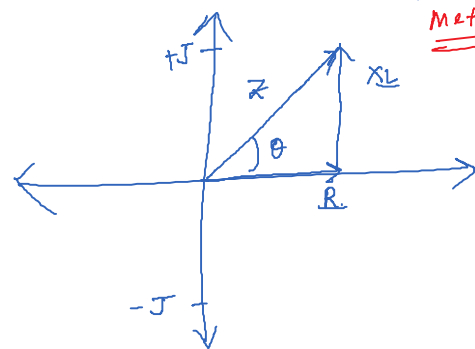

$$Z = R + jX_L$$

(Cartesian)

$$= |Z| \angle \theta$$

$$= \sqrt{R^2 + X_L^2} \angle \tan^{-1}\left(\frac{X_L}{R}\right)$$

Method.

11

$$V = \vec{V}_R + \vec{V}_L$$

$$= [IR + j0] + (0 + jIX_L)$$

$$IX = IR + jIX_L$$

$$Z = R + jX_L \quad \text{--- (2)}$$

Current

$$V = |V| \angle 0^\circ$$

$$I = \frac{V}{Z} = \frac{|V| \angle 0^\circ}{|Z| \angle \theta}$$

$$I = \frac{|V|}{|Z|} \angle -\theta \quad \checkmark$$

$$I = \frac{V_m}{\sqrt{R^2 + X_L^2}} \angle -\tan^{-1}\left(\frac{X_L}{R}\right) \quad \text{--- (1)}$$

$$\underline{v} = V_m \sin \omega t$$


$$\underline{i} = \frac{V_m}{\sqrt{R^2 + X_L^2}} \sin(\omega t - \tan^{-1}\left(\frac{X_L}{R}\right)) \quad \text{--- (2)}$$

$$(i) \quad P_{inst} = v \dot{i} = V_m \sin \omega t I_m \sin(\omega t - \theta) \quad \text{--- (3)}$$

$$= \frac{V_m I_m}{2} \left[2 \sin \omega t \sin(\omega t - \theta) \right]$$

$$= \frac{V_m I_m}{2} \left[\cos(A - B) - \cos(A + B) \right]$$
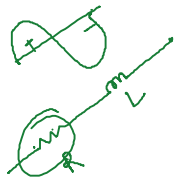
$$= \frac{V_m I_m}{2} \left[\cos \theta - \cos(2\omega t - \theta) \right] \quad \text{--- (4)}$$



$$(ii) \quad P_{avg} = \frac{V_m I_m}{2} \cos \theta$$

$$= \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}} \cos \theta = V_{rms} I_{rms} \cos \theta$$

$$= I_{rms} Z I_{rms} \frac{R}{Z}$$

$$= I_{rms}^2 R =$$

$$(iii) \quad pf = \cos \theta = \frac{R}{Z} \quad \checkmark$$

True power

$$\begin{aligned}
 \text{(iii) } PF &= \cos \theta = \frac{P}{S} \approx \\
 &= \frac{VI \cos \theta}{VI} = \frac{\text{Active power}}{\text{Apparent power}} \quad \text{True power}
 \end{aligned}$$

Ex: 1

A 50Hz sinusoidal voltage $V = 311 \sin \omega t$ is applied to a RL Series ckt. of the $R = 5 \Omega$ and $L = 0.02H$. Calculate (a) rms value of current and relative phase angle.

(b) expression for i

(c) avg power in the ckt.

(d) pf.

(e) Draw the phasor diagram?

$$\begin{aligned}
 \text{(a)} \quad I &= \frac{V}{Z} = \frac{\frac{311}{\sqrt{2}} \angle 0^\circ}{5 + j 2\pi \times 50 \times 0.02} = \frac{\frac{311}{\sqrt{2}} \angle 0^\circ}{5 + j 6.28}
 \end{aligned}$$

$$= \frac{\frac{311}{\sqrt{2}} \angle 0^\circ}{\sqrt{5^2 + 6.28^2} \angle \tan^{-1}\left(\frac{6.28}{5}\right)}$$

$$= \frac{\frac{311}{\sqrt{2}} \angle 0^\circ}{8.03 \angle 51.47^\circ}$$

$$I_{rms} = 27.39 A$$

$$P_m = I_{rms}^2 R$$

$$= 27.39 \angle -51.47^\circ$$

$$\text{(b)} \quad i = I_m \sin(\omega t - \theta)$$

$$= 27.39 \sqrt{2} \sin(\omega t - 51.47^\circ)$$

$$\text{(c)} \quad P_{avg} = I_{rms}^2 R$$

(c)


$$= (27.39)^2 \times 5$$

$$= 3751.06 \text{ W}$$

(d)

$$Pf = \cos 51.47^\circ = \underline{0.622, \text{lagging}}$$

(e)

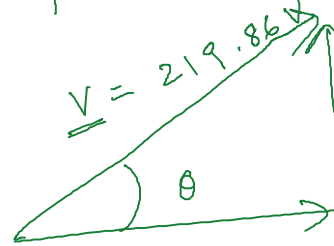

$$V_L = I X_L$$

$$= 27.39 \times 6.28$$

$$= 172.21$$

$$V_R = I R$$

$$= 27.39 \times 5$$

$$= 136.95 \text{ V}$$

$$V = \sqrt{172^2 + 136.95^2}$$

$$= \frac{311}{\sqrt{2}} = \underline{\underline{219.86 \text{ V}}}$$