 


Logic Gates

- Logic gates are electronic circuits that operates on one or more input signals to produce an output signal




x	y	$x.y$
0	0	0
0	1	0
1	0	0
1	1	1

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

x	x'
0	1
1	0

1


Switching Circuit

 

2

NOR Gate

 - NOR Symbol, Equivalent Circuit, Truth Table



3

NAND Gate




- This is a NAND gate. It is a combination of an AND gate followed by an inverter. Its truth table shows this...

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

4

XOR Gate (Exclusive-OR)

 


- This is a XOR gate.
- The switching algebra symbol for this operation is \oplus , i.e. $A \oplus B$.
- $A \oplus B = A'B + AB'$.

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

5

XNOR Gate (Exclusive-NOR)

 

- This is an Exclusive-NOR gate
- The complement of the XOR gate.
- The switching algebra symbol for this operation is \odot , i.e. $A \odot B$.
- $A \odot B = AB + A'B'$.


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

6

- NAND, NOR gates are called universal gate.
- AND, OR and NOT are called basic gates.
- XOR(EX-OR), XNOR(EX-NOR) are called derived gates.

7


S-R Latch with NOR Gates

 

- S-R latch made from cross-coupled NORs
- If $Q = 1$, set state
- If $Q = 0$, reset state
- Usually $S=0$ and $R=0$ is called Memory state
- $S=1$ and $R=1$ generates undefined or indeterminate results.

8



S-R Latch with NAND Gates

 

- S-R Latch made from **cross-coupled** NANDs
- Sometimes called S'-R' latch
- Usually S=1 and R=1 is called Memory state
- S=0 and R=0 generates undefined or indeterminate results.


9

S-R Latches

  


10

Graphic symbol of S-R Latch

 

11

S-R Latch with control input

 

- S-R Latch with control input is called Flip-Flop
- It is used to store one bit of information
- Occasionally, desirable to avoid latch changes
- **C = 0** disables all latch state changes
- Control signal **enables** data change when **C = 1**
- Right side of circuit same as ordinary S-R latch.

12

Clocks and synchronization


- A **clock** is a special device that whose output continuously alternates between 0 and 1.



- The time it takes the clock to change from 1 to 0 and back to 1 is called the **clock period**, or **clock cycle time**.
- The **clock frequency** is the inverse of the clock period. The unit of measurement for frequency is the **hertz**.


13

Graphic symbol of S-R Flip-Flop

 

14

J-K Flip-Flop

 


- S-R Latch with control input is called Flip-Flop
- Replace the two input NAND gate with the three input NAND gate to get a J-K Flip Flop from a S-R FF.
- $C = 0$ disables all the data changes
- Control signal $C=1$ **enables** data change when $C = 1$

15


Flip-Flops

 - A flip-flop is a state of a latch that can be switched by momentary change in the control input.
- This momentary change is called a trigger and the transition it causes is said to trigger the flip-flop.
- The flip-flop is triggered every time the pulse goes to a high or logic level 1.



- The problem with the flip-flops is that as long as the input clock pulse remains at this level, any changes in the input data will cause a change in the output and the state of the latch.
- Race around condition or Racing.

16

 

The Master-Slave Flip-Flop is basically two gated SR flip-flops connected together in a series configuration with the slave having an inverted clock pulse. The outputs from Q and Q from the "Slave" flip-flop are fed back to the inputs of the "Master" with the outputs of the "Master" flip-flop being connected to the two inputs of the "Slave" flip-flop. This feedback configuration from the slave's output to the master's input gives the characteristic toggle of the JK flip-flop .

The input signals J and K are connected to the gated "master" SR flip-flop which "locks" the input condition while the clock (Clk) input is "HIGH" at logic level "1". As the clock input of the "slave" flip-flop is the inverse (complement) of the "master" clock input, the "slave" SR flip-flop does not toggle. The outputs from the "master" flip-flop are only "seen" by the gated "slave" flip-flop when the clock input goes "LOW" to logic level "0".

18


When the clock is "LOW", the outputs from the "master" flip-flop are latched and any additional changes to its inputs are ignored. The gated "slave" flip-flop now responds to the state of its inputs passed over by the "master" section. Then on the "Low-to-High" transition of the clock pulse the inputs of the "master" flip-flop are fed through to the gated inputs of the "slave" flip-flop and on the "High-to-Low" transition the same inputs are reflected on the output of the "slave" making this type of flip-flop edge or pulse-triggered.

Then, the circuit accepts input data when the clock signal is "HIGH", and passes the data to the output on the falling-edge of the clock signal. In other words, the **Master-Slave JK Flip-flop** is a "Synchronous" device as it only passes data with the timing of the clock signal.

19


The Solution

 - A clock pulse goes through two transition from 0 to 1 and the return from 1 to 0
- The solution: by changing the operation of a flip-flop to trigger it only during a signal transition.
- Two types of transition: the positive transition (from 0 to 1) and the negative transition (from 1 to 0)




20

Flip-Flop Symbols

 


21

J-K flip flop Symbols

 

22

D-Flip Flop

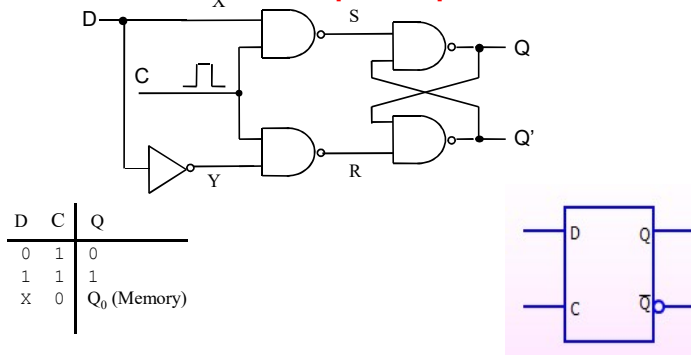


Input value D is passed to output Q when C is high
Input value D is ignored when C is low

23

Clocked D Flip-Flop

 
- Stores a value on the positive edge of C
- Input changes at other times have no effect on output



24

Clocked J-K Flip Flop

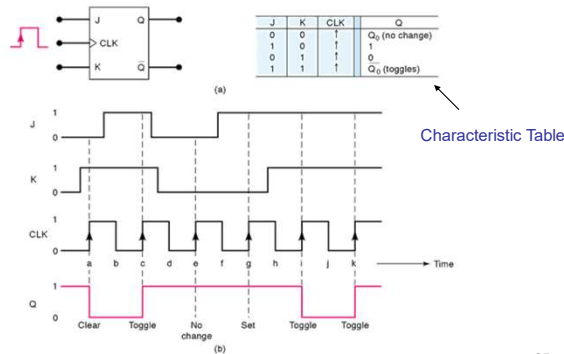- Two data inputs, J and K
- J → set, K → reset, if J=K=1 then toggle output



25

Registers

- A flip-flop can store only one bit data (0 or 1)
 - A single-bit register
- Register consists of a group of flip-flops and gates
- An n-bit register consists of n-bit flip-flops
 - store n-bit information
- Shift register is used to store and shift data.


26

Types of Shift Register

- Serial in serial out (SISO)
- Serial in Parallel out (SIPO)
- Parallel in serial out (PISO)
- Parallel in Parallel out (PIPO)

27

Shift Registers(SISO)

 

- Shifts binary information in one or both directions.
- On the positive edge of the first clock pulse, the signal on the **in** is latched in the first FF.
- On the next clock pulse, the data of the first FF is stored in the second FF, and the data present at the **in** is stored in the first FF, etc.

28

Counters

- Binary counter: follows the binary number sequence.
- An n-bit binary counter:
 - Consists of n flip-flops
 - Can count in binary from 0 to $2^n - 1$
- A counter is a register that goes through a sequence of states.

29

Counters

- Counter categories:
 - Ripple counters
 - Synchronous counters
- **Ripple counters:** The flip-flop's output transition triggers other flip-flops.
- **Synchronous counters:** A common clock triggers all flip-flops simultaneously rather than one at a time in succession as in ripple counters.

30


Binary Ripple Counter

- All the J and K inputs of all the flip-flops are connected to a logic 1.
- Each flip-flop complements if the signal in its C input goes through a negative transition.
- The flip-flop holding the LSB receives the incoming count pulses.
- The count starts with binary 0 and increments by one with each count pulse input.

EC402 Digital Electronic Circuits
Spring 2011



31

3-bit Binary Ripple Counter

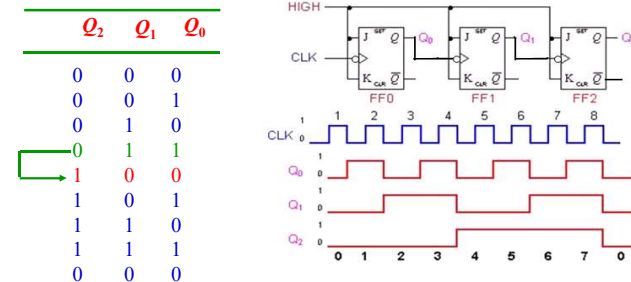

Q_0 is complemented with the count pulse. Since Q_0 goes from 1 to 0, it triggers Q_1 and complements it. As a result, Q_1 goes from 1 \rightarrow 0, which in turn complements Q_2 changing it from 0 \rightarrow 1. Q_2 does not trigger Q_3 because Q_2 produces a positive transition. The flip-flops change one bit at a time in succession and the signal propagates through the counter in a ripple fashion from one stage to the next.

32

 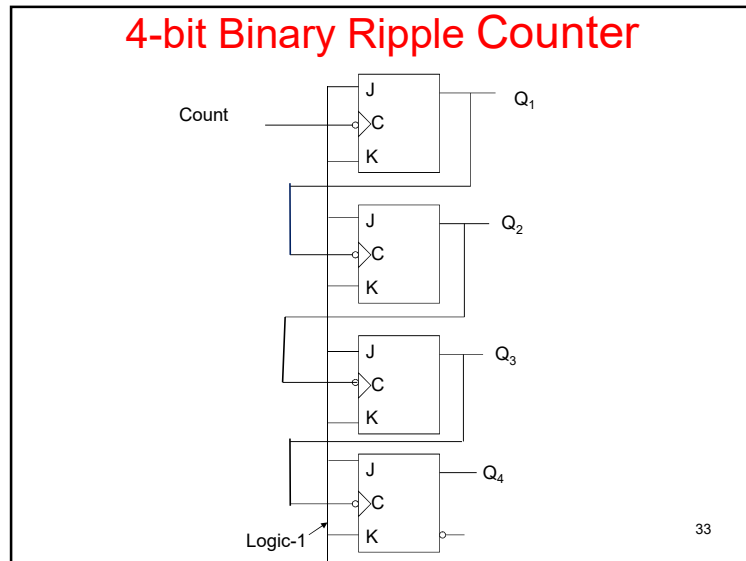

Problems with Ripple Counter

- **Asynchronous or ripple counters** are arranged in such a way that the output of one flip flop changes the state of the next.
- In a long chain of ripple counter stages, the last flip flop changes its state considerably later than the first FF due to propagation delays in each stage.
- Problems occur if this delay is longer than the response time of other logic elements connected to the circuit.

35