 


JK Flip-flop:



```
module JKFF(output Q,output Qb, input J,input K, input clk,input CLR,input PRE);
```

```
reg Q; // output Q and Qb defined as register
```

```
reg Qb;
```

```
initial
```

```
begin
```

```
Q=0;
```

```
Qb=1;
```

```
end
```

```
always @ (negedge clk or negedge CLR or negedge PRE)
```

```
begin
```

```
if (CLR == 0)
```

```
begin
```

```
Q = 0;
```

```
Qb = 1;
```

```
end
```

```
else
```

```
if (PRE == 0)
```

```
begin
```

```
Q = 1;
```

```
Qb = 0;
```

```
end
```

```
else
```

```
if ( J == 0 & K == 0 )
```

```
begin
```

```
Q = Q;
```

```
Qb = ~Q;
```

```
end
```

```
else
```

```
if ( J == 0 & K == 1 )
```

```
begin
```

```
Q = 0;
```

```
Qb = 1;
```

```
end
```

```
else
```

```
if ( J == 1 & K == 0 )
```

```
begin
```

```
Q = 1;
```


```
Qb = 0;
```

```

    end
else
    if ( J == 1 & K == 1 )
    begin
        Q = ~Q;
        Qb = ~Qb;
    end
end

end
endmodule

```

 

D Flip-flop

```

module DFF(output Q,output Qb, input D,input clk,input CLR,input PRE);
reg Q;    // output Q and Qb defined as register
reg Qb;
initial
    begin
        Q=0;
        Qb=1;
    end
always @(posedge clk or negedge CLR or negedge PRE)
begin
    if (CLR == 0)
        begin
            Q = 0;
            Qb = 1;
        end
    else
        if (PRE == 0)
            begin
                Q = 1;
                Qb = 0;
            end
        else
            begin
                Q = D;
                Qb = ~D;
            end
        end
    end
endmodule

```

4 bit SISO:

```
module SISO (d_out,d_outb,d_in,clk,CLR,PRE);
    input d_in,clk,CLR,PRE;
    output d_out,d_outb;

    wire Q3,Q3b,Q2,Q2b,Q1,Q1b;

    D_FF flip_flop1 (Q1,Q1b,d_in,clk,CLR,PRE);
    D_FF flip_flop2 (Q2,Q2b,Q1,clk,CLR,PRE);
    D_FF flip_flop3 (Q3,Q3b,Q2,clk,CLR,PRE);
    D_FF flip_flop4 (d_out,d_outb,Q3,clk,CLR,PRE);

endmodule
```

2 bit asynchronous counter using JK Flip flops:

```
module two_bit_asynch_counter (Q1,Q0,Q1b,Q0b,clk,CLR,PRE);

    output Q1,Q0,Q1b,Q0b;
    input clk,CLR,PRE;

    JK_FF flip_flop1 (Q0,Q0b,1,1,clk,CLR,PRE);

    JK_FF flip_flop2 (Q1,Q1b,1,1,Q0,CLR,PRE);

endmodule
```