

Exp 1 to 8 All HDL Codes with Testbench

Experiment 1:

SOP implementation of Boolean function using $F(A, B, C) = \sum (1,3,6,7)$ using NAND gates.

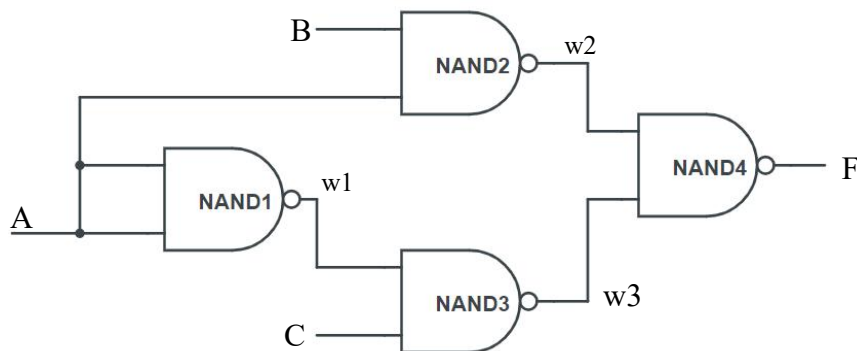


Figure 1: SOP implementation of Boolean function using NAND gates.

```
module SOP ( output F, input A, input B, input C );  
    wire w1,w2,w3 ;  
    nand NAND1 (w1,A,A) ;  
    nand NAND2 (w2,A,B) ;  
    nand NAND3 (w3,w1,C) ;  
    nand NAND4 (F,w2,w3) ;  
endmodule
```

POS implementation of Boolean function using $F(A, B, C) = \prod (0,2,4,5)$ using NOR gates.

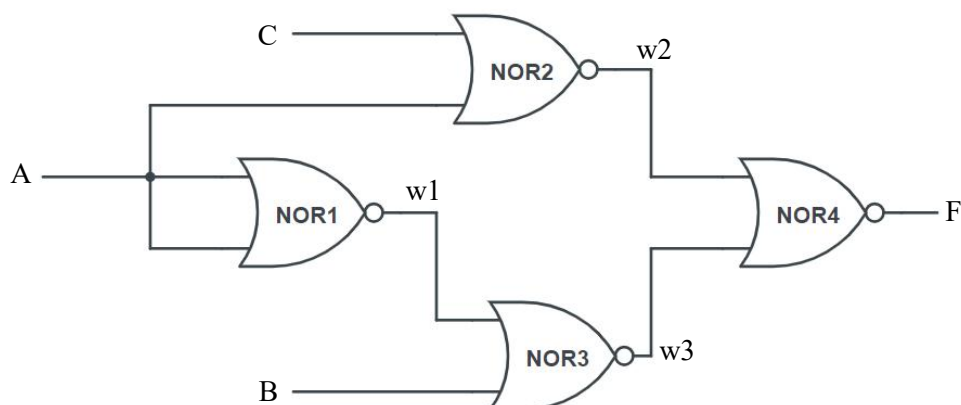


Figure 2: POS implementation of Boolean function using NOR gates.

```

module POS ( output F, input A, input B, input C );
    wire w1,w2,w3 ;
    nor NOR1 (w1,A,A) ;
    nor NOR2 (w2,A,C) ;
    nor NOR3 (w3,w1,B) ;
    nor NOR4 (F,w2,w3) ;
endmodule

```

Design Problem :

Warning indicator using NAND and NOR gates.

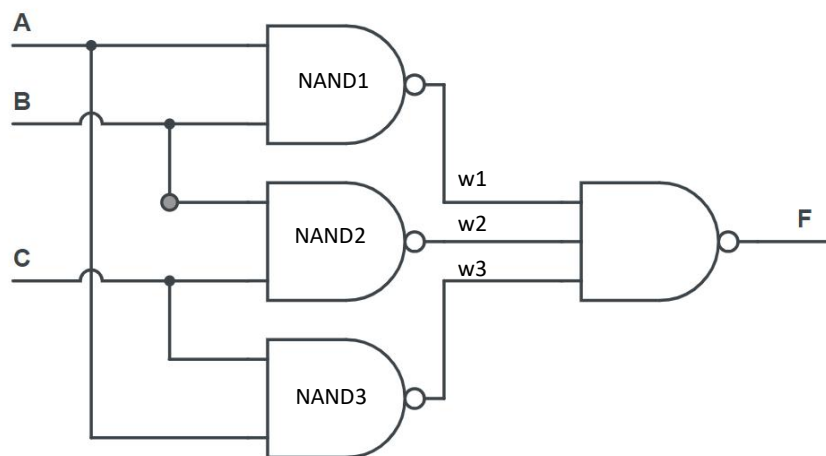


Figure 3: Implementation of warning indicator using NAND gates.

```

module warning_indicator ( output F, input A, input B, input C );
    wire w1,w2,w3;
    nand NAND1 (w1,A,B);
    nand NAND2 (w2,B,C);
    nand NAND3 (w3,A,C);
    nand NAND4 (F,w1,w2,w3);
endmodule

```

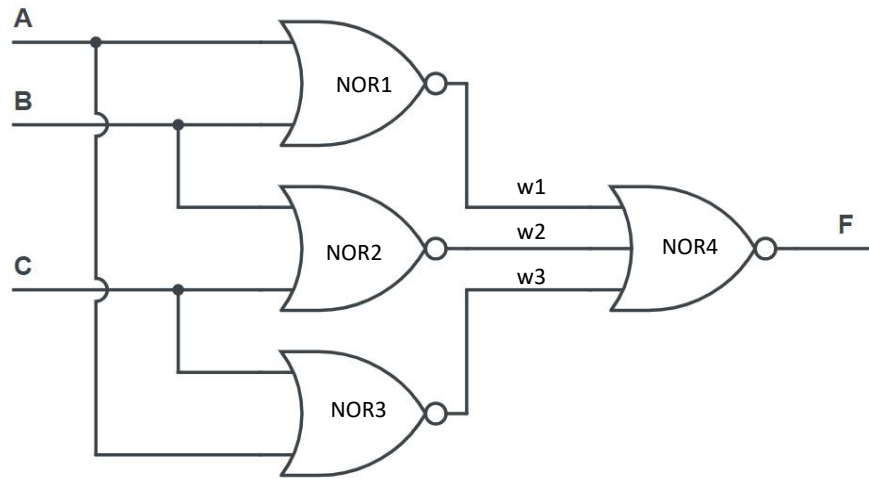


Figure 4: Implementation of warning indicator using NOR gates.

```

module warning_indicator ( output F, input A, input B, input C );
  wire w1,w2,w3;
  nor NOR1 (w1,A,B);
  nor NOR2 (w2,B,C);
  nor NOR3 (w3,A,C);
  nor NOR4 (F,w1,w2,w3);
endmodule

```

Experiment 2:

Full Adder using Logic Gates

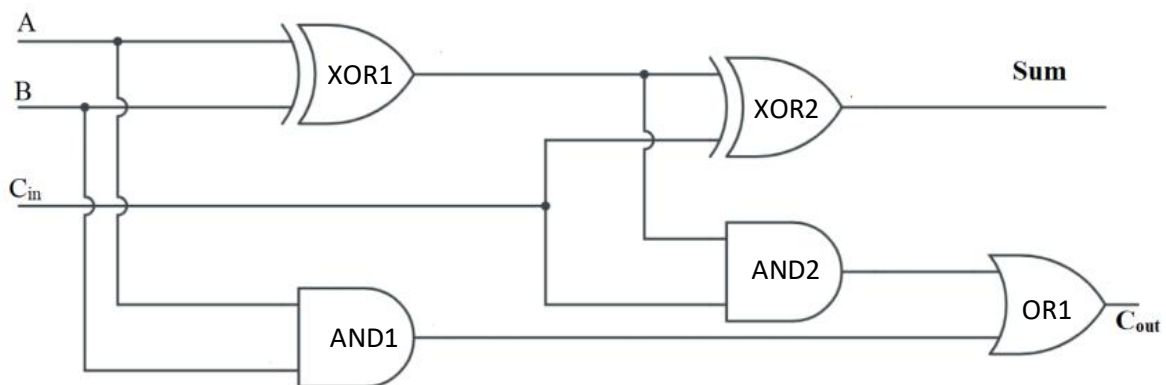


Figure 5: Full Adder using Logic Gates

```
module Full_Adder ( output Cout, output Sum, input A, input B,input Cin ) ;  
    wire w0,w1,w2 ;  
    xor  XOR1 (w0,A,B) ;  
    and  AND1 (w1,A,B) ;  
    xor  XOR2 (Sum,w0,Cin) ;  
    and  AND2 (w2,w0,Cin) ;  
    or   OR1  (Cout,w1,w2) ;  
endmodule
```

Design Problem:

Full Subtractor using Logic Gates

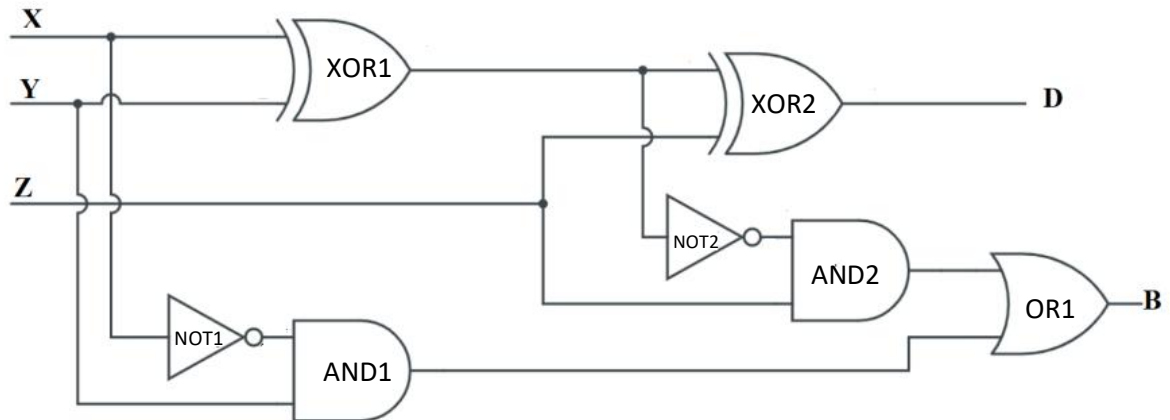


Figure 6: Full Subtractor using Logic Gates

```
module Full_Sub ( output B, output D, input X, input Y, input Z ) ;  
    wire w0,w1,w2,w3,w4,w5 ;  
    xor XOR1 (w0,X,Y) ;  
    not NOT1 (w1,X) ;  
    and AND1 (w2,w1,Y) ;  
    xor XOR2 (D,w0,Z) ;  
    not NOT2 (w4,w0) ;  
    and AND2 (w5,w4,Z) ;  
    or OR1 (B,w2,w5) ;  
endmodule
```

Experiment 3:

3 line to 8 line Decoder using Logic Gates

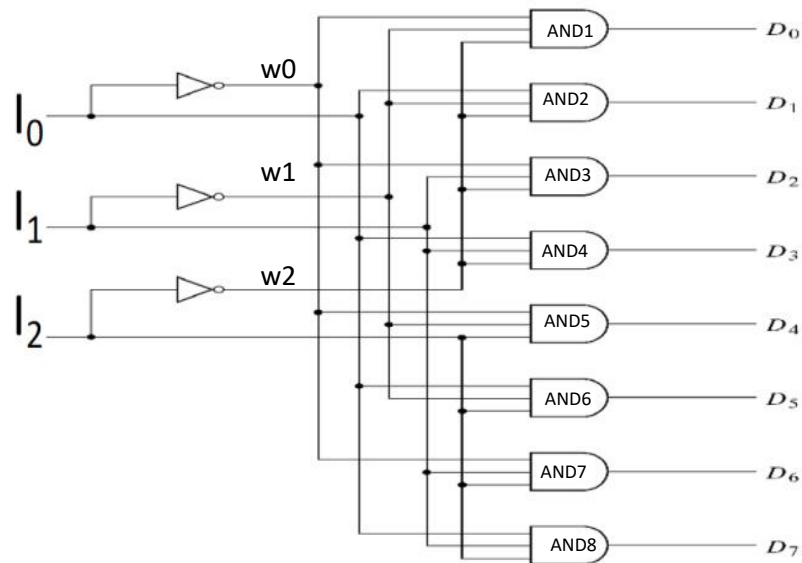


Figure 7: 3 line to 8 line Decoder using Logic Gates

```
module Decoder_three_to_eight ( output D0, output D1, output D2, output D3,  
                                output D4, output D5, output D6, output D7,  
                                input I2, input I1, input I0 );
```

```
    wire w0,w1,w2;
```

```
    not NOT1 (w0,I0);
```

```
    not NOT2 (w1,I1);
```

```
    not NOT3 (w2,I2);
```

```
    and AND1 (D0,w2,w1,w0);
```

```
    and AND2 (D1,w2,w1,I0);
```

```
    and AND3 (D2,w2,I1,w0);
```

```
    and AND4 (D3,w2,I1,I0);
```

```
    and AND5 (D4,I2,w1,w0);
```

```
    and AND6 (D5,I2,w1,I0);
```

```
    and AND7 (D6,I2,I1,w0);
```

```
    and AND8 (D7,I2,I1,I0);
```

```
endmodule
```

Design Problem:


Implementation of 3 bit Binary to Gray Code-converter using Decoder.

```
module Binary_to_Gray ( output G2, output G1,output G0,input B2,input B1,input B0 ) ;  
    wire w0,w1,w2,w3,w4,w5,w6,w7 ;  
    Decoder_three_to_eight Decoder1 ( w0,w1,w2,w3,w4,w5,w6,w7,B2,B1,B0) ;  
    or OR1 (G2,w4,w5,w6,w7) ;  
    or OR2 (G1,w2,w3,w4,w5) ;  
    or OR3 (G0,w1,w2,w5,w6) ;  
endmodule
```

Note: To simulate 3 bit Binary to Gray code-converter using 3:8 Decoder the module of 3:8 Decoder should be in the same project. Here the 3:8 Decoder module is called to implement the 3 bit Binary to Gray code-converter .

Experiment 4:

8 X 1 MUX using Logic Gates

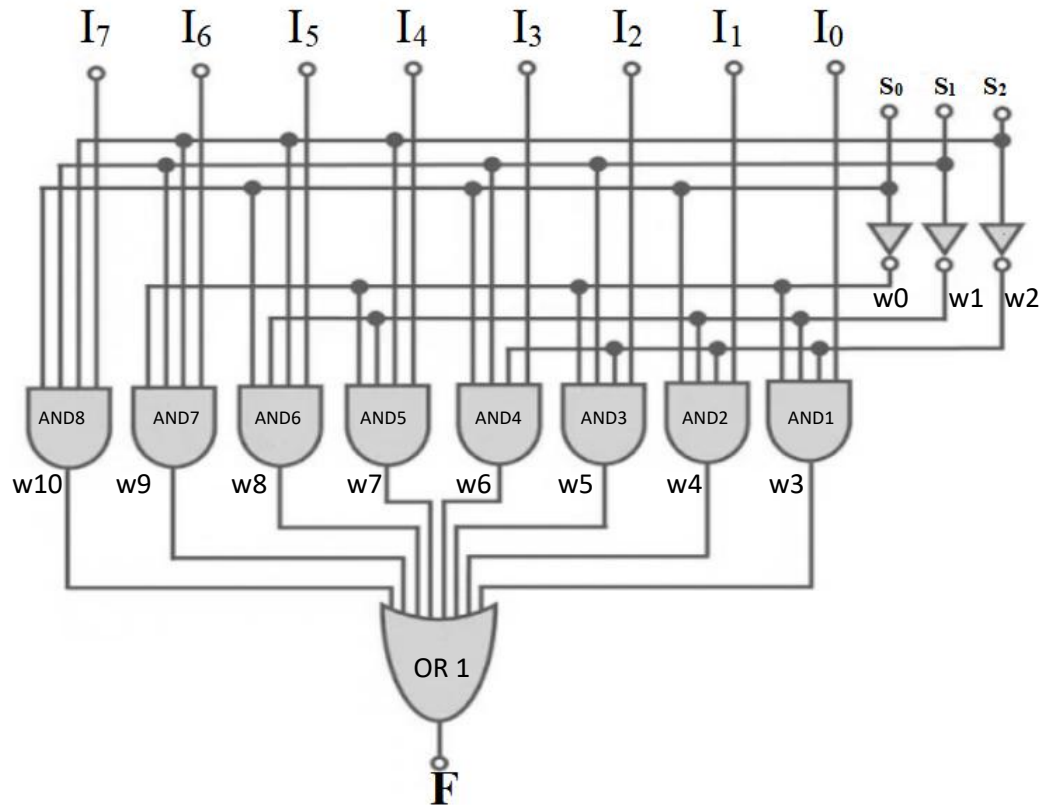

```
module MUX_eight_to_one ( output F, input S2, input S1, input S0, input I7, input I6,  
                           input I5, input I4, input I3, input I2, input I1, input I0 ) ;  
  
    wire w0,w1,w2,w3,w4,w5,w6,w7,w8,w9,w10 ;  
  
    not NOT1 (w0,S0) ;  
    not NOT2 (w1,S1) ;  
    not NOT3 (w2,S2) ;  
  
    and AND1 (w3,I0,w2,w1,w0) ;  
    and AND2 (w4,I1,w2,w1,S0) ;  
    and AND3 (w5,I2,w2,S1,w0) ;  
    and AND4 (w6,I3,w2,S1,S0) ;  
    and AND5 (w7,I4,S2,w1,w0) ;  
    and AND6 (w8,I5,S2,w1,S0) ;  
    and AND7 (w9,I6,S2,S1,w0) ;  
    and AND8 (w10,I7,S2,S1,S0) ;  
  
    or OR1 (F,w3,w4,w5,w6,w7,w8,w9,w10) ;  
  
endmodule
```


Design Problem:

4 X 1 MUX using the 2 X 1 MUX.

```
module two_to_one_mux (output F, input S0, input I1, input I0);
```

```
    wire w0,w1,w2;
```

```
    nand NAND1 (w0,S0,S0);
```

```
    nand NAND2 (w1,w0,I0);
```

```
    nand NAND3 (w2,S0,I1);
```

```
    nand NAND4 (F,w1,w2);
```

```
endmodule
```

Simulation of 4 X 1 MUX using 2 X 1 MUXs:

```
module four_to_one_mux ( output F, input S1, input S0, input I3, input I2, input I1,  
                        input I0 );
```

```
    wire w1,w2;
```

```
    two_to_one_mux Mux1 (w1,S0,I1,I0);
```

```
    two_to_one_mux Mux2 (w2,S0,I1,I0);
```


```
    two_to_one_mux Mux3 (F,S1,w2,w1);
```

```
endmodule
```

Note: To simulate 4X1 MUX using 2X1 MUXs the module of 2X1 MUX should be in the same project. Here the 2X1 MUX module is called three times namely Mux1, Mux2, Mux3 to implement the 4X1 MUX.

Experiment 5


D Flip-flop:

 

```
module DFF(output Q,output Qb, input D,input clk,input CLR,input PRE);
```

```
reg Q;    // output Q and Qb defined as register
reg Qb;
initial
  begin
    Q=0;
    Qb=1;
  end
always @(posedge clk or negedge CLR or negedge PRE)
begin
  if (CLR == 0)
    begin
      Q = 0;
      Qb = 1;
    end
  else
    if (PRE == 0)
      begin
        Q = 1;
        Qb = 0;
      end
    else
      begin
        Q = D;
        Qb = ~D;
      end
    end
end
endmodule
```

JK Flip-flop:

 

```
module JKFF(output Q,output Qb, input J,input K, input clk,input CLR,input PRE);
```

```
reg Q; // output Q and Qb defined as register
```

```
reg Qb;
```

```
initial
```

```
begin
```

```
    Q=0;
```

```
    Qb=1;
```

```
end
```

```
always @ (negedge clk or negedge CLR or negedge PRE)
```

```
begin
```

```
    if (CLR == 0)
```

```
        begin
```

```
            Q = 0;
```

```
            Qb = 1;
```

```
        end
```

```
    else
```

```
        if (PRE == 0)
```

```
            begin
```

```
                Q = 1;
```

```
                Qb = 0;
```

```
            end
```

```
        else
```

```
            if ( J == 0 & K == 0 )
```

```
                begin
```

```
                    Q = Q;
```

```
                    Qb = ~Q;
```

```
                end
```

```
            else
```

```
                if ( J == 0 & K == 1 )
```

```
                    begin
```

```
                        Q = 0;
```

```
                        Qb = 1;
```

```
                    end
```

```
            else
```

```
                if ( J == 1 & K == 0 )
```

```
                    begin
```

```
                        Q = 1;
```

```
                        Qb = 0;
```

```
end  
else  
  if ( J == 1 & K == 1 )  
    begin  
      Q = ~Q;  
      Qb = ~Qb;  
    end  
  
end  
  
endmodule
```

Test-bench Code for D Flip-flop

```
module test_DFF( );  
reg D;  
reg clk;  
reg PRE;  
reg CLR;  
wire Q;  
wire Qb;  
  
    DFF FF1 (Q,Qb,D,clk,CLR,CLR);  
  
initial  
    begin  
        clk=0;  
        forever #10 clk = ~clk;  
    end  
initial  
    begin  
        CLR=1;PRE=1; D = 0; #20  
        CLR=0;#10  
        CLR=1; D = 1; #20;  
        D = 0; #20;  
        PRE=0;#20  
        PRE=1;#10  
        D = 1; #10  
        $finish;  
    end  
endmodule
```

Test-bench code for JK FF

```
module test_JKFF();  
reg J;  
reg K;  
reg clk;  
reg PRE;  
reg CLR;  
wire Q;  
wire Qb;  
  
    JKFF FF1 (Q,Qb,J,K,clk,CLR,PRE);  
  
initial  
    begin  
        clk = 0;  
        forever #10 clk = ~clk;  
    end  
initial  
    begin  
        CLR = 1; PRE = 1; J = 0; K = 0; #20  
        PRE = 0; #10  
        PRE = 1; J = 0; K = 1; #20;  
        J = 1; K = 0; #20  
        CLR = 0; #20  
        CLR = 1; J = 1; K = 1; #20;  
    $finish;  
end  
endmodule
```

MOD 6 counter Design Code

```
module counter_mod6 ( clk ,reset ,dout );

output [2:0] dout ;
reg [2:0] dout ;

input clk ;
input reset ;

initial dout = 0;

always @ (posedge (clk))
begin
if (reset)
dout <= 0;
else if (dout<5)
dout <= dout + 1;
else
dout <= 0;
end

endmodule
```

Testbench code

```
module test_counter_mod6 ();
reg clk ,reset ;
wire [2:0] dout;
counter_mod6 Counter1 ( clk ,reset ,dout ) ;
initial
begin
clk=0;
forever #10 clk = ~clk;
end
initial
begin
reset = 0;#150
reset = 1;#30
$finish;
end
endmodule
```

Experiment - 7

Design code for sequence generator

```
module sequence_gen(op,clk);

input clk;
output [3:0] op;
reg [3:0] op;
begin
    op[3:0] = 4'b1100 ;
end
always @( posedge clk)
    op <= {op[3]^op[1], op[3:1]};

endmodule
```

Testbench

```
module test_sequence_gen();
    reg clk;
    wire [3:0] op;

    sequence_gen SG1 (op,clk);

    initial
        begin
            clk=0;
            forever #10 clk = ~clk;
        end

    initial
        begin
            #200
            $finish;
        end
endmodule
```


Experiment – 8

HDL for Sequence Detector “1011” :

```
module seq_det (input clk, rst, Din, output reg Dout);
    reg [1:0] state;
    initial
    begin
        state <= 2'b00;
    end
    always @ (posedge clk, posedge rst)
    begin
        if (rst)
            state <= 2'b00;
        else begin
            case ({state, Din})
                3'b000: state <= 2'b00;
                3'b001: state <= 2'b01;
                3'b010: state <= 2'b10;
                3'b011: state <= 2'b01;
                3'b100: state <= 2'b10;
                3'b101: state <= 2'b11;
                3'b110: state <= 2'b10;
                3'b111: state <= 2'b01;
            endcase
        end
    end
end
```

```
        end
    end

    always @*
    begin
        Dout = (({state, Din}) == 3'b111) ? 1'b1 : 1'b0;
    end
endmodule
```

Test Bench :

```
module testbench ( );
reg clk, rst, Din;
wire Dout;
seq_det det1(clk, rst, Din, Dout);
initial
begin
    clk=0;
    forever #10 clk = ~clk;
end
initial
begin
    rst = 0;
    Din = 0; #20
    Din = 1; #20
    Din = 0; #20
end
```

Din = 1; #20

Din = 1; #20

Din = 0; #20

Din = 1; #20

Din = 1; #20

Din = 0; #20

Din = 0; #20

Din = 0; #20

Din = 1; #20

\$finish;

end