

16.8. R-C SERIES CIRCUIT

Fig. 16.15 shows a resistance of R ohms connected in series with a capacitor of C farad.
Let V = r.m.s. value of the applied voltage
 I = r.m.s. value of the circuit current

$$V_R = IR \quad \dots \text{where } V_R \text{ is in phase with } I$$

$$V_C = IX_C \quad \dots \text{where } V_C \text{ lags } I \text{ by } 90^\circ$$

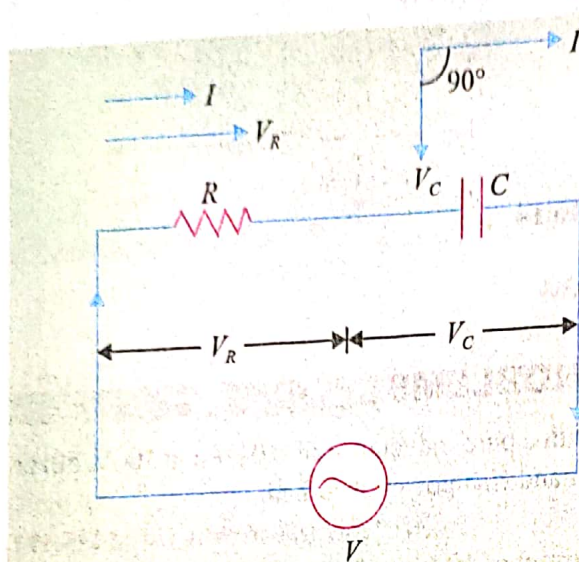


Fig. 16.15

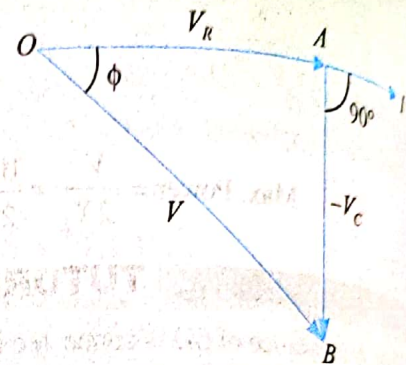


Fig. 16.16

The phasor diagram of the circuit is shown in Fig. 16.16. The supply voltage V is the phasor sum of $V_R (= IR)$ and $V_C (= IX_C)$ drops i.e.

$$V = \sqrt{V_R^2 + V_C^2} = \sqrt{(IR)^2 + (-IX_C)^2} = I \sqrt{R^2 + X_C^2}$$

$$I = \frac{V}{\sqrt{R^2 + X_C^2}}$$

The quantity $\sqrt{R^2 + X_C^2}$ offers opposition to current flow and is called *impedance* of the circuit.

$$I = V/Z \quad \text{where } Z = \sqrt{R^2 + X_C^2}$$

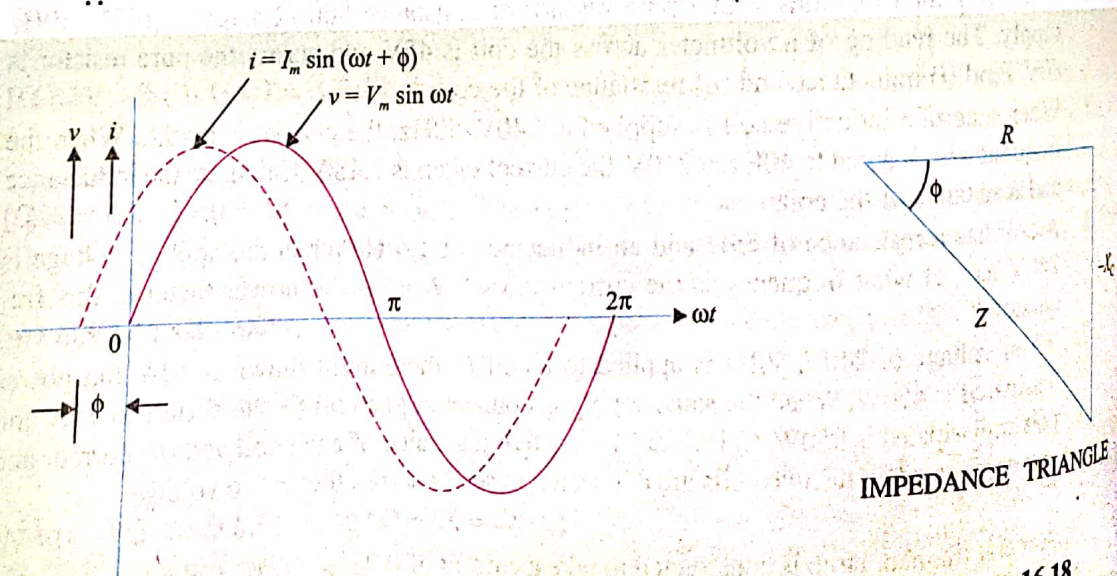


Fig. 16.17

Fig. 16.18

It is clear from the phasor diagram that circuit current I leads the applied voltage V by ϕ where :

$$\tan \phi = -\frac{V_C}{V_R} = -\frac{IX_C}{IR} = -\frac{X_C}{R}$$

Since current is taken as the reference phasor, negative phase angle implies that voltage lags behind the current. This is the same thing as current leads the voltage [See Fig. 16.17].

Power. The equations for voltage and current are :

$$v = V_m \sin \omega t$$

$$i = I_m \sin (\omega t + \phi)$$

Average power,

$$P = \text{Average of } vi$$

$$= VI \cos \phi$$

[By same way as in Art. 16.1]

Alternatively

$$P = \text{Power in } R + \text{Power in } C$$

$$= I^2 R + 0$$

$$= IR \times I = IR \times \frac{V}{Z} = VI \times \frac{R}{Z} = VI \cos \phi$$

Example 16.17. A capacitor of capacitance $79.5 \mu\text{F}$ is connected in series with a non-inductive resistance of 30Ω across 100 V , 50 Hz supply. Find (i) impedance (ii) current (iii) phase angle and (iv) equation for the instantaneous value of current.

Solution.

$$(i) \quad X_C = \frac{1}{2\pi fC} = \frac{10^6}{2\pi \times 50 \times 79.5} = 40\Omega$$

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{30^2 + 40^2} = 50\Omega$$

$$(ii) \quad I = V/Z = 100/50 = 2\text{A}$$

$$(iii) \quad \phi = \tan^{-1} X_C/R = \tan^{-1} 40/30 = 53^\circ \text{ lead}$$

$$(iv) \quad I_m = 2 \times \sqrt{2} = 2.828 \text{ A}; \omega = 2\pi f = 2\pi \times 50 = 314 \text{ rad s}^{-1}$$

$$\therefore i = 2.828 \sin (314 t + 53^\circ) \text{ Ans.}$$

Example 16.18. A capacitor and resistor are connected in series across a 120 V , 50 Hz supply. The circuit draws a current of 1.144 A . If power loss in the circuit is 130.8 W , find the values of resistance and capacitance.

Solution. Power loss occurs in resistance only as capacitor consumes no power.

$$P = I^2 R$$

$$\therefore R = P/I^2 = 130.8/(1.144)^2 = 100\Omega$$

$$Z = V/I = 120/1.144 = 104.91 \Omega$$

$$X_C = \sqrt{Z^2 - R^2} = \sqrt{(104.9)^2 - (100)^2} = 31.7\Omega$$

$$\therefore C = \frac{1}{2\pi fX_C} = \frac{1}{2\pi \times 50 \times 31.7} = 100 \times 10^{-6} \text{ F}$$

Example 16.19. A resistor R in series with a capacitor C is connected to 50 Hz , 240 V supply. Find the value of C so that R absorbs 300 W at 100 V . Find also the maximum charge and maximum energy stored in C .

Solution.

R absorbs 300W when connected to 100V so that $R = V^2/P = 100^2/300 = 100/3\Omega$

Now,

$$I^2 R = 3000W \quad \therefore I = \sqrt{300 \times 3/100} = 3A$$

$$Z = V/I = 240/3 = 80\Omega$$

$$X_C = \sqrt{Z^2 - R^2} = \sqrt{80^2 - (100/3)^2} = 72.7\Omega$$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \times 50 \times 72.7} = 43.7 \times 10^{-6} F$$

$$Q_{\max} = CV_{\max} = (43.7 \times 10^{-6}) \times 240 \sqrt{2} = 0.0148C$$

$$E = \frac{1}{2} CV_{\max}^2 = \frac{1}{2} \times (43.7 \times 10^{-6}) \times (240 \times \sqrt{2})^2 = 2.5 J$$

Example 16.20. A 10Ω resistor and $400\mu F$ capacitor are connected in series to a sinusoidal supply. The circuit current is 5A. Calculate the supply frequency and phase angle between the current and voltage.

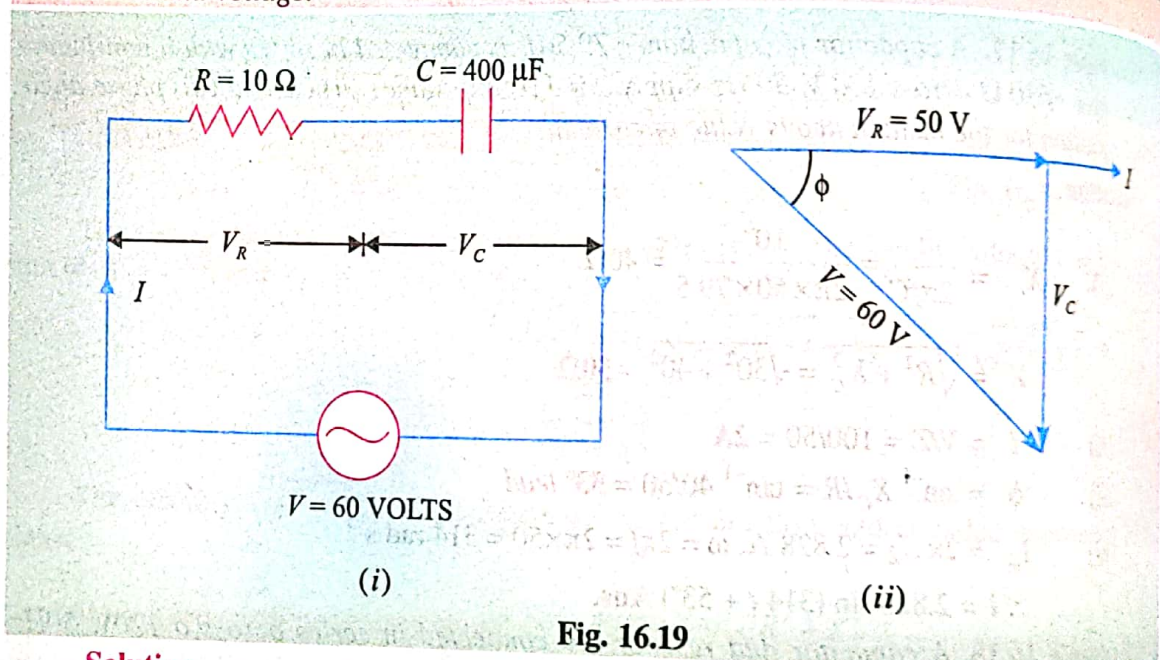


Fig. 16.19

Solution.

$$V_R = IR = 5 \times 10 = 50V$$

$$V_C = \sqrt{V^2 - V_R^2} = \sqrt{60^2 - 50^2} = 33.17 V$$

$$X_C = V_C/I = 33.17/5 = 6.634\Omega$$

$$f = \frac{1}{2\pi C X_C} = \frac{10^6}{2\pi \times 400 \times 6.634} = 60 \text{ Hz}$$

$$\phi = \tan^{-1} V_C/V_R = \tan^{-1} 33.17/50 = 33.6^\circ \text{ lead}$$

Example 16.21. Calculate the capacitance of a condenser to be connected in series with 100V, 80W lamp to enable it to be used on a 200V, 50Hz supply. What is p.f. of the circuit?

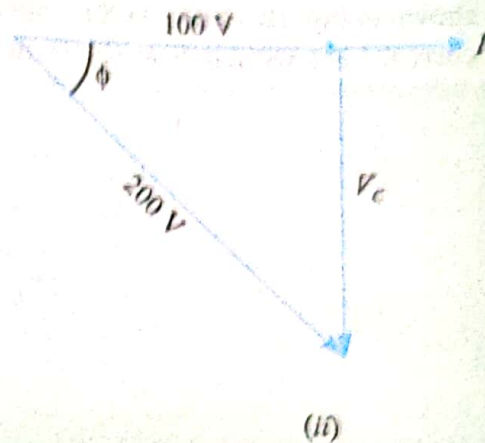
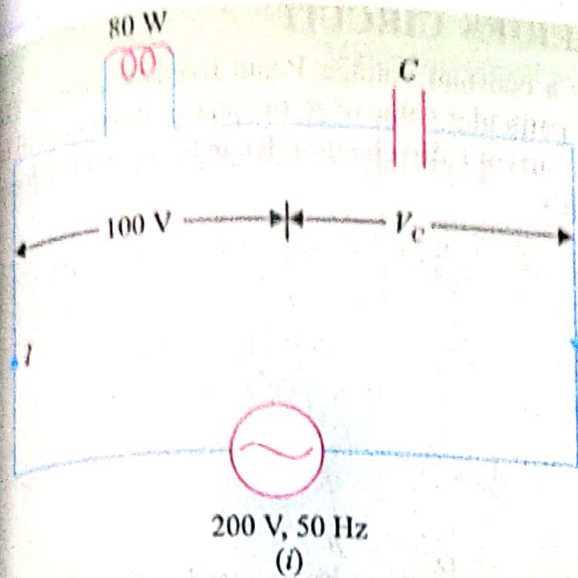


Fig. 16.20

Solution. The voltage across the bulb (pure resistance) should remain 100V for its proper operation. Fig. 16.20 (i) shows the required condenser of C farad in series with the lamp. The phasor diagram of the circuit is shown in Fig. 16.20 (ii).

Rated current of bulb, $I = 80/100 = 0.8 \text{ A}$

$$V_C = \sqrt{200^2 - 100^2} = 173.2 \text{ V}$$

$$X_C = V_C/I = 173.2/0.8 = 216.5 \Omega$$

$$\therefore C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \times 50 \times 216.5} = 14.7 \times 10^{-6} \text{ F}$$

$$\text{Circuit p.f.} = \cos \phi = V_R/V = 100/200 = 0.5 \text{ lead}$$

Example 16.22. A load consisting of a capacitor in series with a resistor has an impedance of 50Ω and power factor 0.707 leading. The load is connected in series with a 40Ω resistor across an a.c. supply and the resulting current is 3A. Determine the supply voltage and the overall phase angle.

Solution.

$$R_L = Z_L \cos \phi = 50 \cos 45^\circ = 35.35 \Omega$$

$$X_C = Z_L \sin \phi = 50 \sin 45^\circ = 35.35 \Omega$$

$$R_T = R + R_L = 40 + 35.35 = 75.35 \Omega$$

$$Z = \sqrt{(75.35)^2 + (35.35)^2} = 83.23 \Omega$$

$$V = IZ = 3 \times 83.23 = 250 \text{ V}$$

$$\phi = \tan^{-1} X_C/R_T = \tan^{-1} 35.35/75.35 = 25.17^\circ \text{ lead}$$

TUTORIAL PROBLEMS

1. A circuit when connected to 200V, 50Hz mains takes a current of 10A, leading the voltage by one-twelfth of time period. Calculate (i) resistance (ii) capacitive reactance and (iii) capacitance of the circuit. [(i) 17.32 Ω (ii) 10 Ω (iii) $318 \times 10^{-6} \text{ F}$]
2. A resistor R in series with a capacitance C is connected to a 50 Hz, 240V supply. Find the value of C so that R absorbs 300W at 100V. Find also maximum charge and the maximum stored energy in C . [44 μF ; 0.0135C; 2.1J]
3. A circuit has a fixed resistance of 2Ω and a capacitive reactance of 10Ω in series with a resistor R across 100V constant frequency mains. For what value of R is the power consumed in it a maximum? [10.2 Ω]