

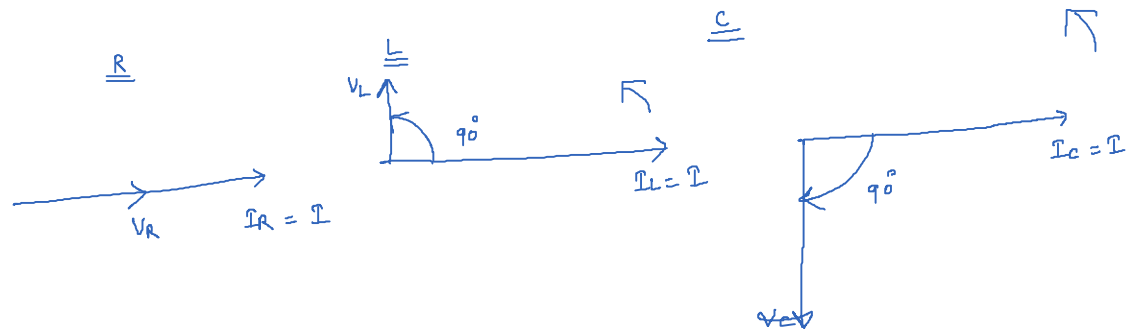


Series R-L-C Circuit

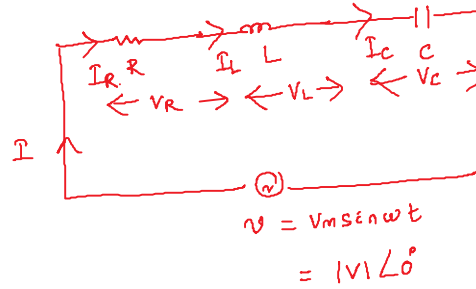

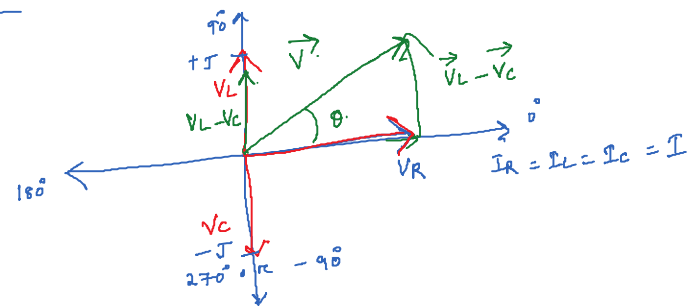Case 1
 $X_L > X_C$
 $I X_L > I X_C$
 $V_L > V_C$



$$\vec{V} = \vec{V}_R + j(\vec{V}_L - \vec{V}_C)$$

$$I Z = I R + j(I X_L - I X_C)$$

$$Z = R + j(X_L - X_C) \quad (1)$$

$$= |Z| \angle \theta$$

$$= \sqrt{R^2 + (X_L - X_C)^2} \angle \tan^{-1} \left(\frac{X_L - X_C}{R} \right) \quad (2)$$

$$I = \frac{V}{Z} = \frac{|V| \angle 0^\circ}{|Z| \angle \theta} = \frac{|V|}{|Z|} \angle -\theta \quad (3)$$

$$v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t - \theta)$$

$$I = \frac{V_m}{\sqrt{R^2 + (X_L - X_C)^2}}$$


$$\theta = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) \quad (4)$$

Case II

$$X_L < X_C$$

$$I_{X_L} < I_{X_C}$$

$$V_L < V_C$$

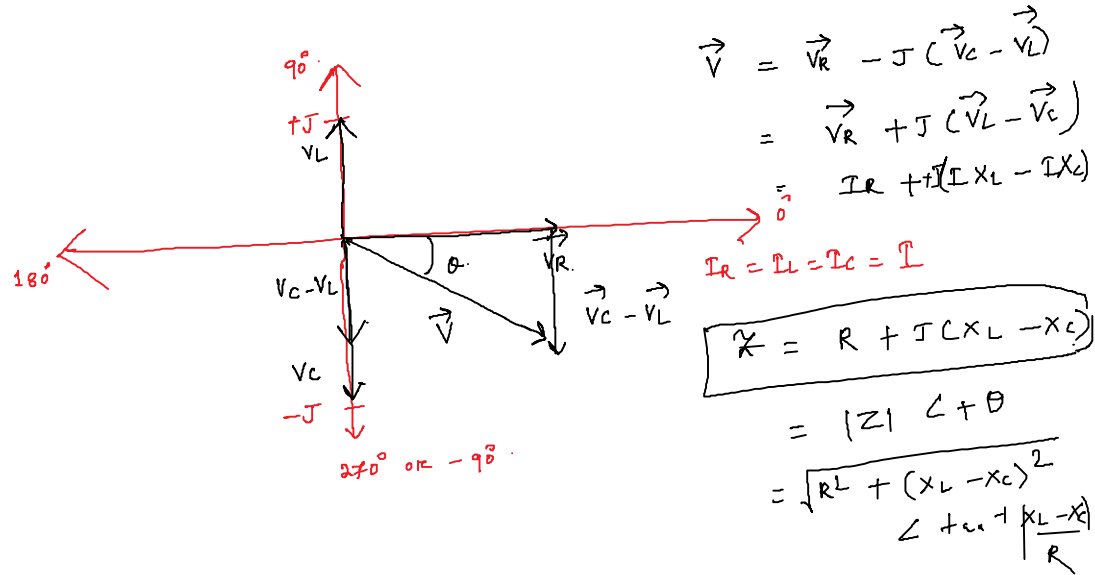


(1) If $X_L > X_C$ the circuit is inductive. θ is -ve, behavior as purely cap.

(2) If $X_C > X_L$ the circuit is capacitive. θ is +ve, behavior as purely cap.

(3) If $X_C = X_L$ the circuit is resistive. $\theta = 0^\circ$, behavior as purely resistive.

Q. 1.

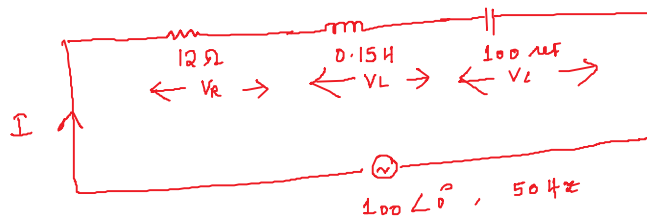

Calculate

a) Z

(2)

P_f

... Dissipate

Calculate

- a) Z (e) P_f
 (b) I (f) Apparent power.
 (c) phase angle (g) Avg power
 (d) V_R, V_L, V_C (h) phasor diagram

(a)

$$R = 12 \Omega$$

$$X_L = 2 \times 3.142 \times 50 \times 0.15$$

$$= 47.1 \Omega$$

$$X_C = \frac{1}{2 \pi f C} = 31.8 \Omega$$

$$Z = 12 + j(47.1 - 31.8)$$

$$= \frac{12 + j15.3}{17.4 \angle 51.9^\circ}$$

(b)

$$I = \frac{V}{Z} = \frac{100 \angle 0^\circ}{17.4 \angle 51.9^\circ}$$

$$= 5.15 \angle -51.9^\circ$$

(c)

$$\phi = -51.9^\circ$$

(d)

$$V_R = IR = 5.15 \times 12 = 61.8 \text{ V}$$

$$V_L = IX_L = 5.15 \times 47.1 = 242.5 \text{ V}$$

$$V_C = IX_C = 5.15 \times 31.8 = 163.8 \text{ V}$$

(e)

$$P_f = \cos(51.9^\circ) = 0.617 \text{ lagging}$$

(f)

$$P_{app} = V_{rms} I_{rms} = 100 \times 5.15 = 515 \text{ VA}$$


(g)

$$P_{avg} = VI \cos \theta$$

$$= 100 \times 5.15 \times 0.617 = 317.75 \text{ W}$$

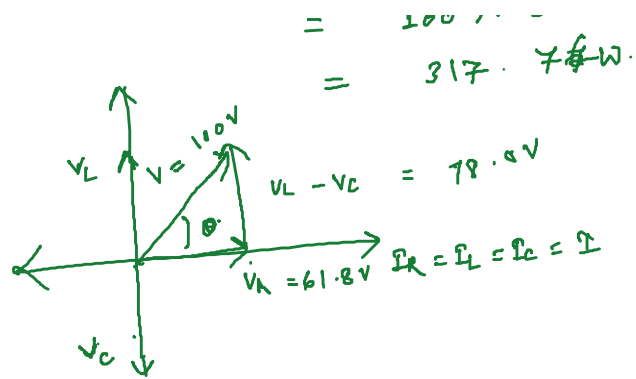178.6)

$$\sqrt{(61.8)^2 + (78.6)^2} = 100 \text{ V}$$




Q.2.

- $R = 100 \Omega$, $L = 0.2 \text{ H}$, $C = 20 \mu\text{F}$
 $V = 240 \angle 0^\circ$
 Calculate
 (a) Z (b) I
 (c) pf (d) V_R, V_L, V_C
 (e) power consumed
 (f) phasor diagram

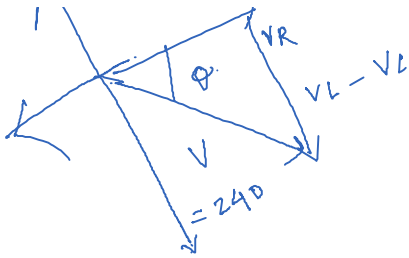a) $Z = R + j(X_L - X_C)$
 $= 100 + j(62.8 - 159)$
 $= 139 \angle -43.9^\circ$
 b) $I = \frac{V}{Z} = \frac{240 \angle 0^\circ}{139 \angle -43.9^\circ} = 1.725 \angle 43.9^\circ$
 (c) $\text{pf} = 0.72 \text{ leading}$
 (d) $V_R = IR = 1.725 \times 100 \angle 43.9^\circ = 172.5 \angle 43.9^\circ$
 (e) $V_L = I X_L = 1.725 \angle 43.9^\circ \times 62.8 \angle 90^\circ = 108.5 \angle 133.9^\circ$





$$= 108.5 \angle 133.7$$

$$(f) \quad V_C = I X_C = \frac{1.725 \angle 43.9^\circ}{\times 159 \angle -90^\circ} \\ = 274.2 \angle \text{---}$$

$$(g) \quad P = I_{rms}^2 R \\ = [1.725]^2 \times 10 = 298 \text{ W}$$