

OPAMP

①

It is a - Multistage
- very high gain
- direct coupled
- feedback Amp.

It has - high i/p impedance
- low o/p impedance
- Operated betⁿ 0Hz to 1MHz
- can amplify both dc & ac.


It performs mathematical operations —
Summation, Subtraction, Multiplication,
Differentiation, Integration.

Ideal OPAMP characteristics


- Input Impedance = ∞
- Output Impedance = 0
- Voltage Gain = $-\infty$
- Bandwidth = ∞
- Slew Rate = ∞ (max. o/p changes with unit time)
- CMRR = ∞ (free from undesired signal)
- Offset voltage = 0 (o/p is zero when i/p is zero)

OPAMP (Integrated IC)


Typical OPAMP 74LS741

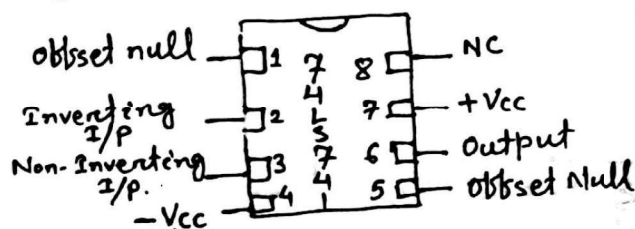

[Pin Diagram]

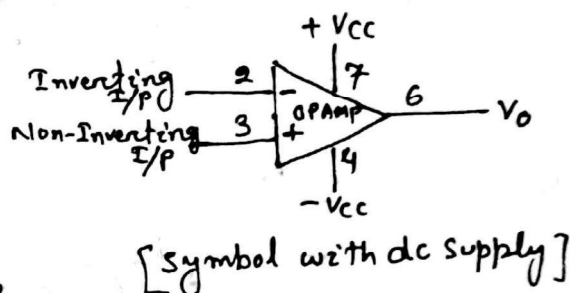


AC Equivalent Circuit of OPAMP

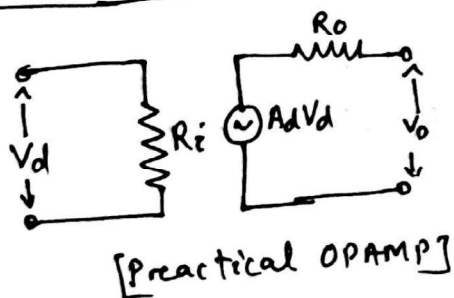

[Practical OPAMP]

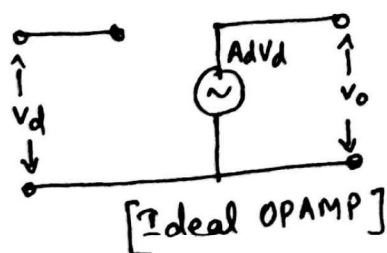- Very high input impedance R_i
- o/p voltage is amplified gain time to the i/p voltage.
- Output Impedance is very low R_o .



[Ideal OPAMP]

- Input Impedance is ∞ (so open)
- Output Impedance is 0 (so short)
- Voltage gain is ∞ .

OP-AMP Configuration ← operates for ac & dc

Open Loop
(No connection betⁿ o/p to i/p)


- Differential amp
- Inverting amp
- Non-inverting amp

Closed Loop
(Connection betⁿ o/p to i/p)


Positive feedback

Negative feedback

Differential Amp

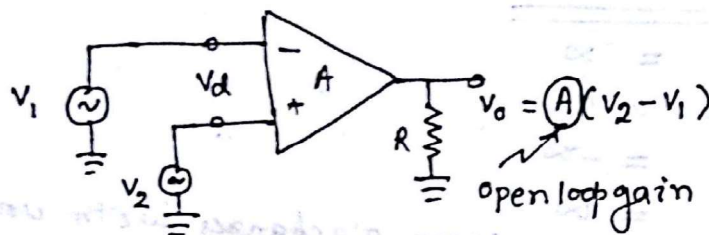


Inverting Amp

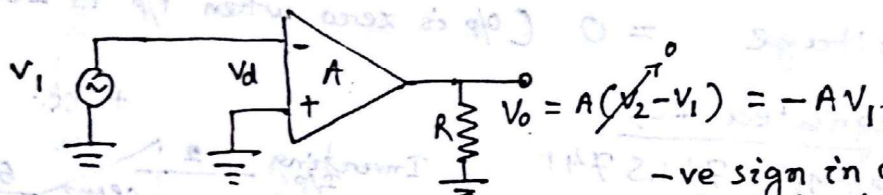


-ve sign in o/p shows 180° out of phase.

Non-Inverting Amp

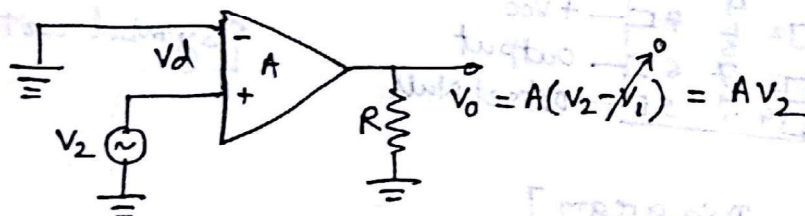


Note. Due to open loop gain is very high, when the i/p signal is slightly greater than o/p is driven to saturation level.

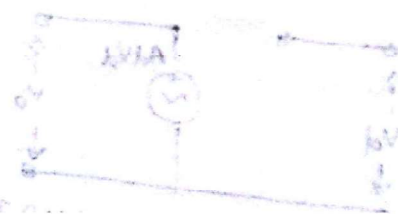- which creates distortion in o/p
- So for linear operation the gain should be controlled which can be achieved by feedback or closed loop config.



Inverting Amp

(3)

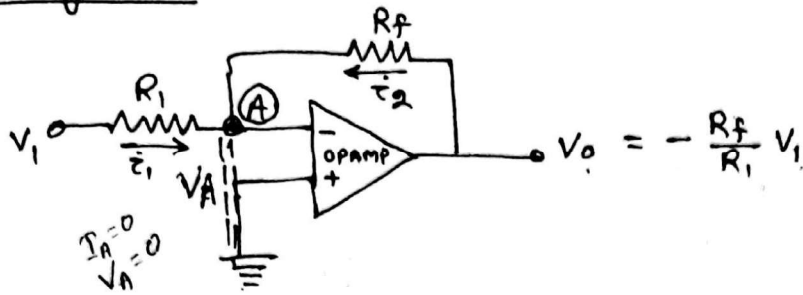


- The feedback resistor R_f feeds some portion of o/p to the i/p which employs negative feedback.
- The i/p current and feedback current are algebraically sum at point "A".
- When $i_1 = i_2$ then at point "A" the sum of current is equal to zero.
- So the voltage from point "A" that is " $V_A = 0V$ ", is termed as Virtual Ground (~~not actual ground~~).
- Due to the virtual ground the current goes through R_1 & R_f that is $i_1 = i_2 = i$

$$\text{So } i = \frac{V_1}{R_1} = -\frac{V_o}{R_f}$$

$$\Rightarrow \frac{V_o}{V_1} = \boxed{-\frac{R_f}{R_1} = A}$$

Non-Inverting Amp

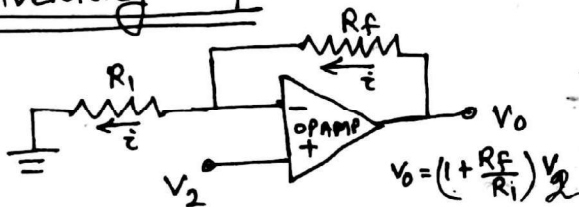

- Due to the virtual short betⁿ two terminals the voltage across R_1 is i/p voltage V_2 .

- The V_o applied across the series combination of $R_1 + R_f$.


$$\therefore V_2 = i R_1$$

$$V_o = i(R_1 + R_f)$$


$$\text{So } A = \frac{V_o}{V_2} = \frac{i(R_1 + R_f)}{i R_1} = \left(1 + \frac{R_f}{R_1}\right)$$

$$\Rightarrow \boxed{A = \left(1 + \frac{R_f}{R_1}\right)}$$

Unit Follower

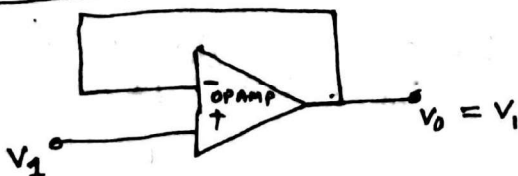

Summing Amplifier

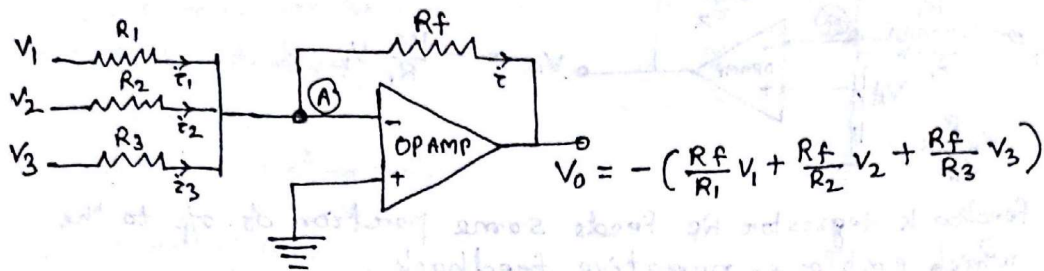


Here $i_1 = \frac{V_1}{R_1}$, $i_2 = \frac{V_2}{R_2}$, $i_3 = \frac{V_3}{R_3}$ & $i = -\frac{V_0}{R_f}$

At point "A"


$$i_1 + i_2 + i_3 - i = 0$$

$$\Rightarrow V_0 = -\frac{R_f}{R} (V_1 + V_2 + V_3) \quad \text{if } R_1 = R_2 = R_3 = R$$


Integrator

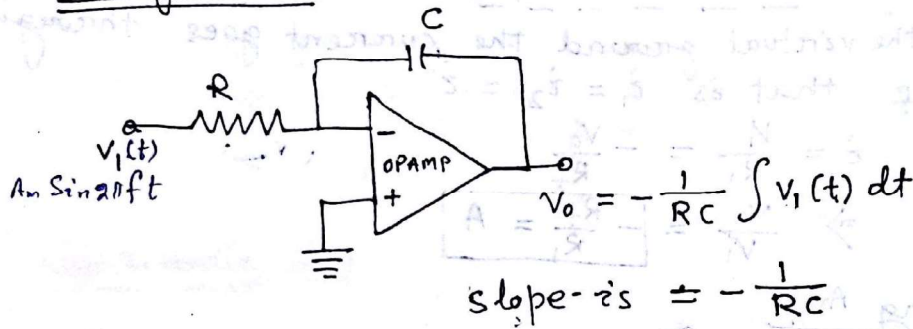


Summing Integrator

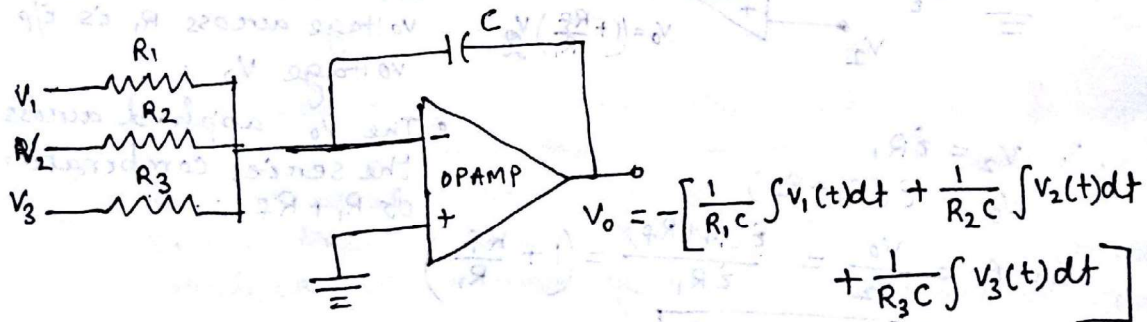

Differentiator

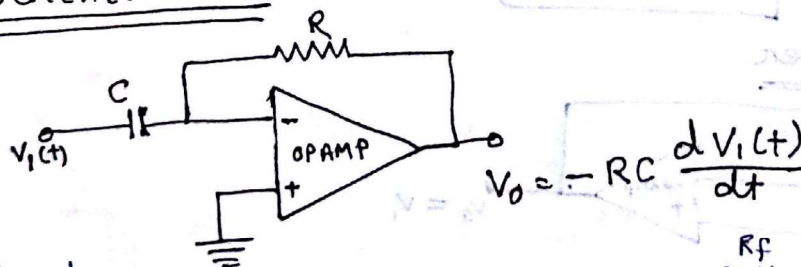

Subtractor

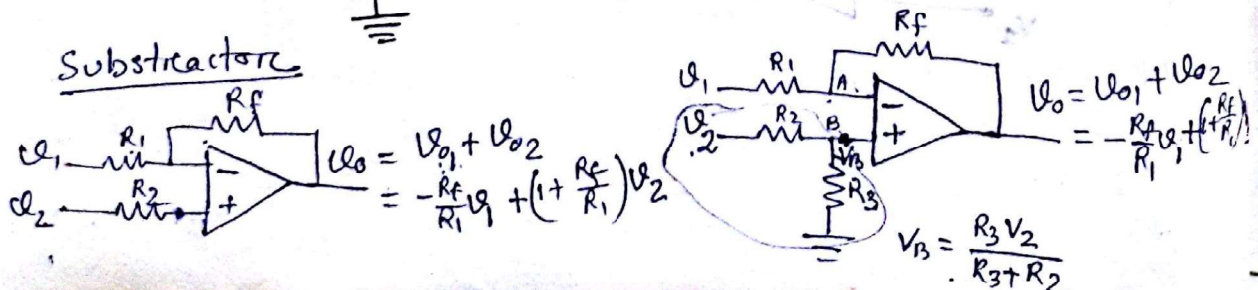

OP-AMP Parameters

(5)

① I/P & O/P OFFSET Voltage -

- In a device when input is zero output should be zero, but in practical OP-AMP there will be some output voltage, called as O/P offset voltage. Which is due to manufacturing defect.
- So a small amount of voltage is applied ~~to~~ ^{or to cancel} externally to nullify the output offset voltage is known as input offset voltage. Typical range is 1mV to 5mV.

② Slew Rate -

It is the maximum rate of change of output voltage per unit time and expressed in volts per microseconds.


$$SR = \left. \frac{dV_o}{dt} \right|_{\max} \text{ V}/\mu\text{s}$$

It indicates the change in output in response to change in input frequency.

③ CMRR (Common Mode Rejection Ratio)

OP-AMP has two type operation

(a) Differential operation

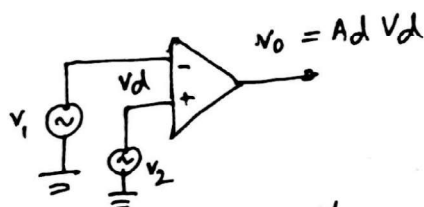


$$V_o = A_d V_d$$

$$\text{where } V_d = V_2 - V_1$$

A_d = Differential gain

$$\text{So } \boxed{A_d = \frac{V_o}{V_d}}$$

(b) Common Mode operation

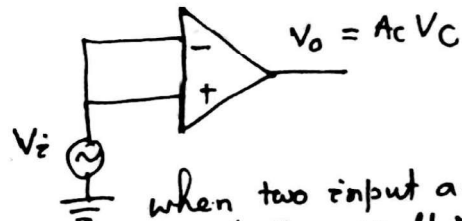

$$V_o = A_c V_c$$

When two input are equal the resulting output should be zero. It has no meaning.

$$\text{So } V_c = \frac{1}{2} (V_{i1} + V_{i2})$$

A_c = Common mode Gain

$$\text{So } \boxed{A_c = \frac{V_o}{V_c}}$$

The ratio of differential gain (open loop gain) and the common mode gain is called CMRR.


$$\boxed{CMRR = \frac{A_d}{A_c}}$$

$$\boxed{CMRR \text{ in dB} = 20 \log_{10} \frac{A_d}{A_c}}$$

V_B

OP-AMP AS A Differential Amp

6

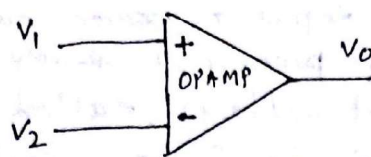

Actually $V_0 = A_d (V_1 - V_2)$

where $A_d = \text{Gain}$

- But when $V_1 = V_2$ then $V_0 = 0$ has no meaning. So practically the o/p depends on both —

- (a) difference signal V_d
- (b) common mode signal V_c

where $V_d = V_1 - V_2$

$$V_c = \frac{1}{2} (V_1 + V_2)$$

• So output is defined by \longleftrightarrow

$$V_0 = A_d V_d + A_c V_c$$

where $A_d = \text{Differential Gain}$
 $A_c = \text{Common mode Gain}$

Measure of A_d

Set $V_1 = -V_2 = 0.5V$

So $V_d = 1V$ & $V_c = 0$

\therefore measured o/p is the differential gain " A_d ".

Measure of A_c

Set $V_1 = V_2 = 1V$

So $V_d = 0V$, $V_c = 1V$

\therefore Measured o/p is the common mode gain " A_c ".

Note
 \therefore The ratio of A_d & A_c is called CMRR gives the figure of merit of Amplifier.

$$CMRR = \rho = \left| \frac{A_d}{A_c} \right|$$

other form

$$V_0 = A_d V_d + A_c V_c$$

$$= A_d V_d \left(1 + \frac{A_c V_c}{A_d V_d} \right)$$

$$\Rightarrow V_0 = A_d V_d \left(1 + \frac{1}{\rho} \frac{V_c}{V_d} \right)$$