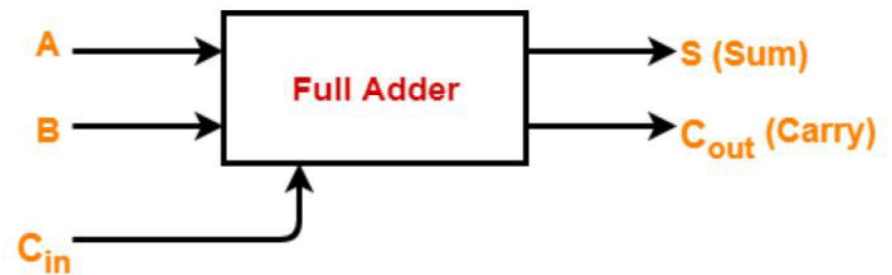


ADDERS

- Full Adder (FA)-
- It is used for the purpose of adding three single bit numbers.
- It contains 3 inputs and 2 outputs (sum and carry).



Step-01:

Identify the input and output variables-

Input variables = A, B, C_{in} (either 0 or 1)

Output variables = S, C_{out} where
S = Sum and C_{out} = Carry

Step-02:

Inputs			Outputs	
A	B	C _{in}	C _{out} (Carry)	S (Sum)
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Step-03: K-maps

		BC_{in}			
A	\bar{A}	$\bar{B}\bar{C}_{in}$	$\bar{B}C_{in}$	BC_{in}	$B\bar{C}_{in}$
	A	$\bar{B}\bar{C}_{in}$	$\bar{B}C_{in}$	BC_{in}	$B\bar{C}_{in}$
			1		1
		1		1	

$$S = A \oplus B \oplus C_{in}$$


For C_{in} :

		BC_{in}			
A	\bar{A}	$\bar{B}\bar{C}_{in}$	$\bar{B}C_{in}$	BC_{in}	$B\bar{C}_{in}$
	A	$\bar{B}\bar{C}_{in}$	$\bar{B}C_{in}$	BC_{in}	$B\bar{C}_{in}$
				1	
			1	1	1

Full Adder K maps & Boolean Expression

$$C_{out} = AB + BC_{in} + C_{in}A$$

Step-04: Logic Diagram

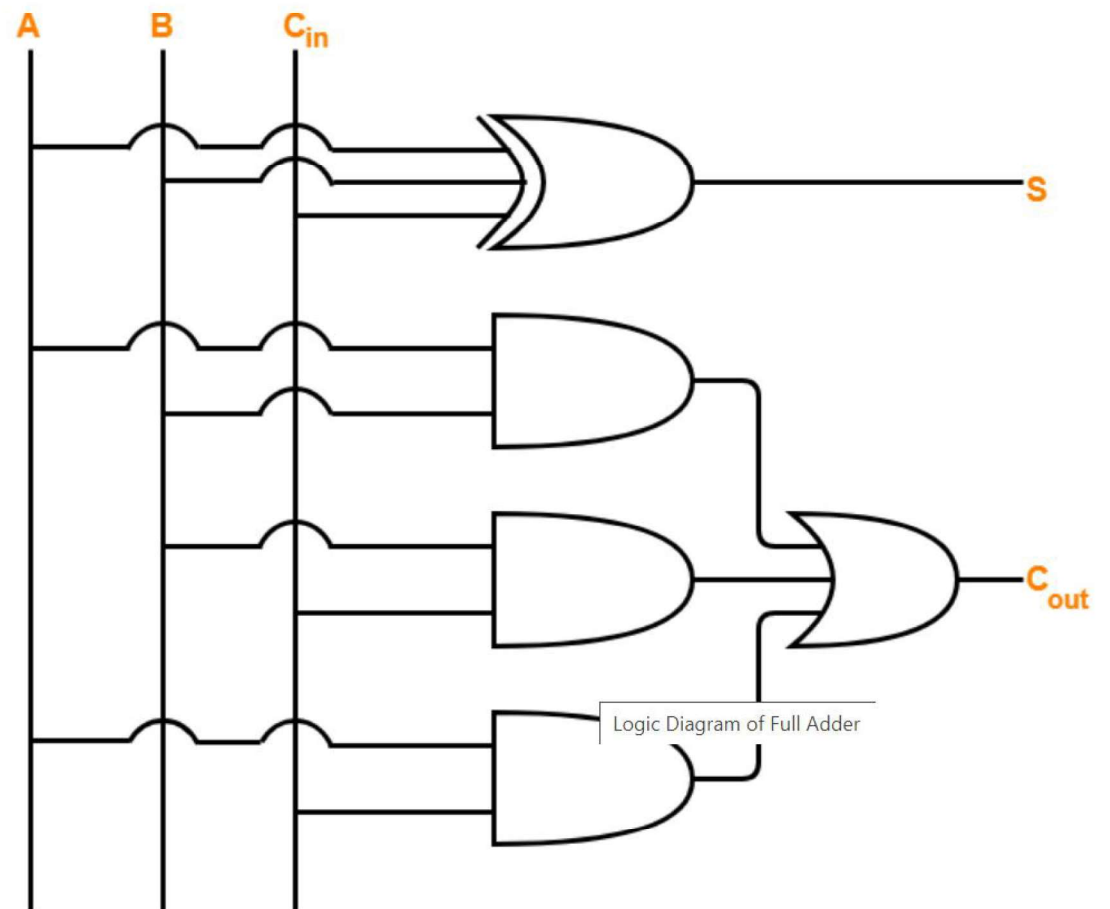

FA using HA

