



SCHOOL OF ELECTRICAL ENGINEERING, KIIT UNIVERSITY  
MID-SEMESTER EXAMINATION, 2016

SEMESTER: 1<sup>ST</sup> ; BRANCH: ALL


SUBJECT: BASIC ELECTRICAL ENGINEERING, (CODE: EE1003)

Maximum Marks: 25


Time Allowed : 2 Hrs.

**Instructions:** Answer any five questions including Q. No. 1. The figures in right hand margin indicate full marks. Candidates are required to give answers of all parts of a question at one place only in their own words.

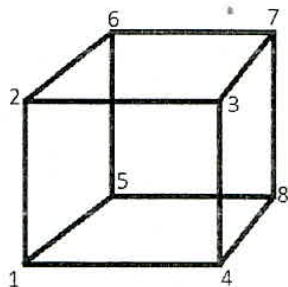- Q.1
- a) The current through a wire depends on time  $I = (2 + 3t)A$ . Calculate the charge crossed through a cross section of the wire in first 10 second. [1]
  - b) Why bulb of lesser wattage in series combination will shine more? [1]
  - c) What is the purpose of using fuse in an electrical installation? [1]
  - d) State Norton's Theorem. [1]
  - e) If an ideal voltage source and an ideal current source are connected in parallel, then the combination has exactly the same properties as a voltage source alone. Justify it. [1]
- Q2. Find the resistance of the wire frame shaped as a cube when measured between the points 1 and 4. The resistance of each edge is R ohm. [5]



- Q3 [5]

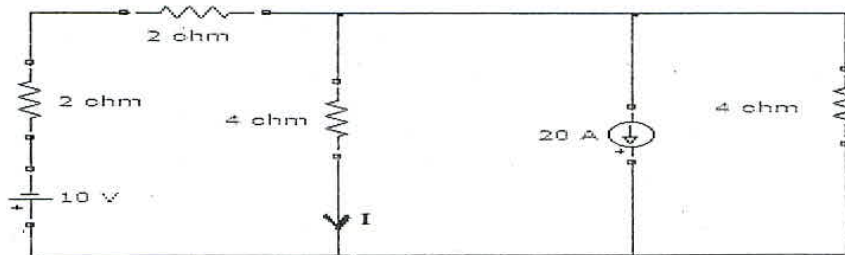


[PTO]

Find I by using superposition theorem.


Q4

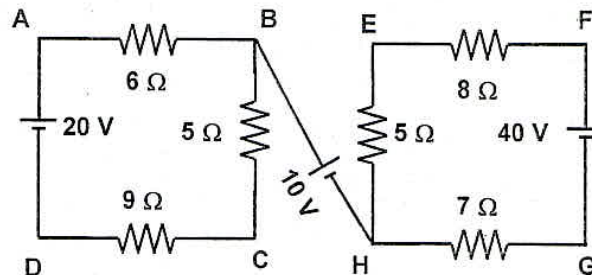- a) Resistances  $R$ ,  $2R$ ,  $4R$ ,  $8R$ ....infinity are connected in parallel. What is the equivalent resistance? [2]
- b) For the circuit shown as below, find  $V_{CE}$  and  $V_{AG}$ . [3]



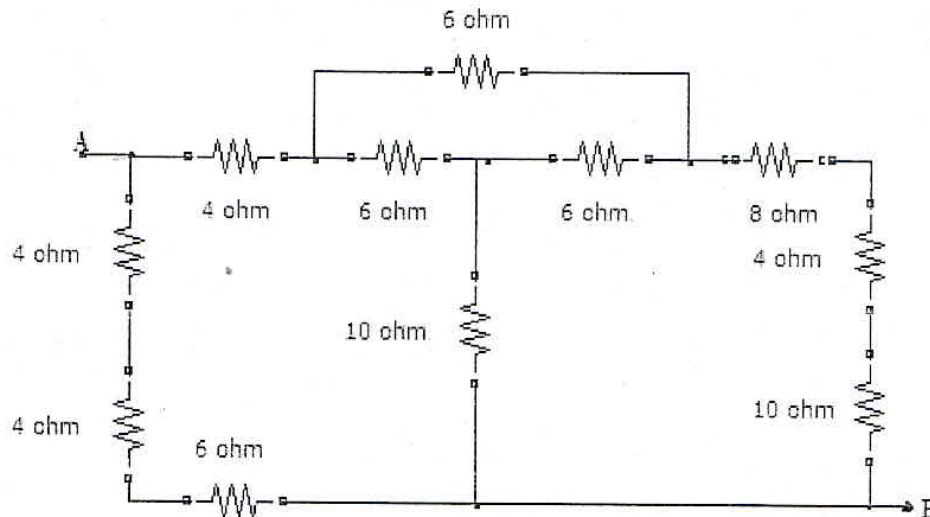Q5

Using star/delta transformations for the given circuit, find the equivalent resistance between terminals AB. [5]



Q6.

- a) Explain various types of wiring circuits and describe different methods of house wiring. [2]
- b) With neat sketch show the general layout of a power system and explain each component of the system. [3]

\*\*\*\*\*THE END\*\*\*\*\*