

SOLUTION

AUTUMN MID-SEMESTER EXAMINATION-2015

DIGITAL ELECTRONIC CIRCUITS

[EC-2009]

1. a) BCD Subtraction: 476.7 - 297.8

[1]

$$\begin{array}{r}
 0100 \ 0111 \ 0110 \ . \ 0111 \\
 - 0010 \ 1001 \ 0111 \ . \ 1000 \\
 \hline
 0001 \ 1101 \ 1110 \ . \ 1111 \\
 - \quad \quad 0110 \ 0110 \ . \ 0110 \\
 \hline
 0001 \ 0111 \ 1000 \ . \ 1001
 \end{array}$$

b) 101010

[1]

Sign-Magnitude Form: **-10**

1's Complement Form: **-21**

2's Complement Form: **-22**

c) $U\bar{V} + UW + V\bar{W} = U + V\bar{W}$

[1]

$$\begin{aligned}
 \text{L.H.S: } & U\bar{V} + UW + V\bar{W} \\
 &= U(\bar{V} + W) + V\bar{W} \\
 &= U(\overline{V \cdot \bar{W}}) + V\bar{W} \\
 &= U + V\bar{W} = \text{R.H.S}
 \end{aligned}$$

[Since, $A + \bar{A} \cdot B = A + B$]

d) Advantage of **Look-Ahead Carry Adder** : **Faster, Less Propagation Delay(Ripple Delay)**

[1]

$$C_1 = P_0 C_0 + G_0$$

$$C_2 = P_1 P_0 C_0 + P_1 G_0 + G_1$$

$$C_3 = P_2 P_1 P_0 C_0 + P_2 P_1 G_0 + P_2 G_1 + G_2$$


$$C_4 = P_3 P_2 P_1 P_0 C_0 + P_3 P_2 P_1 G_0 + P_3 P_2 G_1 + P_3 G_2 + G_3$$

e) Half Subtractor using 2 to 4 Active High DECODER

[1]

$$\text{Difference} = \sum m(1, 2) = A \oplus B$$
 
$$\text{Borrow} = \sum m(1) = \bar{A} B$$




2. $F(P,Q,R,S) = \prod M(4, 6, 8, 9, 12, 13, 14) \cdot d(1, 3, 7)$ [POS Form]
 $= \sum m(0, 2, 5, 10, 11, 15) \cdot d(1, 3, 7)$ [SOP Form] [1]
 [SOP Form is for "NAND-NAND" Two-Level Universal gate implementation]

PQ \ RS	00	01	11	10
00	1	X	X	1
01		1	X	
11			1	
10			1	1

After K-MAP simplification:

$$F(P,Q,R,S) = \bar{P}\bar{Q} + \bar{P}S + \bar{Q}R + RS$$

[K-Map :2 Marks]

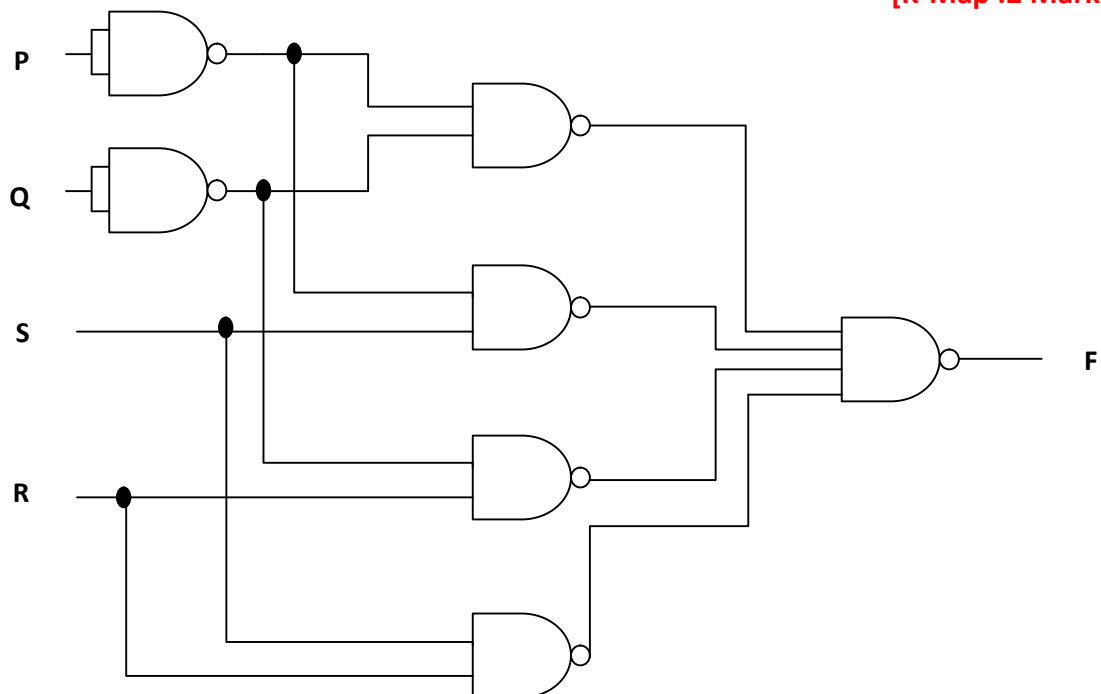

[NAND-NAND Circuit implementation 2 Marks]

3. a) $F(A,B,C,D) = \bar{A}B + BC + B\bar{D}$ [Ordinary SOP Form]


- MULTIPLEXER will implement Min-terms for the given input variables connected to its SELECT LINES A,B,C will be connected to S2,S1 and S0 respectively and D will be connected to input lines according to the requirement.
- Thus, for implementation using Decoder, Ordinary SOP has to be converted to Standard SOP Form.

$$F(A,B,C,D) = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + B\bar{C}\bar{A}\bar{B} + B\bar{C}\bar{A}B + B\bar{C}A\bar{B} + B\bar{C}AB + B\bar{D}\bar{A}\bar{C} + B\bar{D}\bar{A}C + B\bar{D}A\bar{C} + B\bar{D}AC$$

$$= m_4 + m_5 + m_6 + m_7 + m_6 + m_7 + m_{14} + m_{15} + m_4 + m_6 + m_{12} + m_{14}$$

$$= \sum m(4, 5, 6, 7, 12, 14, 15) \quad [1] + \text{Table } [2] + \text{circuit } [1]$$


S2S1S0	A	B	C	D	F	
000	0	0	0	0	0	F=0
	0	0	0	1	0	
001	0	0	1	0	0	F=0
	0	0	1	1	0	
010	0	1	0	0	1	F=1
	0	1	0	1	1	
011	0	1	1	0	1	F=1
	0	1	1	1	1	
100	1	0	0	0	0	F=0
	1	0	0	1	0	
101	1	0	1	0	0	F=0
	1	0	1	1	0	
110	1	1	0	0	1	F= \bar{D}
	1	1	0	1	0	
111	1	1	1	0	1	F=1
	1	1	1	1	1	

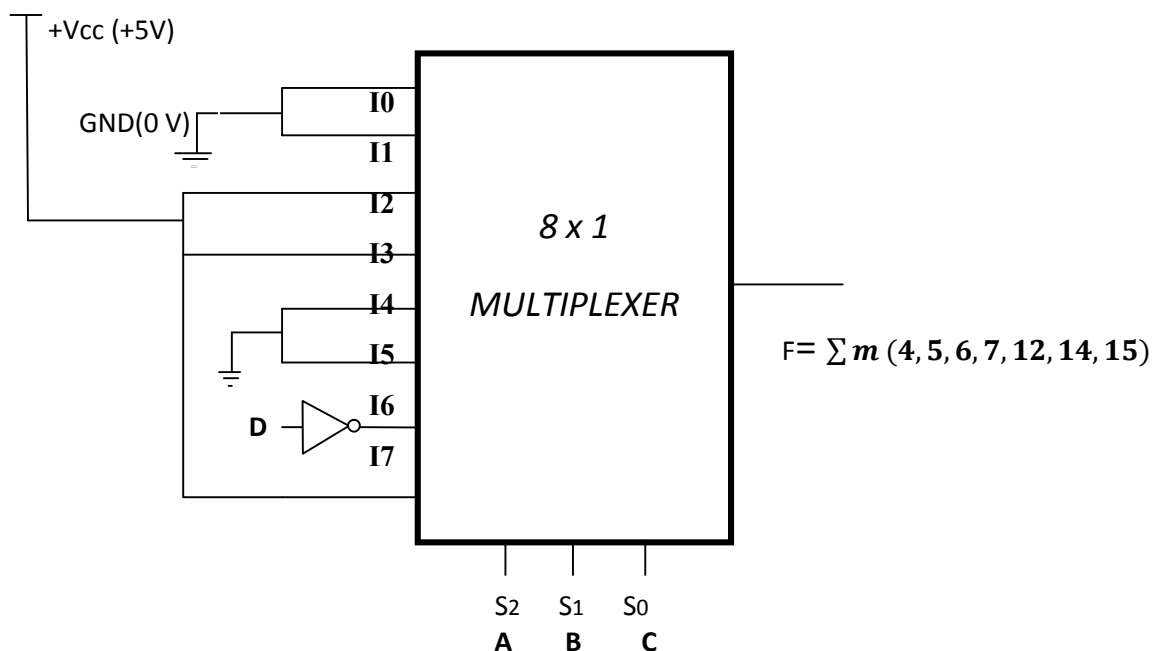

b) $F(A, B) = \overline{A \oplus B}$

$= \sum m(0, 3)$

[1]

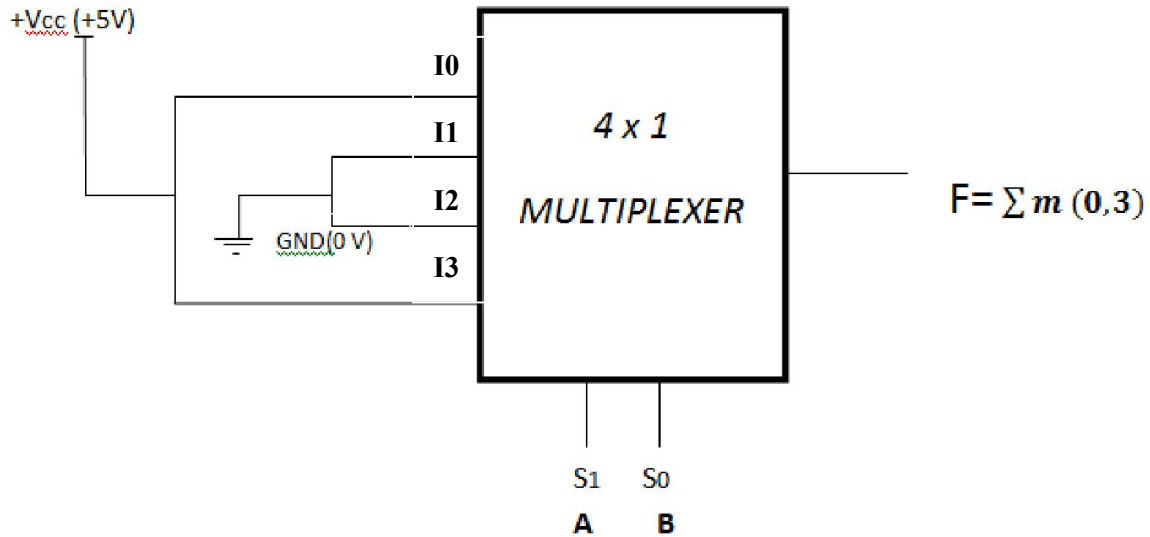

4. a)

[0.5]

FAN_1	FAN_2	FAN_3	ALARM
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0


$ALARM = \sum m(0, 1, 2, 4)$

[1]

$= \prod M(3, 5, 6, 7)$

- DECODER having ACTIVE LOW outputs will give MAX-TERMS

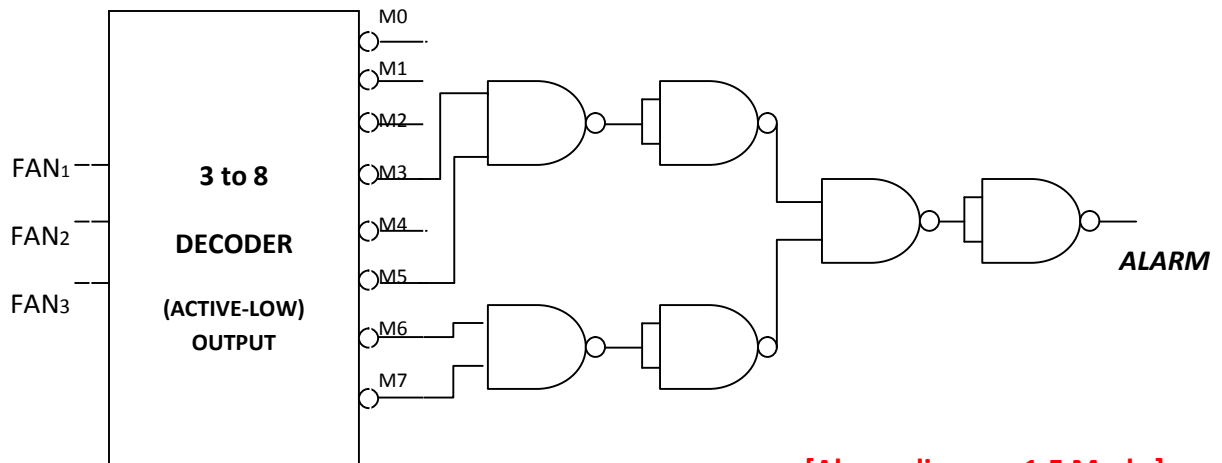- Implementation can be done by NAND gates, We need product of MAX-TERMS so each stage NAND gate has to be converted into AND gate so we get 4 stage logic. NAND-NAND-NAND-NAND , which will work like AND-AND \approx AND i.e Product of MAX-TERMS




[Above diagram 1.5 Marks]

b) **1 bit Magnitude Comparator:**

Explanation: [0.5 MARKS]

A	B	A<B	A=B	A>B
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0
Boolean Function: \rightarrow		$\sum m(1)$ $= \bar{A}B$	$\sum m(0,3)$ $= \bar{A}\bar{B} + AB$ $= A \odot B$	$\sum m(2)$ $= A\bar{B}$

 [0.5 Marks for Correct Expression above table]



[Implementation using Minimum 5 NAND Gates 1 Marks]

5. a) **2 bit Priority Encoder**; where the given order of the priorities for 4 inputs are $D_3 > D_2 > D_1 > D_0$.

[Table: 0.5]

D3	D2	D1	D0	A	B	V
0	0	0	0	x	x	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

A

[Each Corect expression A,B & V 1 Mark Each]

D ₃ D ₂ \ D ₁ D ₀	00	01	11	10
00	X	1	1	1
01		1	1	1
11		1	1	1
10		1	1	1

$$A = D_3 + D_2$$

B

D ₃ D ₂ \ D ₁ D ₀	00	01	11	10
00	X	1	1	
01	1	1	1	
11	1	1	1	
10		1	1	

$$B = D_3 + \overline{D_2} D_1$$

Valid :

$$V = D_3 + D_2 + D_1 + D_0$$

- Draw the logic diagram using basic gates for above simplified expressions. [0.5]

b) Received 7-bit Hamming code is '**1110100**' then find the 4-bit data word. (Even Parity) **[1]**

P1	P2	D3	P4	D5	D6	D7
1	1	1	0	1	0	0

$$c1 = p1 \oplus D3 \oplus D5 \oplus D7$$


$$c2 = p2 \oplus D3 \oplus D6 \oplus D7$$

$$c4 = p4 \oplus D5 \oplus D6 \oplus D7$$

C1	C2	C4
1	0	1

- Thus, D5 is in error; so instead of '1' it should be '0' (1 bit is in error)
- Correct 4 bit data word will be : **1000**

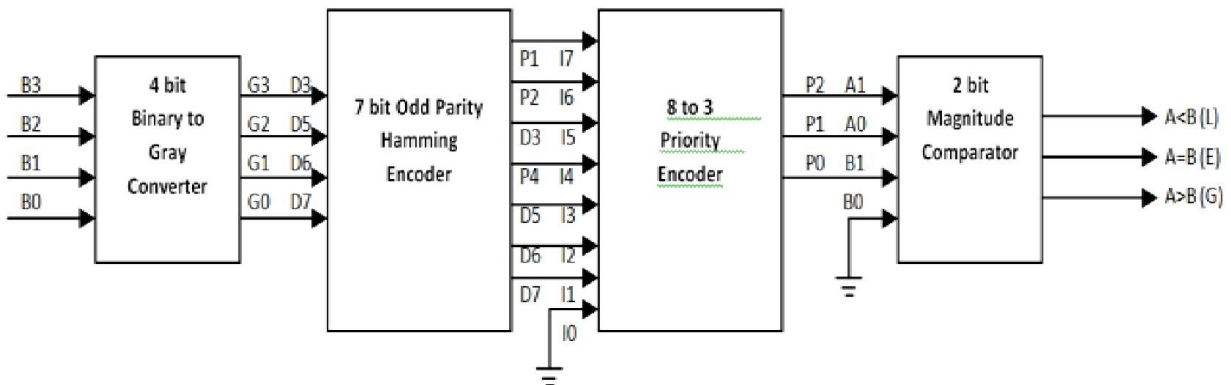6. a) **Each Correct Block Answer : 1 Mark each Block]**



1st Block:

Binary (input)				Gray (output)			
B3	B2	B1	B0	G3	G2	G1	G0
1	0	1	0	1	1	1	1

2nd Block:

Gray code = Data word (input)				Odd Hamming Code (Output)						
D3	D2	D1	D0	P1	P2	D3	P4	D5	D6	D7
1	1	1	1	0	0	1	0	1	1	1

3rd Block:


Odd Hamming Code = (I7 – I0) Input to Priority Encoder (input)							Priorities (Output)		
P1	P2	D3	P4	D5	D6	D7	P2	P1	P0
0	0	1	0	1	1	1	1	0	1

Note: D3 (data) is connected to I5 of Priority encoder so the Output of Priority Encoder is **101**
th Block:

A and B two 2 bit Numbers				2 bit Magnitude Comparator (Output)		
A1	A0	B1	B0	A < B	A = B	A > B
0	0	1	0	0	1	0

b)

[0.5]

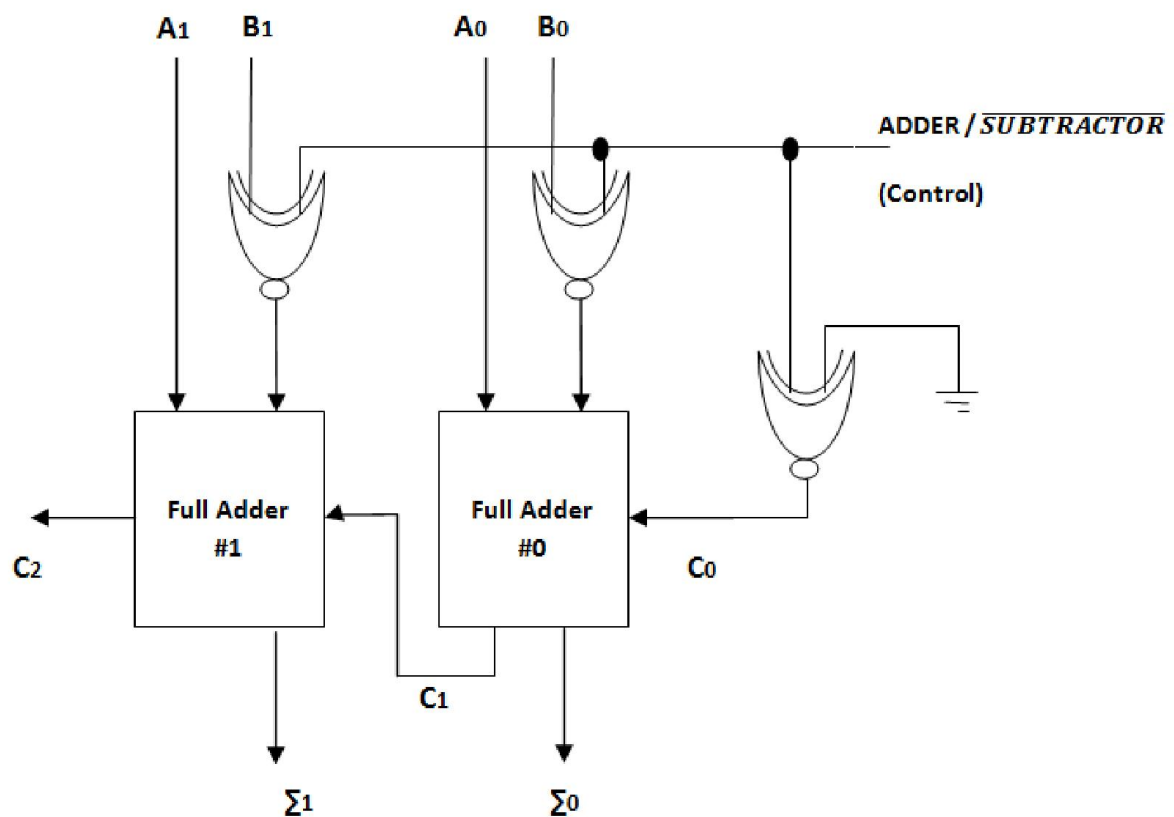

[0.5]

Control (X) <i>ADDER / SUBTRACTOR</i>	Mode of Operation
1	Adder
0	Subtractor